




Bipolar Transistor - Lecture 12



2012142219 Kim Hong-suk

From Before

▶ Active Forward Bias(Region)

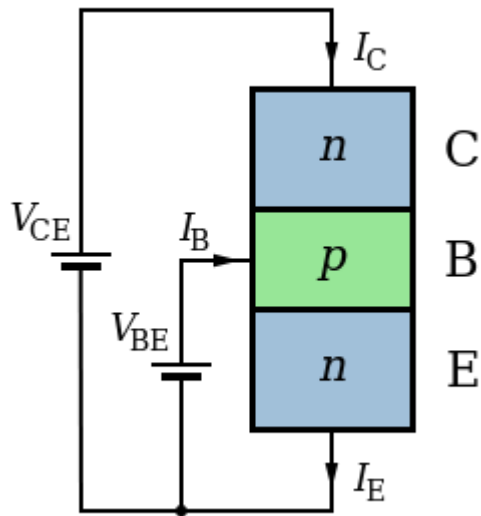


By KVL

$$V_{CB} = V_{CE} - V_{BE} \geq 0$$



Collector Current

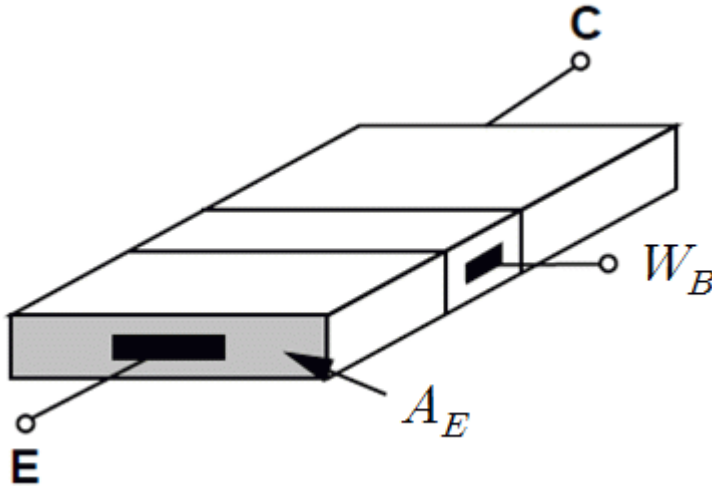

$$I_s = \frac{A_E q n_i^2 D_n}{W_B N_B}$$

- ▶ A_E -> Emitter Area
- ▶ W_B -> Base Width
- ▶ N_B -> Doping in Base



Collector Current

$$I_c = I_s \exp\left(\frac{V_{BE}}{V_T} - 1\right)$$


- ▶ In most case the -1 can be negligible.

$$I_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow V_{BE} = V_T \ln \frac{I_C}{I_s}$$



I_C vs V_{CE}

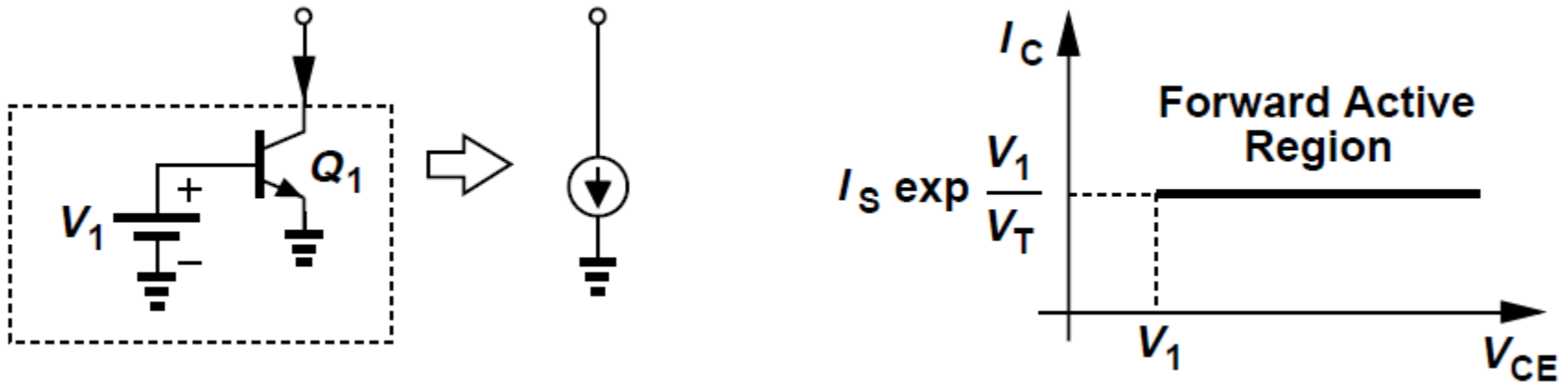- ▶ First, consider I_C with $V_{BE} = \text{const.}$




- ▶ It behaves like voltage-dependent current source.
-




I_C vs V_{CE}

- ▶ When V_{BE} changes.

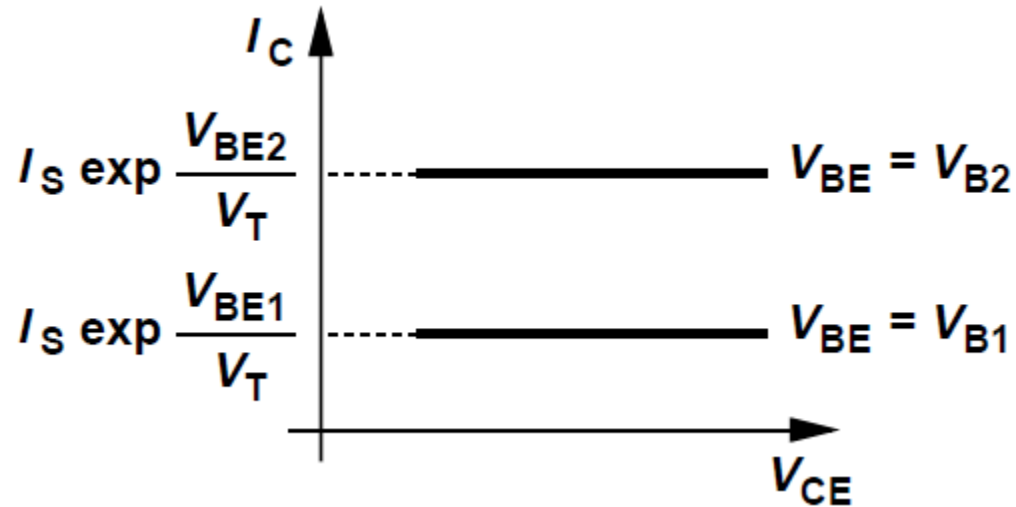

I_C vs V_{CE}

- ▶ I_B is proportional to I_C

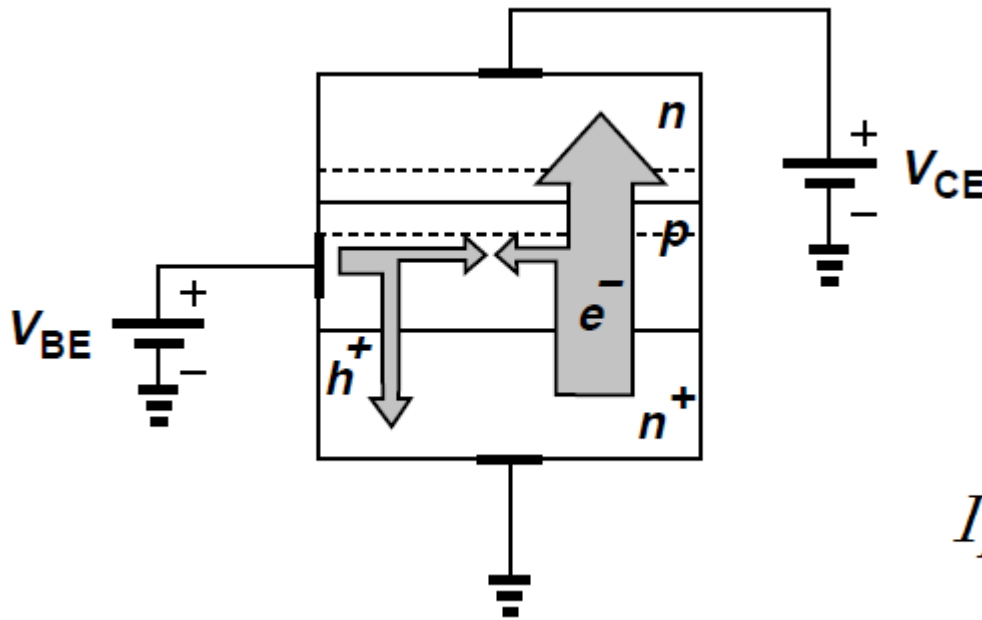

$$I_C = \beta I_B$$

By KCL

$$\begin{aligned} I_E &= I_C + I_B \\ &= \left(1 + \frac{1}{\beta}\right) I_C \end{aligned}$$

$$I_E = \frac{\beta + 1}{\beta} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$I_C \approx I_E$$

Thank you

