
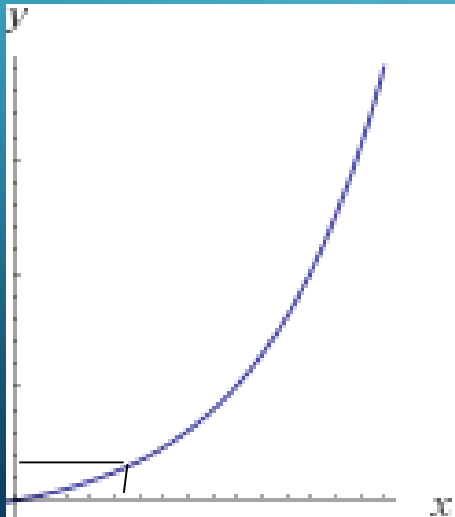


A decorative graphic on the left side of the slide, consisting of white and light blue lines forming a circuit board pattern with various nodes and connections.

BIAS AND TRANSCONDUCTANCE



15.10.08 2014142052 석민호

SIMPLE AMPLIFIER

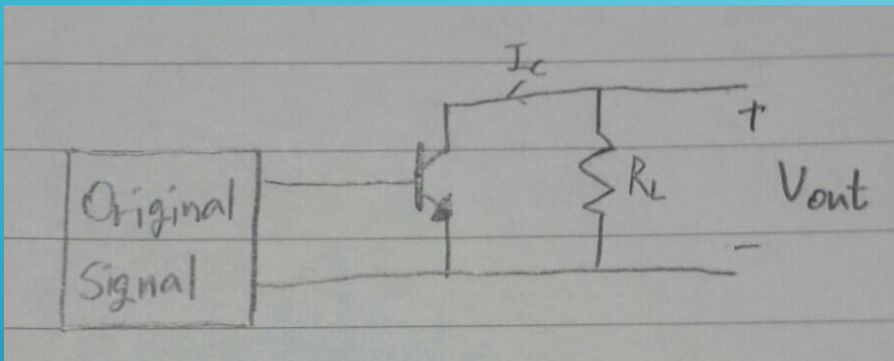

- $I_c = \frac{-V_{out}}{R_L}$
- $V_{out} = -R_L I_c$
$$= -R_L I_s \left\{ \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right\}$$
- V_{BE} moves 0~10mV, I_c moves 0~5 × 10⁻¹⁶A
- if we want V_{out} to be 0~100mv, IMPOSSIBLY LARGE RESISTANCE is needed

BIASING

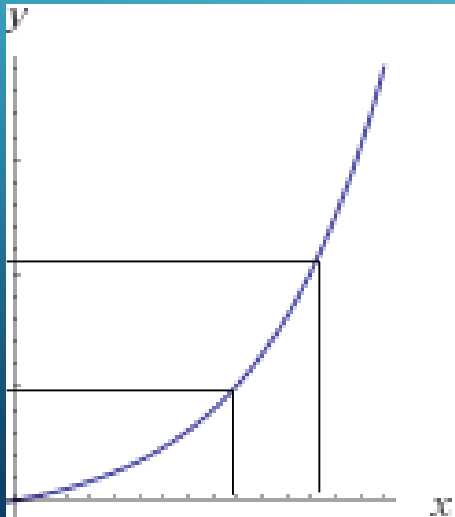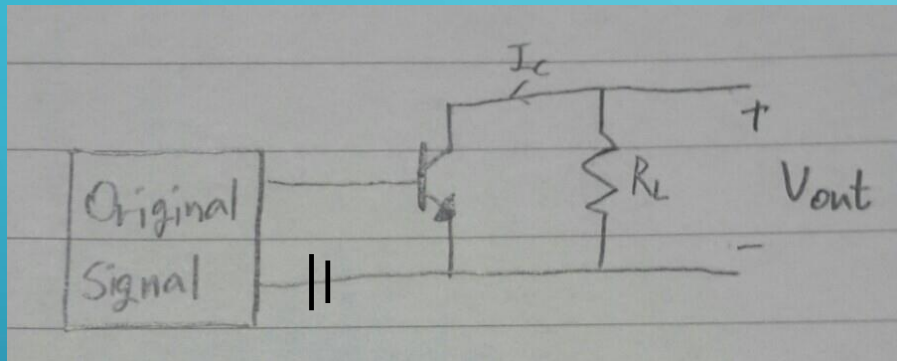

- Biasing
- Adding the battery 750mV, I_C moves 1.7mA \Rightarrow 128 Ω R_L needed
- Operating point determines how transistor works

TRANSCONDUCTANCE

- Transconductance means how sensitively collector current moves
- $g_m = \frac{dI_c}{dV_{BE}} = \frac{d}{dV_{BE}} \left(I_s \exp \left(\frac{V_{BE}}{V_T} \right) \right)$
$$= \frac{I_s}{V_T} \exp \left(\frac{V_{BE}}{V_T} \right)$$
$$= \frac{I_c}{V_T}$$
- No bias means $g_m = 0$, no amplification. We need certain g_m
- Power consumption vs g_m
- “Small” means small fraction of V_T
- V_{CE} must be a constant