


Lesson 14&15

BJT Small-Signal Model 1,2

2014142192 심동훈

*Combining Time Response with I,V Characteristics

YouTube
Lecture 16

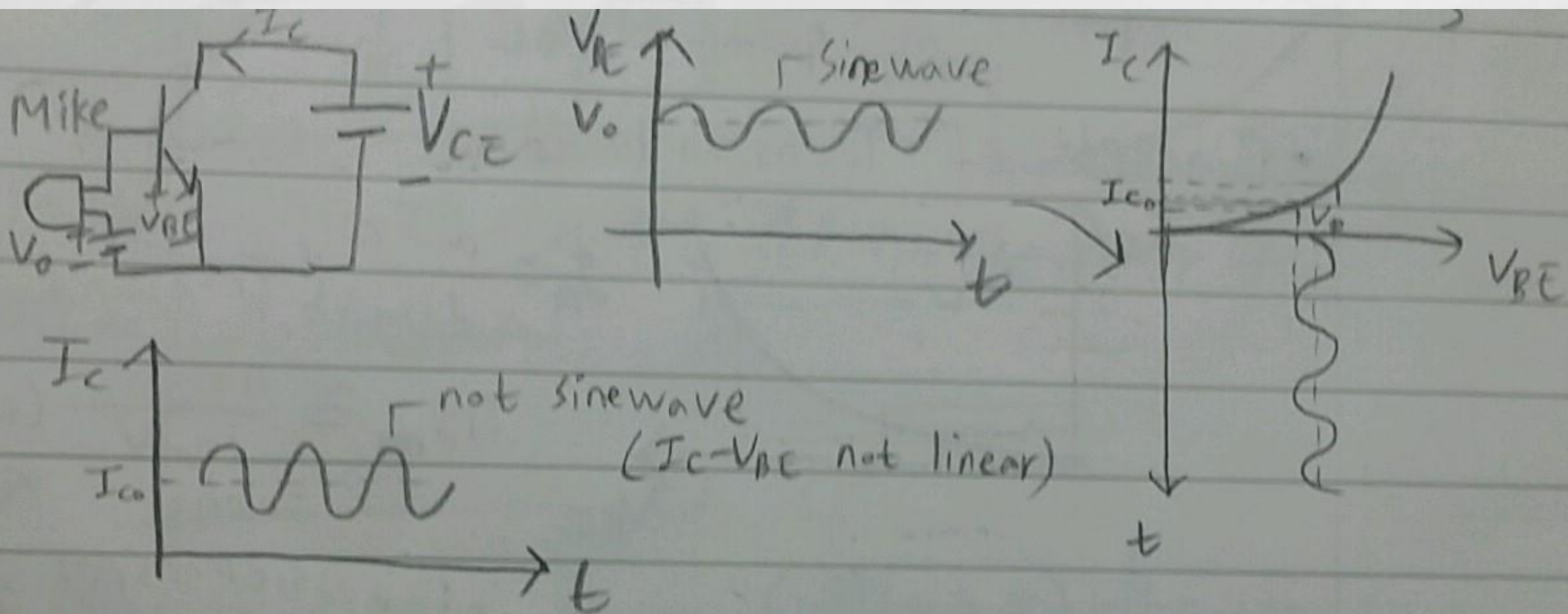


*Large-Signal and Small-signal

·We have to think about “Small-signal” operation for pervious page.

Large-Signal operation : the signal is arbitrarily large
=>Change of I_C is larger than I_{C0}

Small-Signal operation

=>Ch

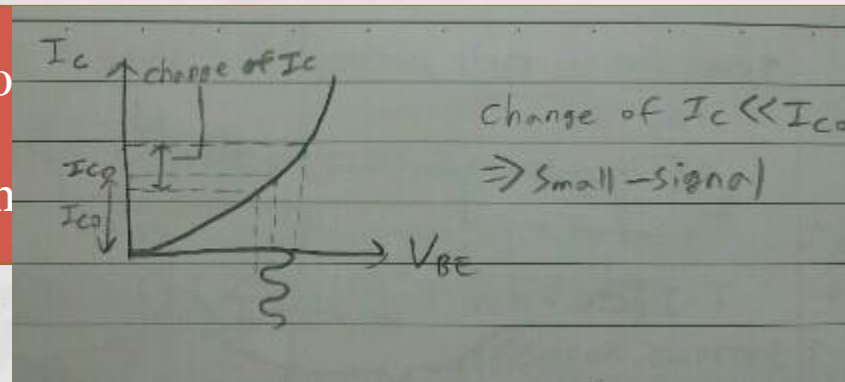

only a

*Combining Time Response with I,V Characteristics in Small-Signal operation 1

•In page 2, we know $I_C = I_S \exp \frac{V_o + V_m \sin \omega t}{V_T}$.


$$\approx I_S \exp \frac{V_o}{V_T} \left(1 + \frac{V_m \sin \omega t}{V_T} \right) \quad (e^\varepsilon \approx 1 + \varepsilon \text{ if } \varepsilon \ll 1)$$

$$= I_{C0} \left[1 + \frac{I_{C0}}{V_T} V_m \sin \omega t \right]$$






g_m

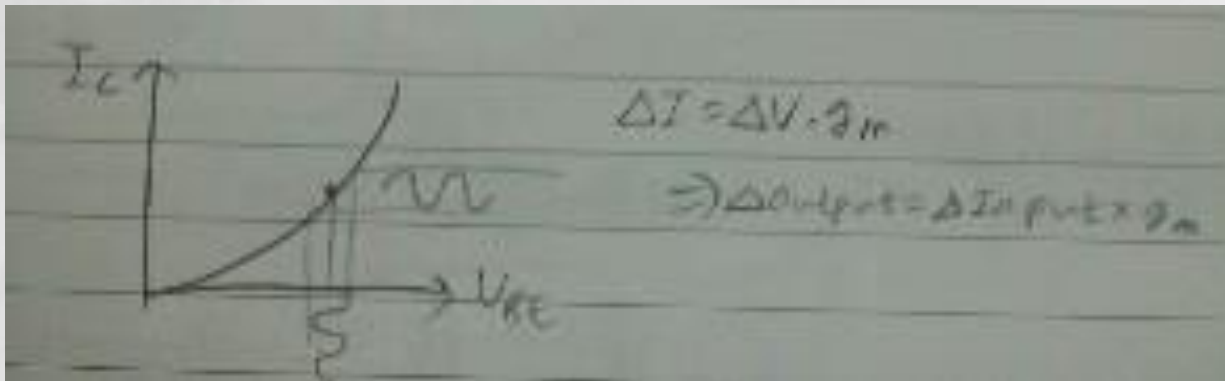*Combining Time Response with I,V Characteristics in Small-Signal operation 2




Linear!


*Simple Bipolar Transistor Model

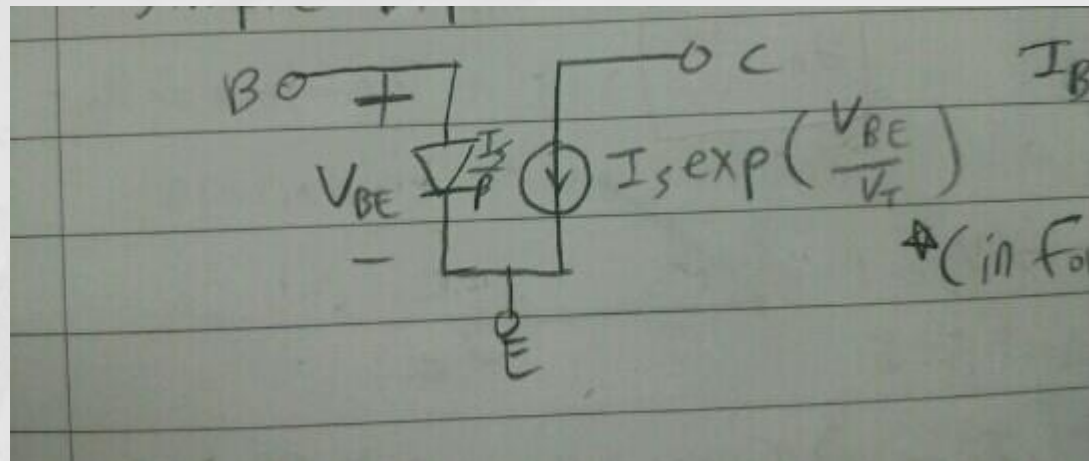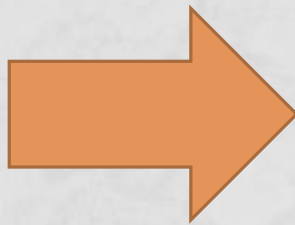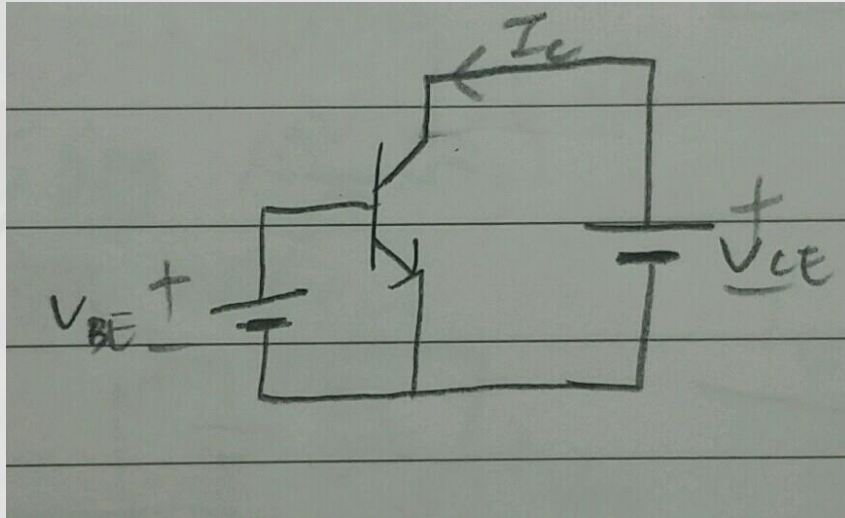

*Small-Signal Model 1

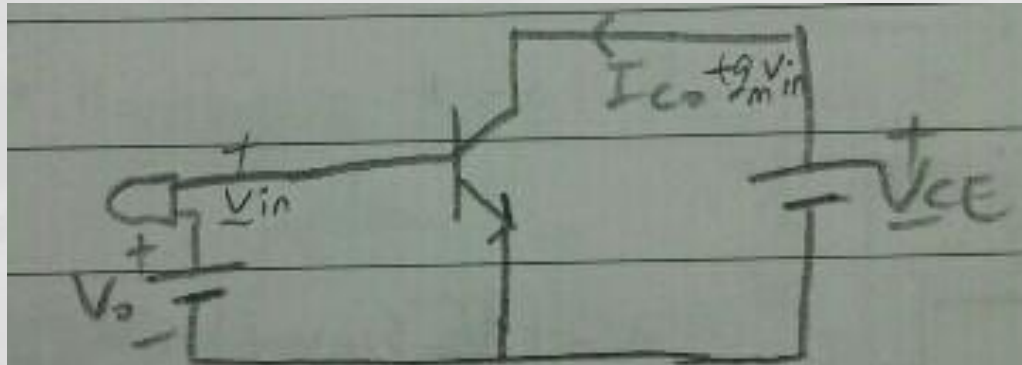


YouTube
Lecture 17

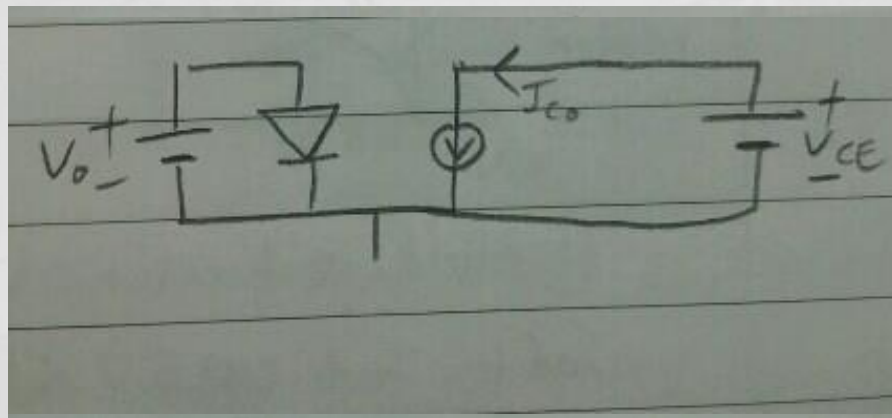


?

*Small-Signal Model 2

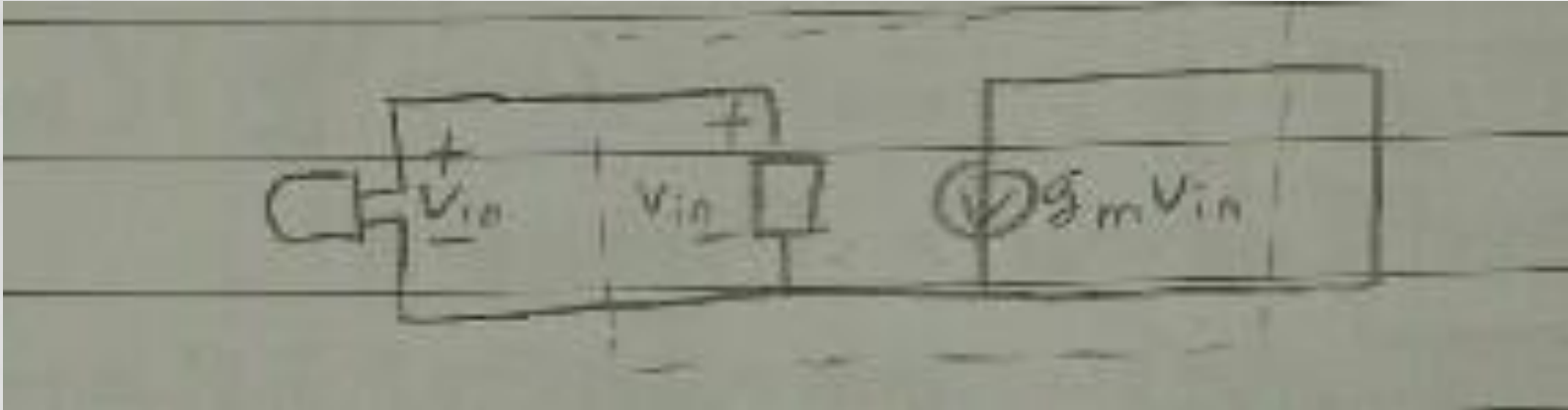·First, we can expect Small-signal Model like below picture.




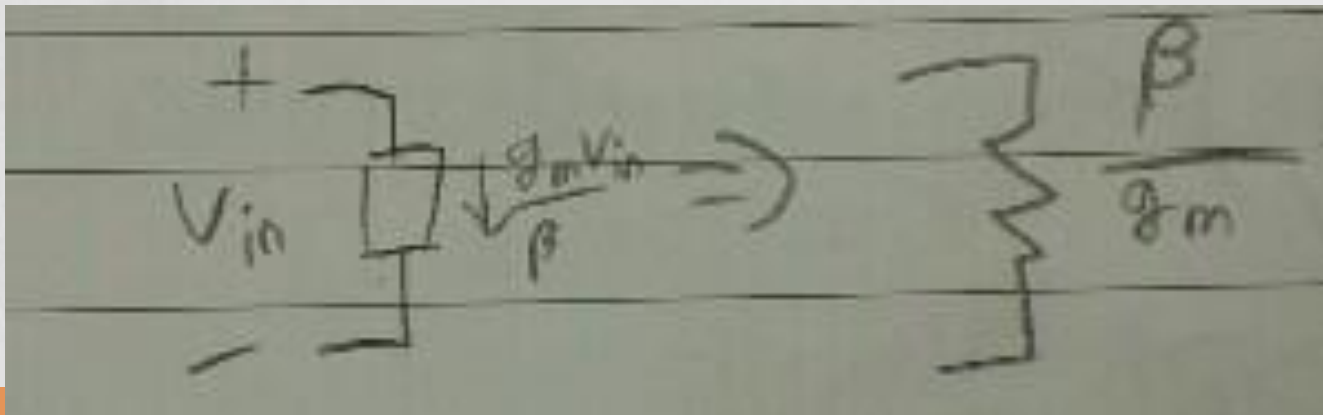·Second, we expect rectangle device for I_B .



*Small-Signal Model 3

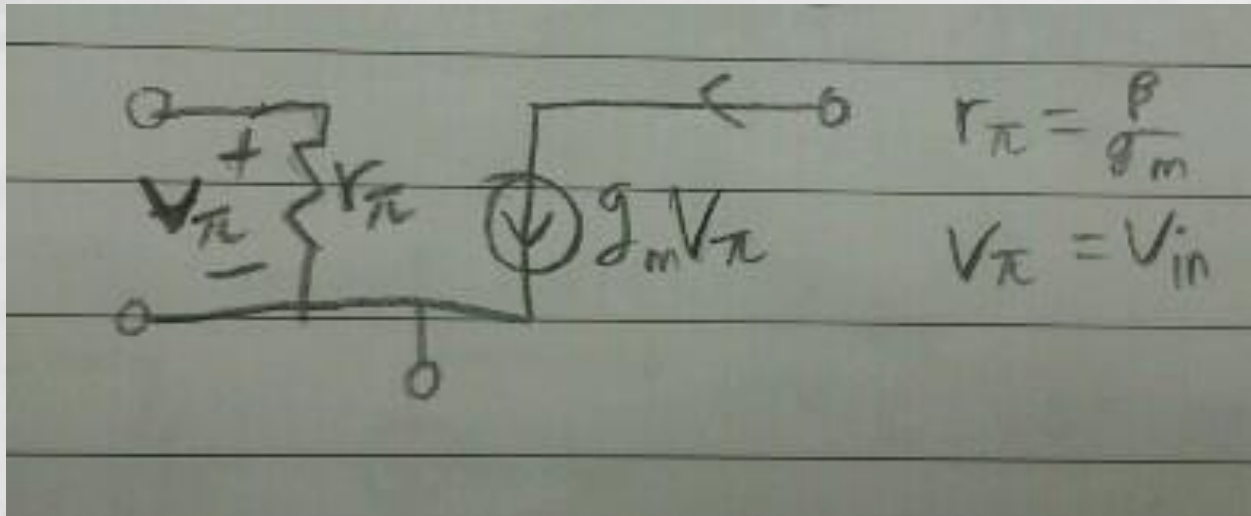·Finally, we can draw Small-Signal Model!



*Small-Signal Model(Note)

·To find small-signal parameters, we must first calculate the bias conditions.

·In small-signal operation, batteries are replaced with a short circuit.

·Notation

Large-signal quantities : uppercase


- $V_{in}, I_C, V_{BE}, V_{CE} \dots$

Small-signal quantities : lowercase

- $v_{in}, i_C, v_{BE}, v_{CE} \dots$

*Early effect 1

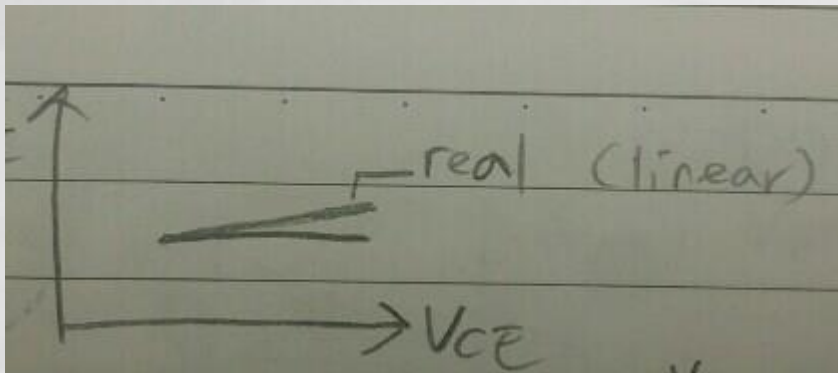• In real bipolar transistors, I_C is not constant according to V_{CE} .



WHY?

Because V_{CE} change depletion region of C-B
=> concentration of electrons is more sharply decrease
=> Current increase!

*Early effect 2

$$I_S = \frac{AqD_n n_i^2}{N_B W_B}$$

$V_{CE} \uparrow \Rightarrow W_B \downarrow$
 \Rightarrow Diffusion current \uparrow

$$*I_C = (I_S \exp \frac{V_{BE}}{V_T}) (1 + \frac{V_{CE}}{V_A}) \text{ in Large-signal}$$

** V_A = early voltage

*Official method of Small-Signal model derivation

YouTube
Lecture 18


Step 1. Assume the transistor is biased at a certain operating point

Step 2. Apply a voltage change between two terminals and measure the resulting current changes

Step 3. Model the current changes by proper electric devices


*Early effect in small-signal model 1

• Inclusion of early effect

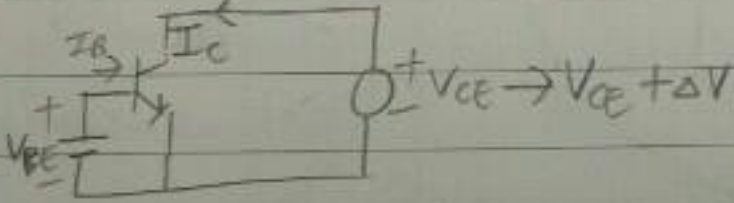
$$I_C + \Delta I_C = I_S \left(\exp \frac{V_{BE}}{V_T} \right) \left(1 + \frac{V_{CE}}{V_A} \right) + I_S \left(\exp \frac{V_{BE}}{V_T} \right) \frac{\Delta V}{V_A}$$


I_C
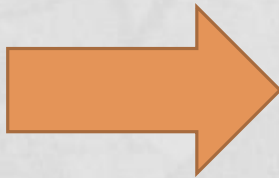
$$\Delta I_C = \left(I_S \exp \frac{V_{BE}}{V_T} \right) \frac{\Delta V}{V_A} \quad \text{linear}$$




Using resistance for ΔI_C , ΔV .

*Early effect in small-signal model 2

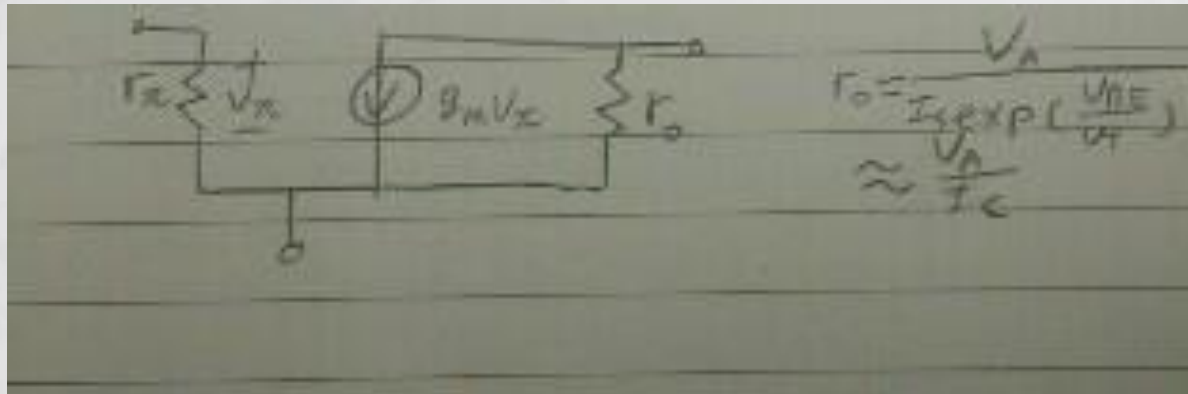

*Saturation region

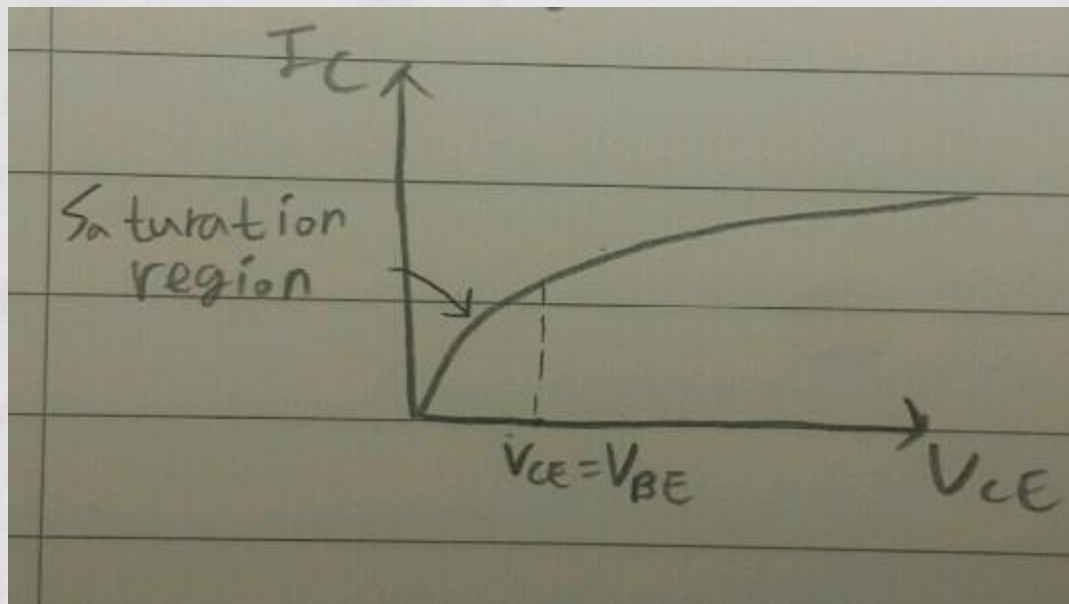- If $V_{CE} < V_{BE}$, we can't get desired value of anything because C-B is forward Bias.



The background of the slide features a faint, light-colored image of a group of people. Many of the individuals have their hands raised in the air, suggesting a moment of praise, thanksgiving, or a celebratory gesture. The image is centered and occupies most of the slide's area, with a blue horizontal bar at the top and an orange horizontal bar at the bottom.

Thank you