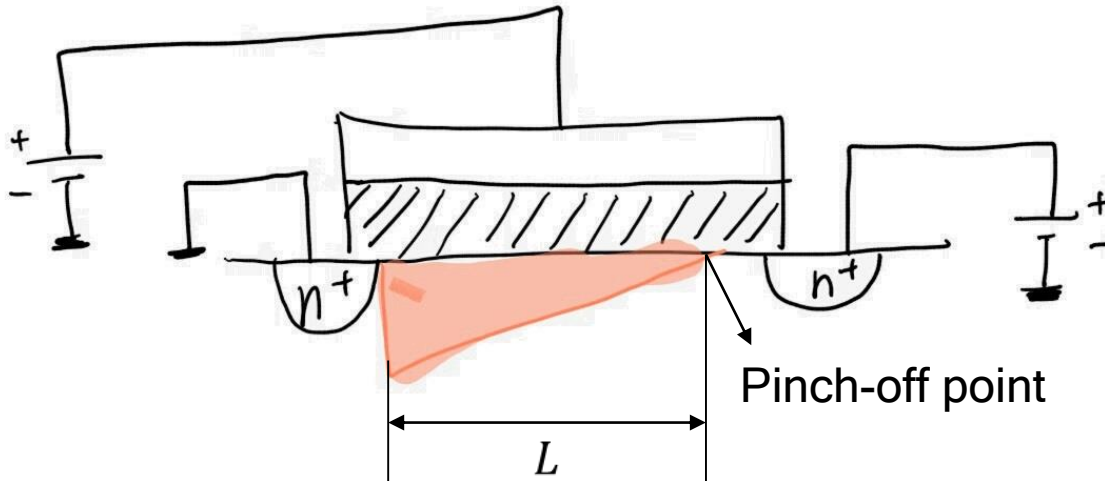


Lesson 27 : MOSFET Channel Length Modulation / Transconductance

Make by 성홍제

Lesson 27 : MOSFET Channel Length Modulation





$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$V_{DS} \uparrow \Rightarrow$ pinch - off point move left $\Rightarrow L \downarrow \Rightarrow I_D \uparrow$



Lesson 27 : MOSFET Channel Length Modulation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

λ : $\left[\frac{1}{V}\right]$ channel-length modulation coefficient

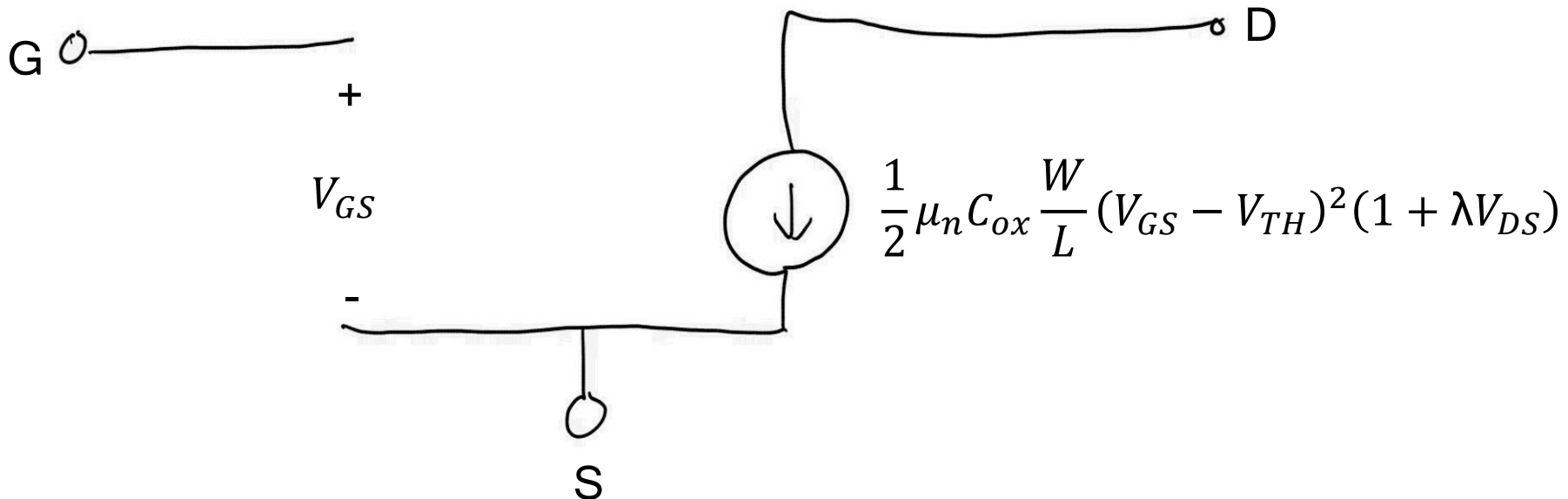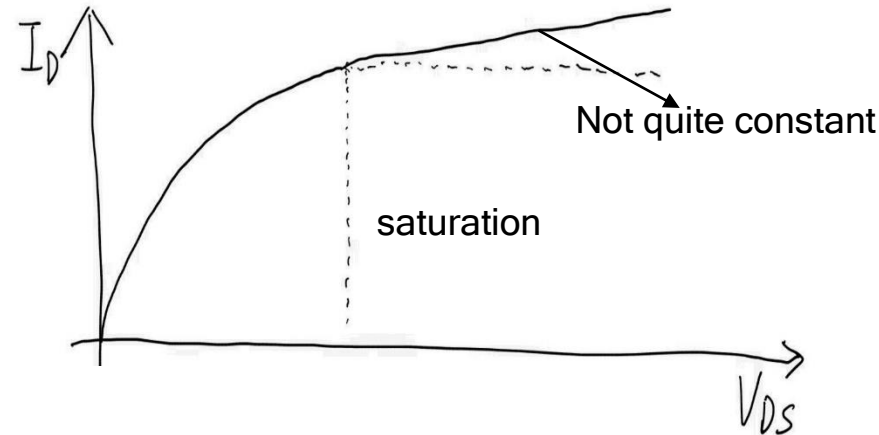

Lesson 27 : Biasing

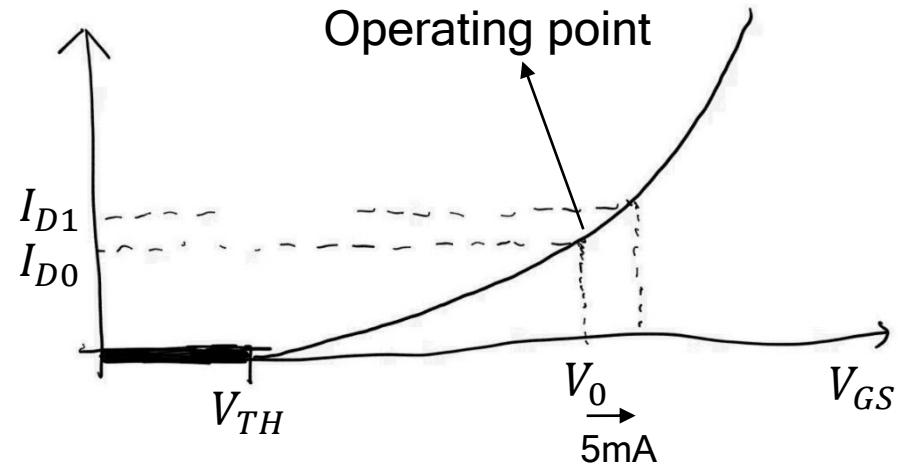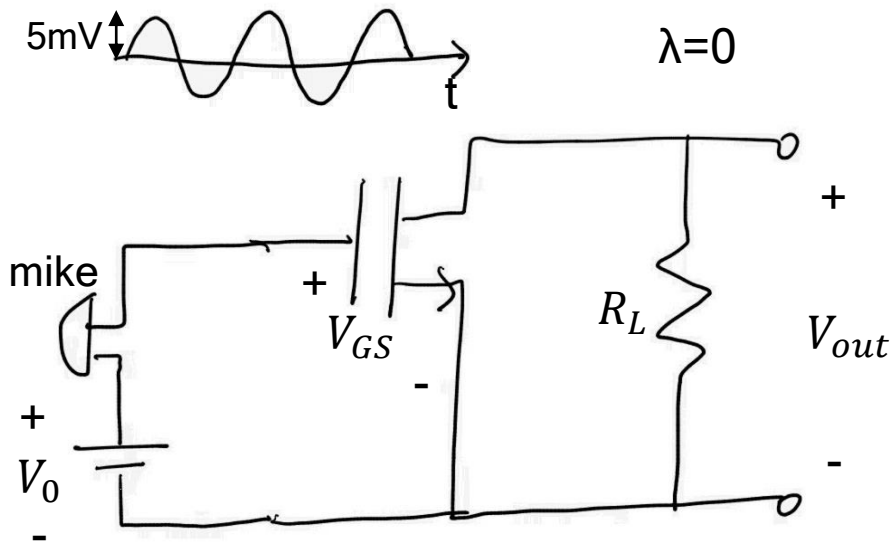


If $V_{TH} = 0.5V$, $\mu_n C_{ox} = 100\mu A/V^2$, $\frac{W}{L} = 10$ and choose $V_0 = 0.9V$

We want get 10 times amplitude

$$I_{D0} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.9V - 0.5V)^2 = 80\mu A$$

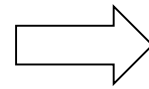
$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.905V - 0.5V)^2 = 82\mu A$$



$$R_L = \frac{50mV}{2\mu A} = 25K\Omega$$

Lesson 27 : Biasing

$$V_{GS} = V_{mike} + V_0$$

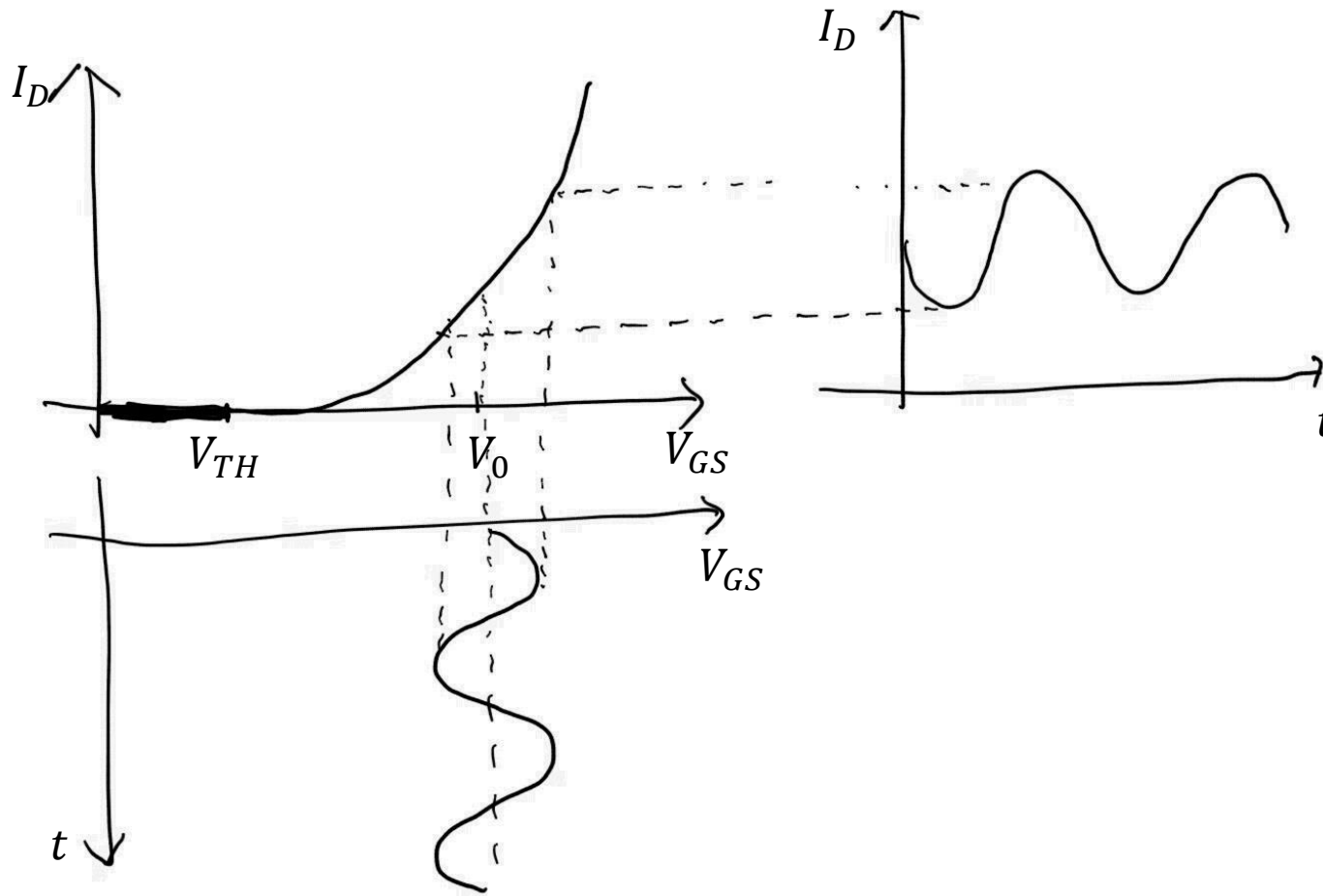

Lesson 27 : Concept of Transconductance

$$g_m = \frac{dI_D}{dV_{GS}} \quad \lambda=0$$



$$\text{unit : } \left[\frac{1}{V} \right], \text{ Siemens [S]}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$
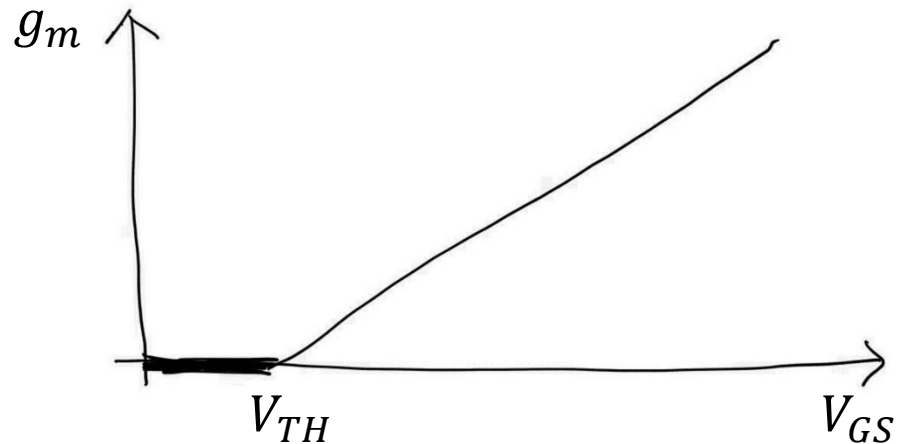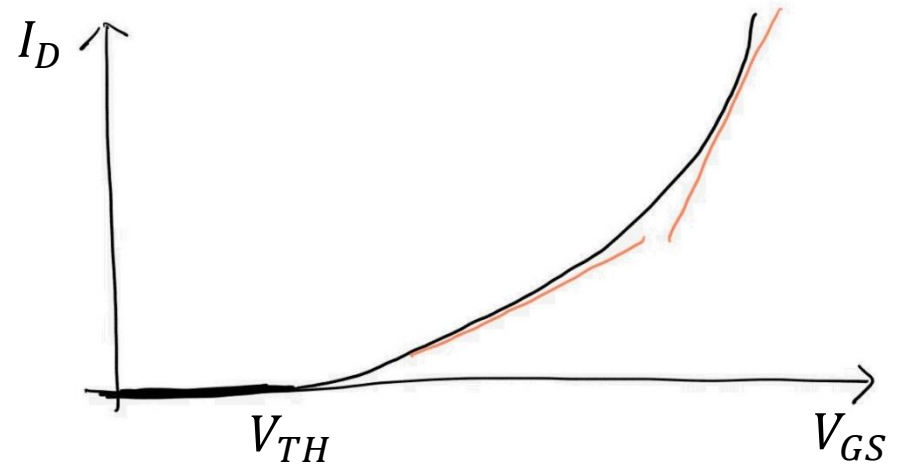
$$g_m = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}}$$



Thank you for watching!