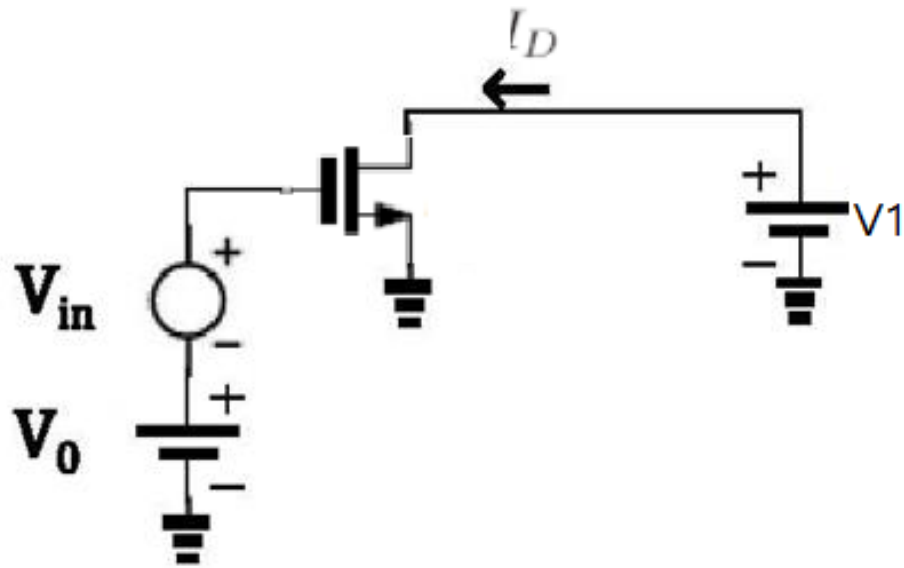


Lesson 28: Small-Signal Model



2012142164 Shin dong woo



$$\lambda = 0$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_0 - V_{TH} + V_m \sin \omega t)^2$$

Assume $V_m \ll V_0 - V_{TH}$ & $(1 + \epsilon)^2 \approx 1 + 2\epsilon$




$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_0 - V_{TH})^2 \left(1 + 2 \frac{V_m \sin \omega t}{V_0 - V_{TH}}\right)$$


$$I_{D0} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_0 - V_{TH})^2$$

$$I_D = I_{D0} + 2 \frac{I_{D0}}{V_0 - V_{TH}} V_m \sin \omega t$$

Bias current


signal current

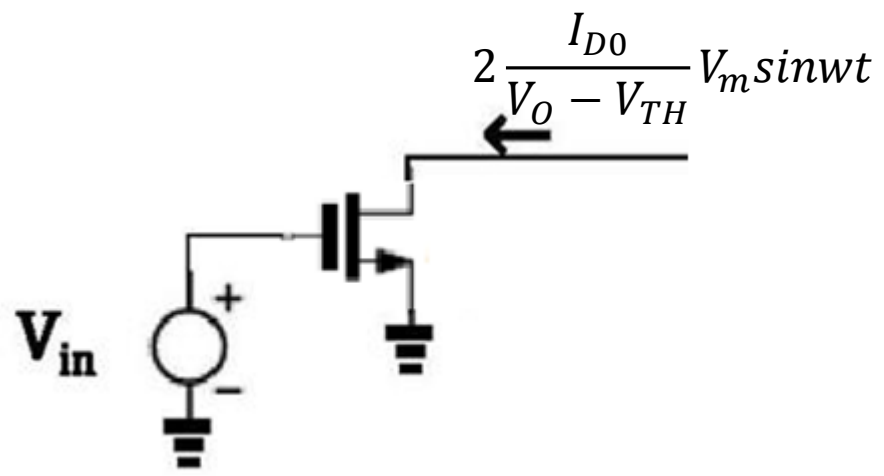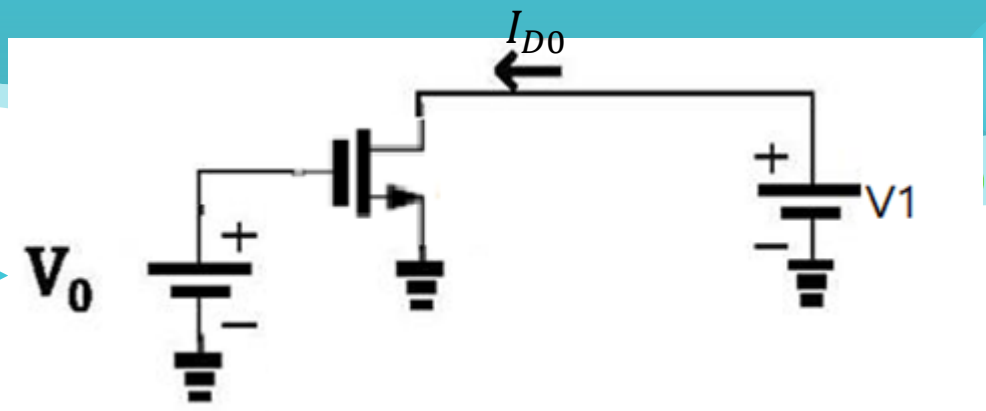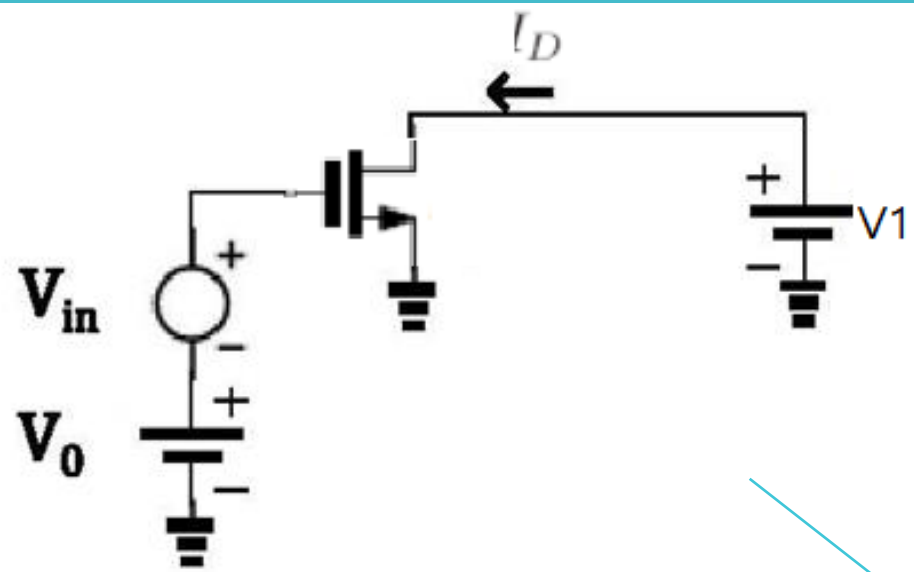

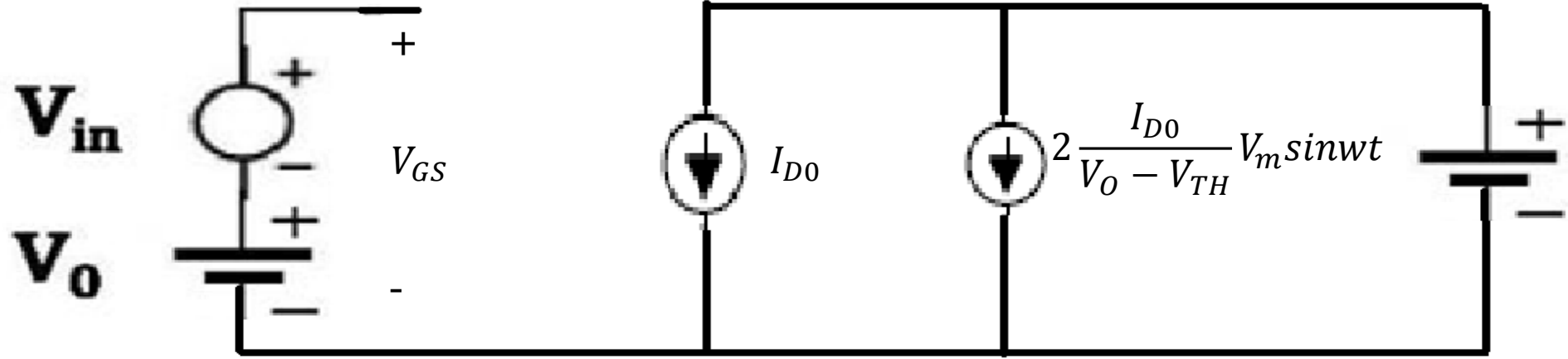


trans conductance

$$g_m = 2 \frac{I_{D0}}{V_O - V_{TH}}$$

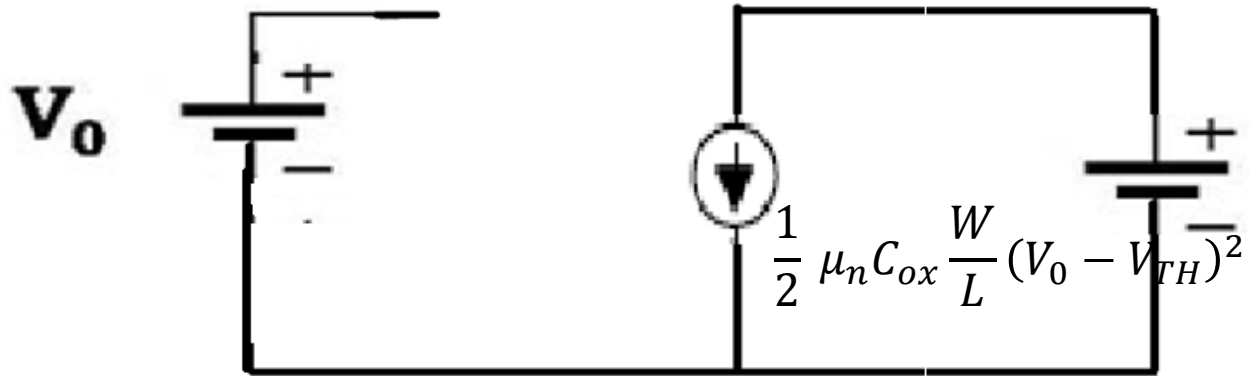


Large signal
(bias model) => const.

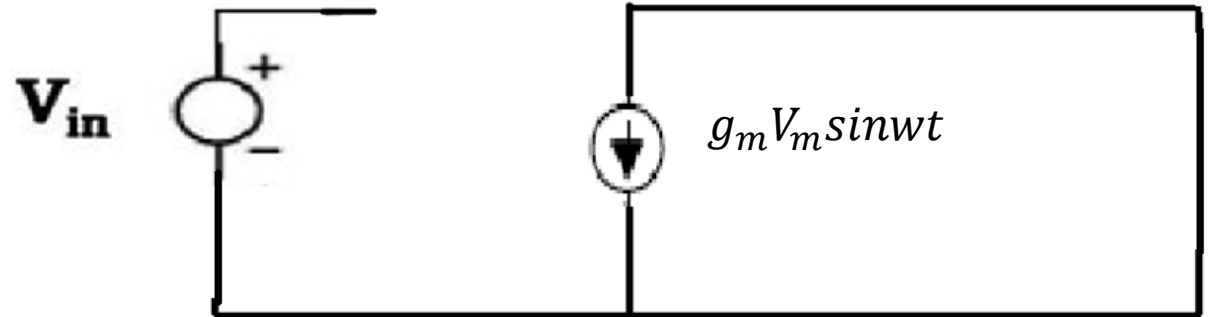


Small signal model
=> changed by time


General procedure for constructing a small signal model

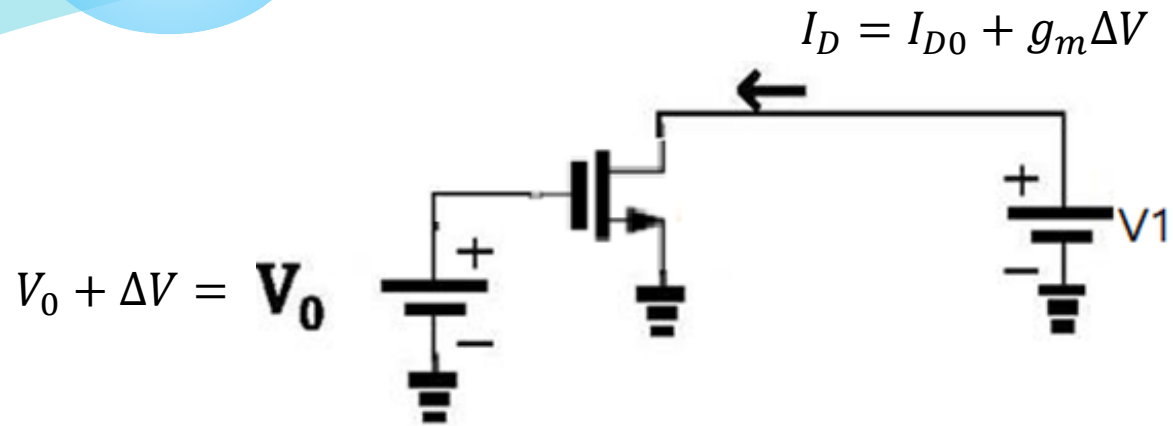1. Apply proper bias voltages to the device



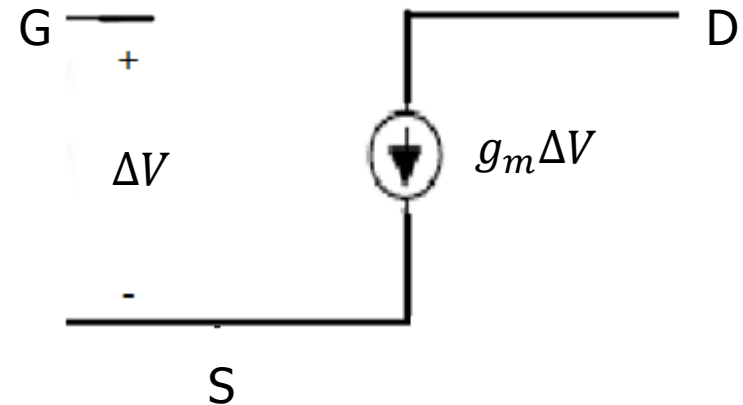2. Increment the voltage difference between two terminals.
3. Measure all current increments.
4. Model this change by a proper electrical device.



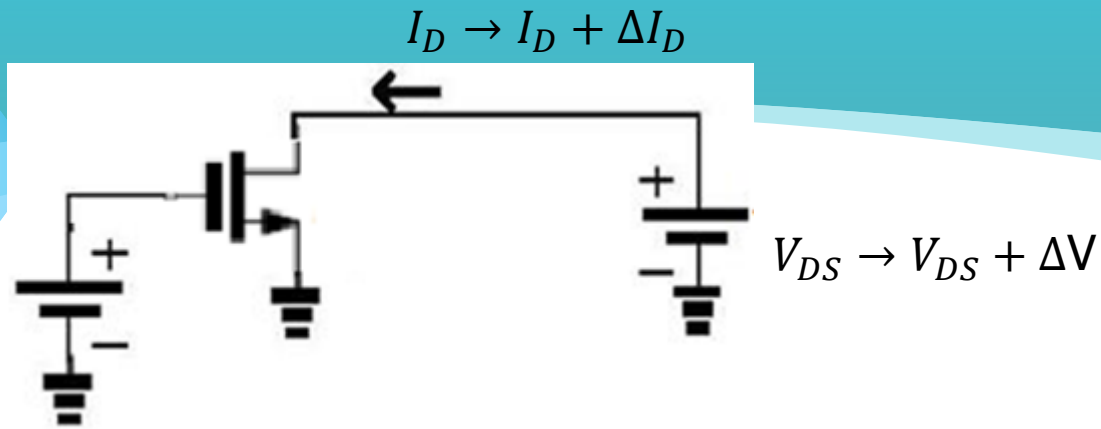


$$I_D + \Delta I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS} + \lambda \Delta V)$$

$$\Rightarrow \Delta I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (\lambda \Delta V)$$

$$\Rightarrow \frac{\Delta V}{\Delta I_D} = \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda \right)^{-1}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$
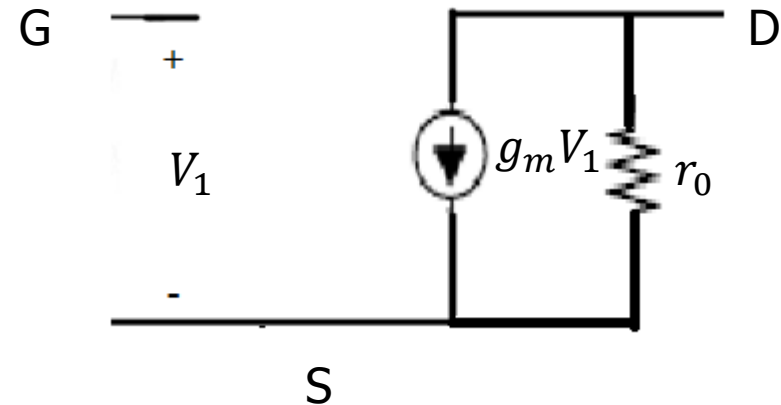
$$\frac{\Delta V}{\Delta I_D} \approx \frac{1}{\lambda I_D} = r_0$$





THANK YOU FOR LISTENING