

Review Presentation

L33 : Source Follower

2014142019

황순욱


Youtube Lecture.41

Content

1. What is Source Follower?
2. Voltage gain of Source Follower
3. Impedance of Source Follower
4. Biased design




What is Source Follower?

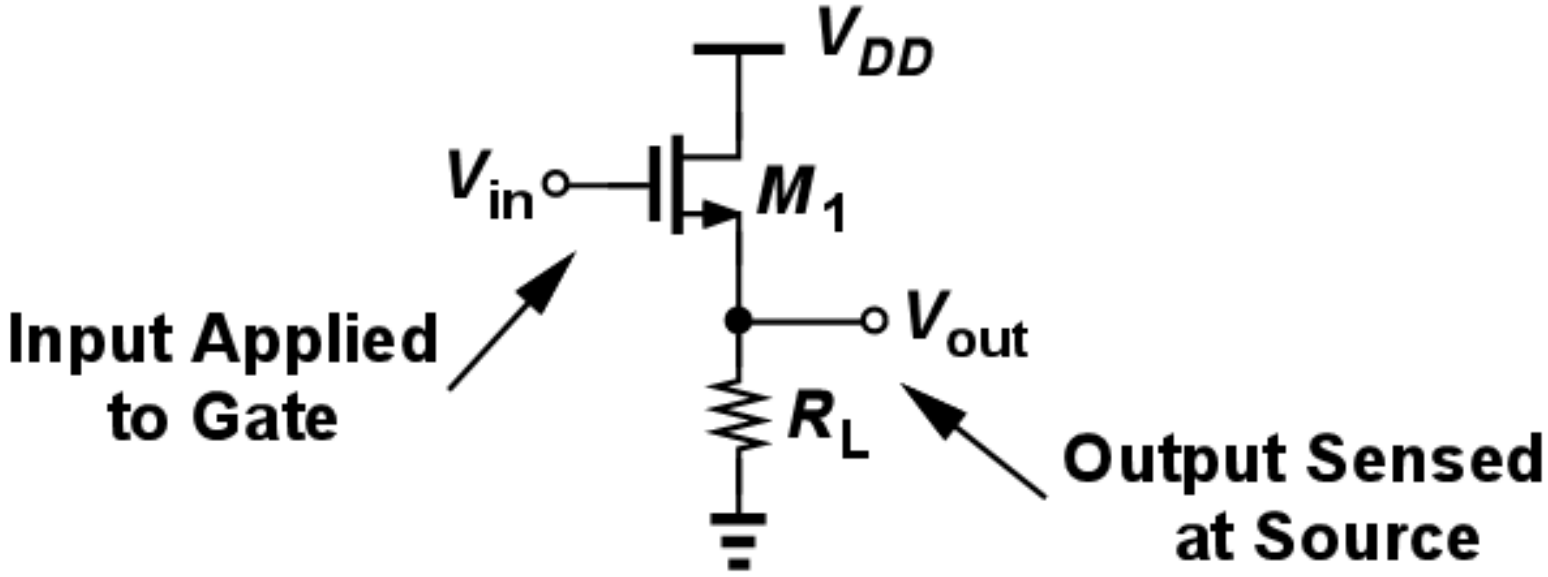

Voltage gain of Source Follower

(When λ is 0)

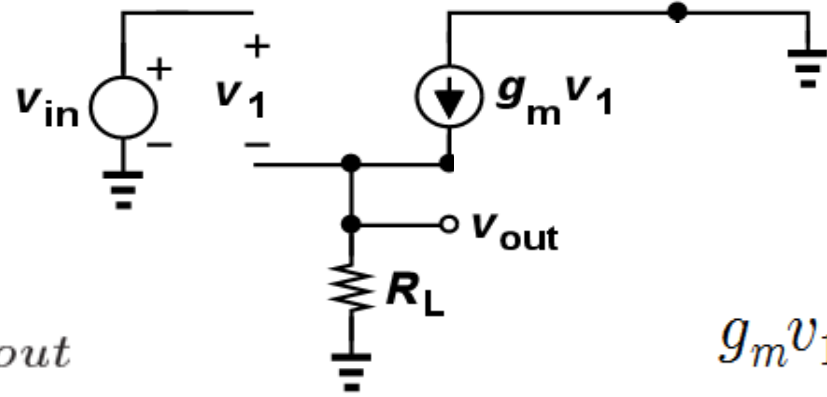

$$v_{in} = v_1 + v_{out}$$

$$g_m v_1 = \frac{v_{out}}{R_L}$$



$$\frac{v_{out}}{v_{in}} = \frac{R_L}{\frac{1}{g_m} + R_L}$$

$$\frac{v_{out}}{v_{in}} = \frac{\text{resistance tied between source and ground}}{\frac{1}{g_m} + \text{resistance tied between source and ground}}$$



Voltage gain of Source Follower

(When λ is not 0 , $\lambda > 0$)

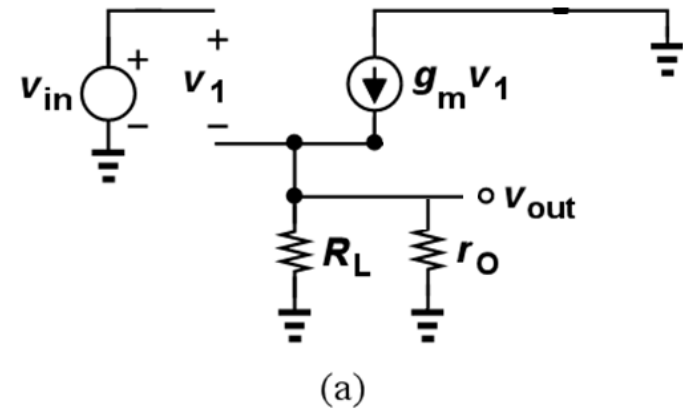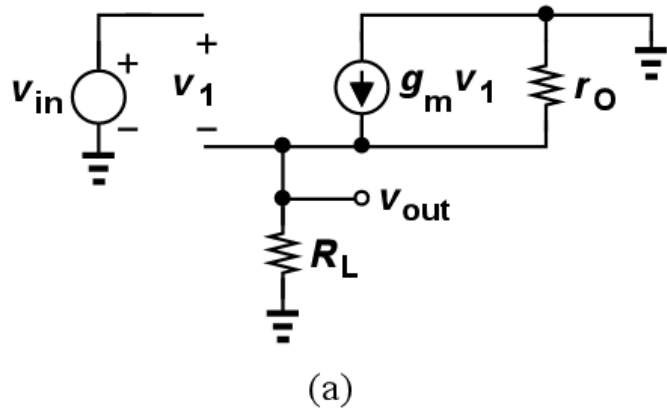

$$\frac{v_{out}}{v_{in}} = \frac{\text{resistance tied between source and ground}}{\frac{1}{g_m} + \text{resistance tied between source and ground}}$$




$$\frac{v_{out}}{v_{in}} = \frac{R_L || r_o}{\frac{1}{g_m} + R_L || r_o}$$

※ Voltage gain < 1 (when $R \uparrow$, $A_v \doteq 1$)



Impedance of Source Follower

(When λ is not 0 , $\lambda > 0$)

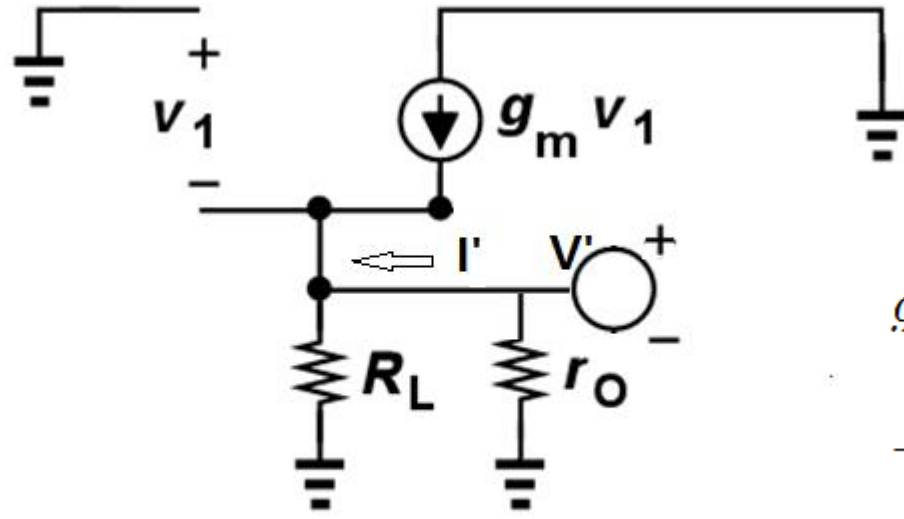

(a)

At low frequency,
 $R_{in} = \infty$

$$g_m v_1 + i' = \frac{v'}{r_o} + \frac{v'}{R_L}$$


$$-v_1 = v'$$

$$\frac{v'}{i'} = \frac{1}{g_m + \frac{1}{r_o} + \frac{1}{R_L}}$$

$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_L$$



Biased design

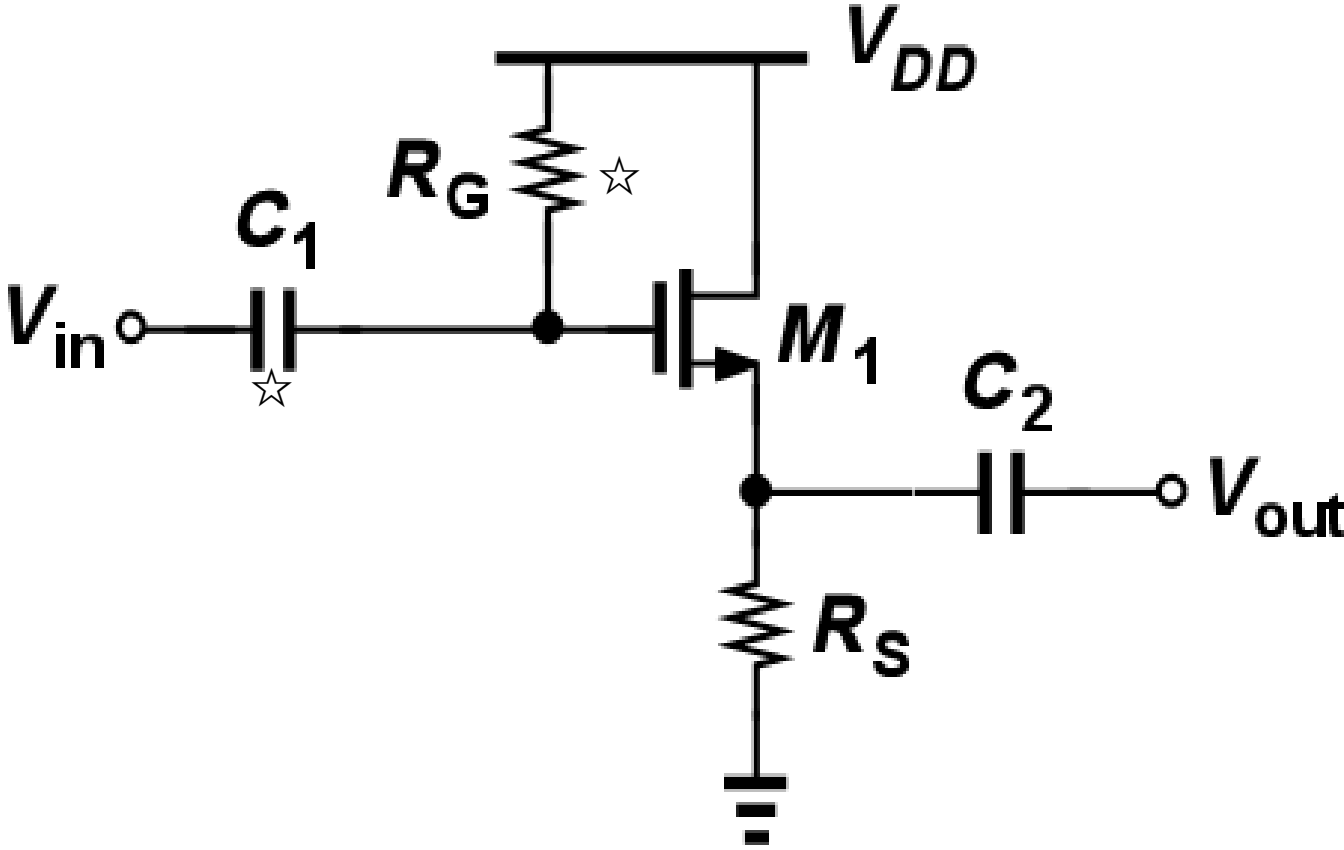

Thank you for listening.

