
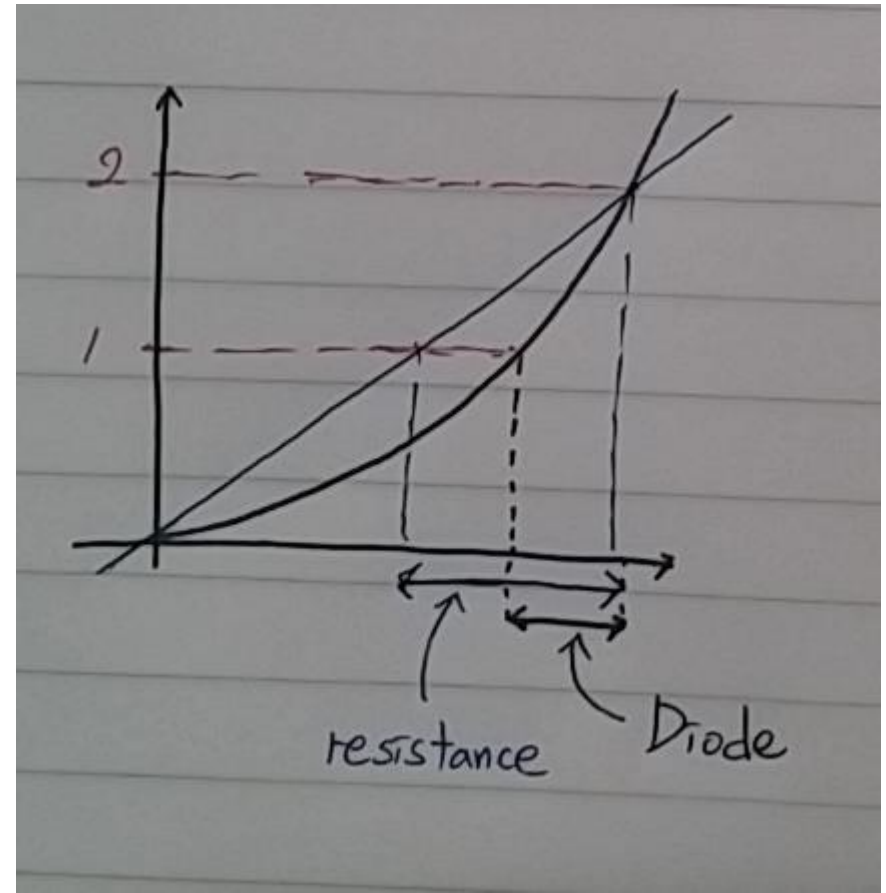
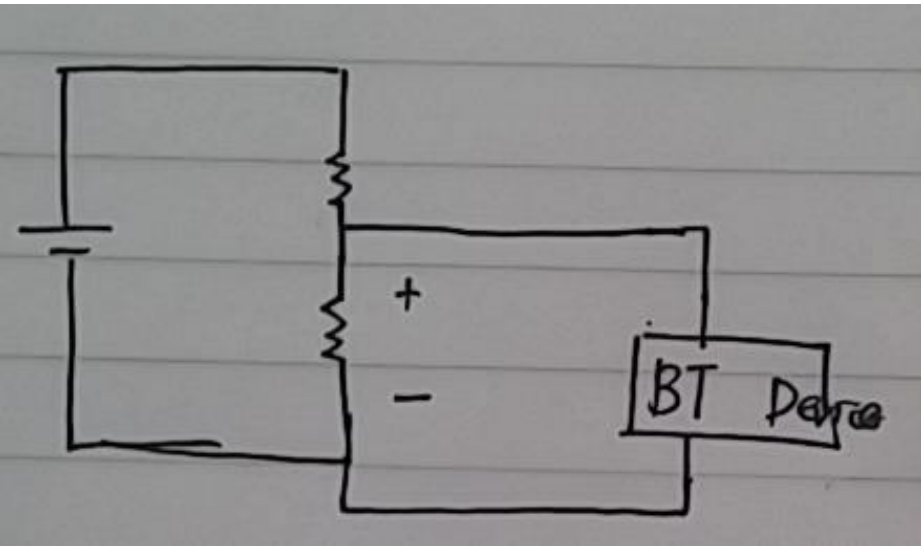


Lec 7

2009142050 이진배

1. Why use Diode, why not Resistor ?

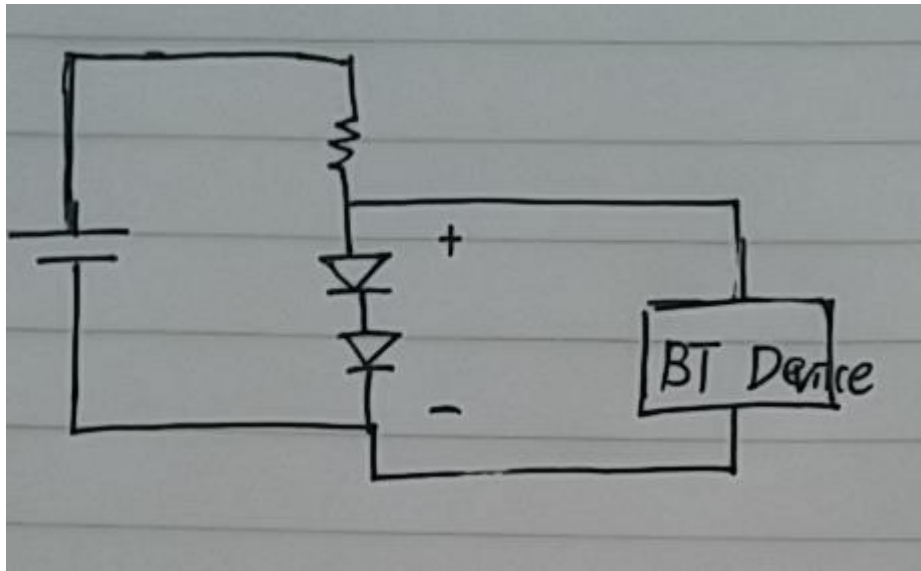

The voltage across each diode is a weak function of its current.



1. Why use Diode, why not Resistor?

- ➔ The voltage across each diode is a weak function of its current.
The diodes operate as a simple voltage regulator.


2. Principle of Diode Circuit Analysis

1. Begin by assuming certain states for all diodes check the final result against these assumptions.
2. If a diode is about to turn on or off, it must sustain a voltage of $V_{D,on}$ but its current is small.
3. If a diode is on and carries a current the current must flow from the anode to the cathode.


Example 1

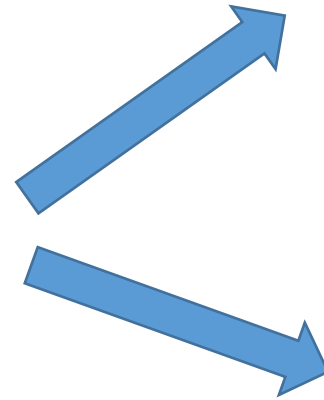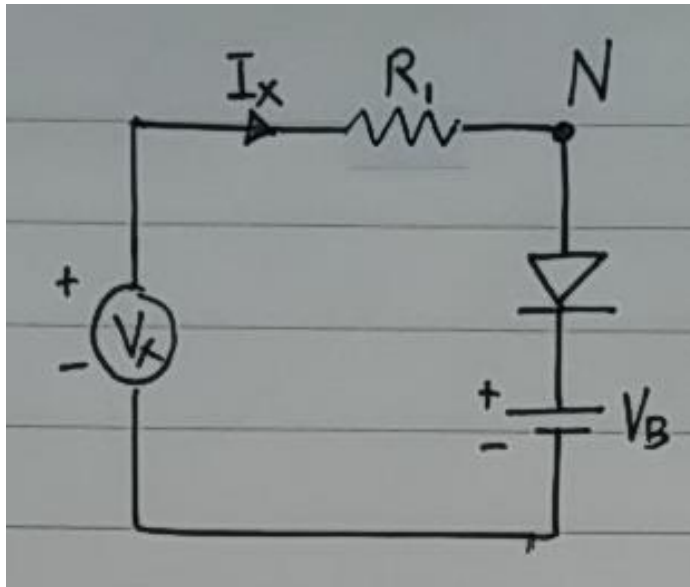

Reverse bias

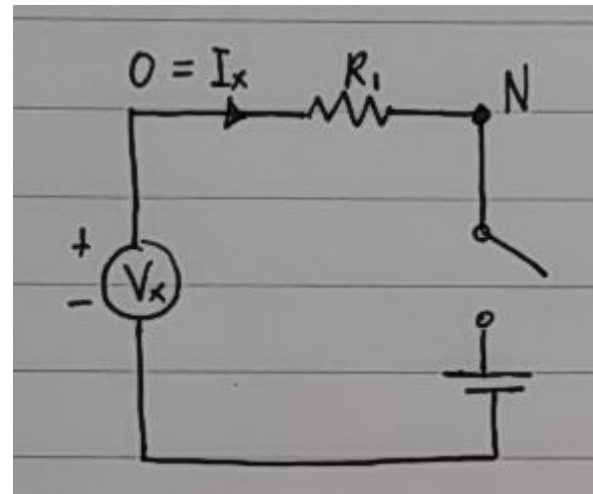

Forward bias

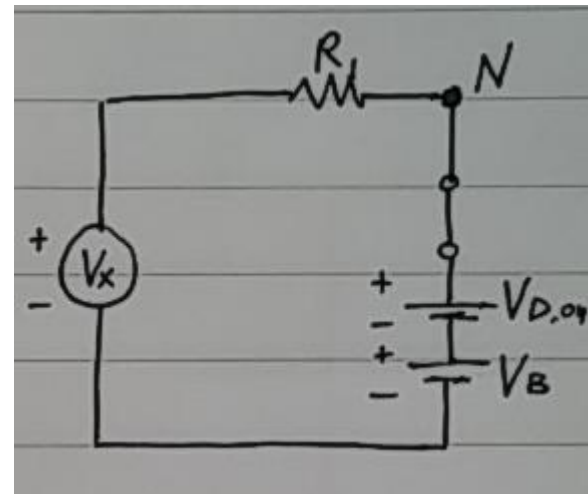

Find V_{x1}

$V_{x1} = \text{Point, diode turn on/off}$

$$V_{x1} = I_x R_1 + V_{D_{on,+}} + V_B$$




Because, $I_x = 0$ (principle 2)

$$V_{x1} = V_{D_{on,+}} + V_B$$

Example 1 : $I_x - V_x$ graph





Example 1 : $V_N - V_x$ graph

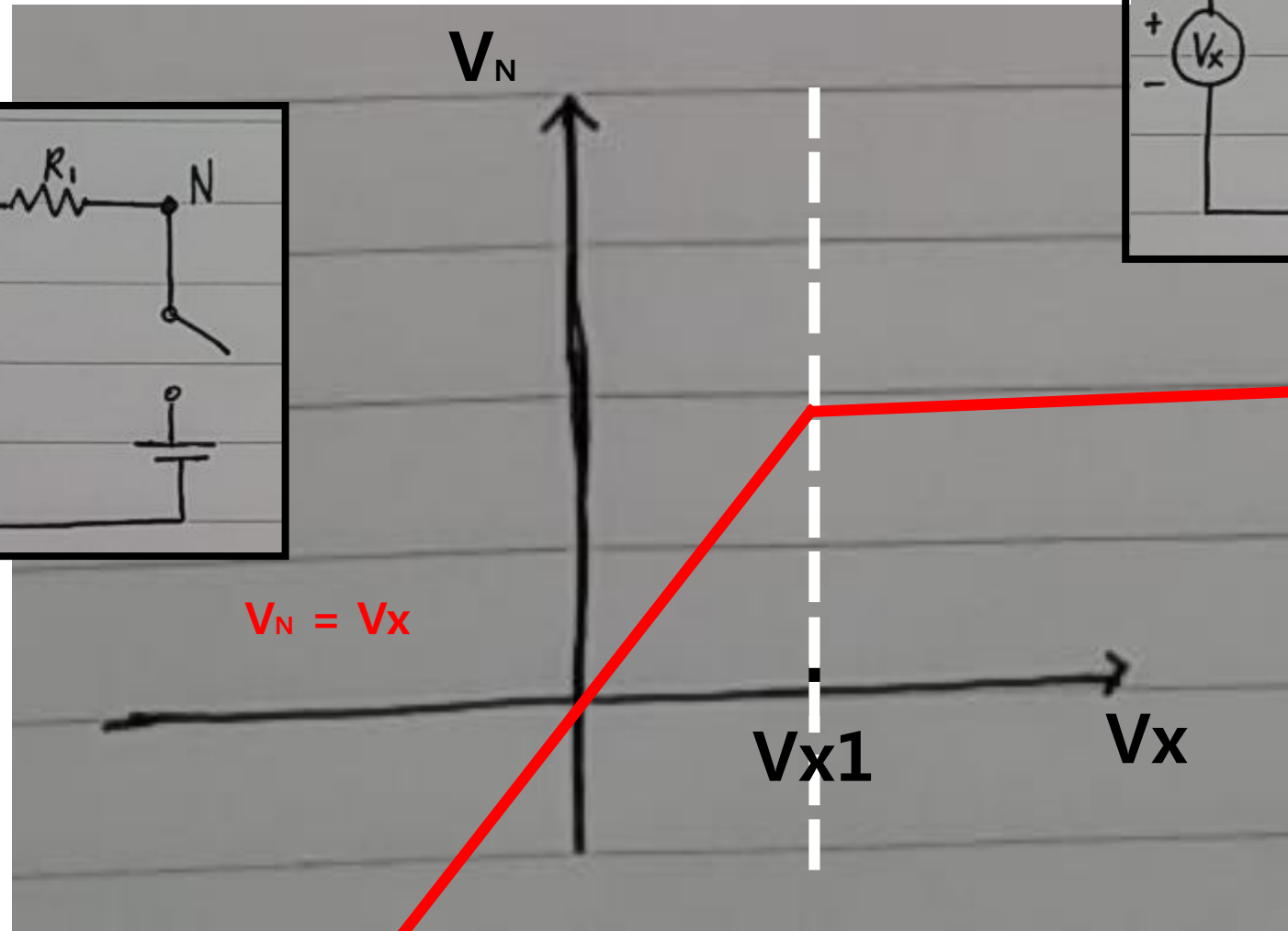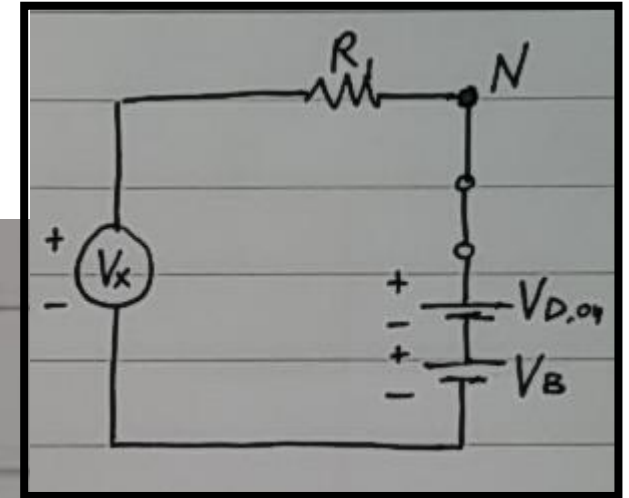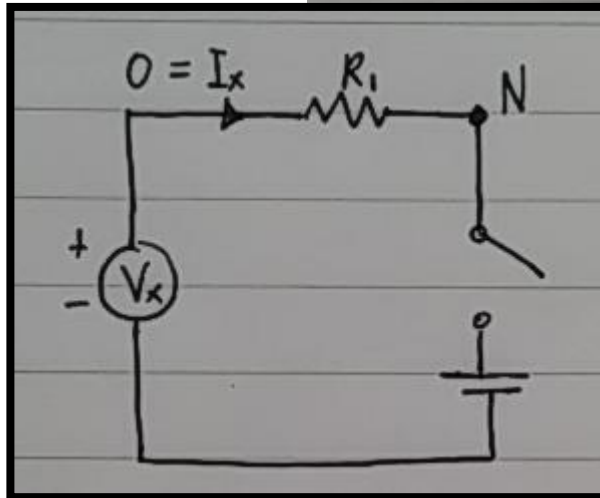


$$V_N = V_{D,09} + V_B$$

Example 2

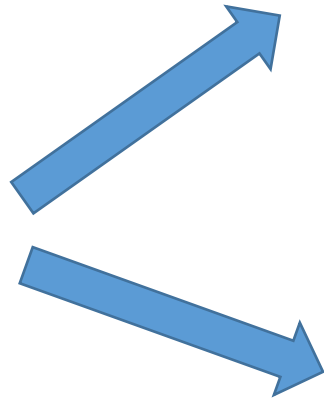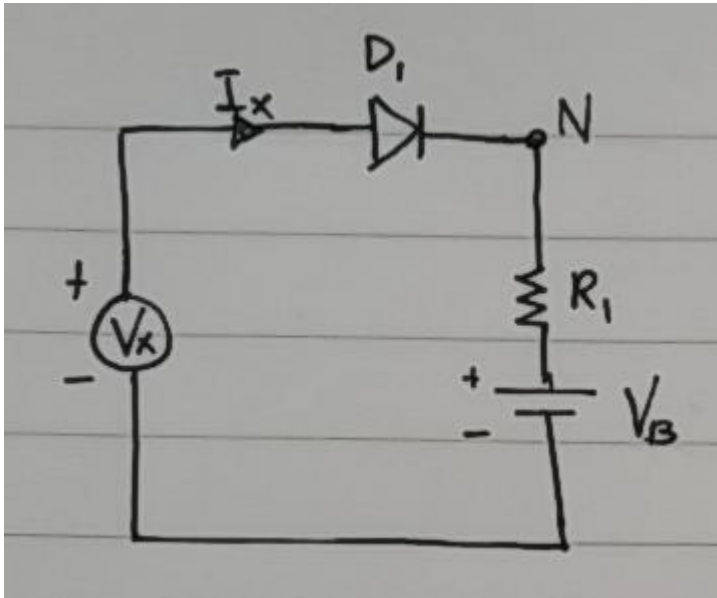

Reverse bias

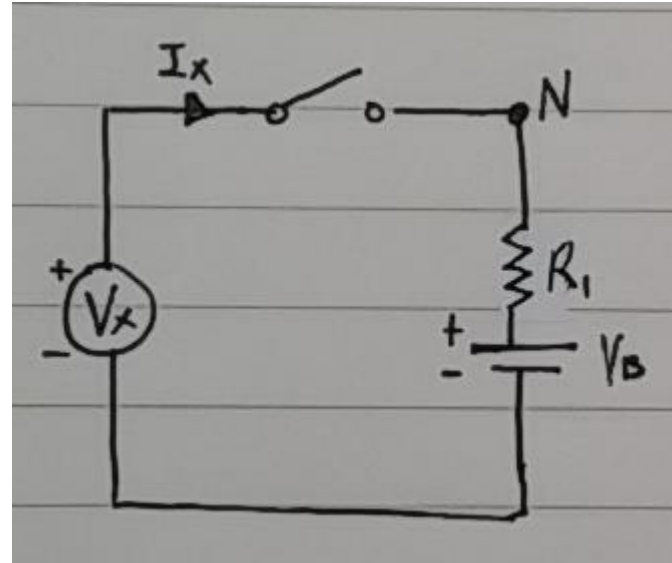


Find V_{x1}

$V_{x1} =$ Point, diode turn on/off

$$V_{x1} = I_x R_1 + V_{D_{on,+}} + V_B$$




Because, $I_x = 0$ (principle 2)

Forward bias

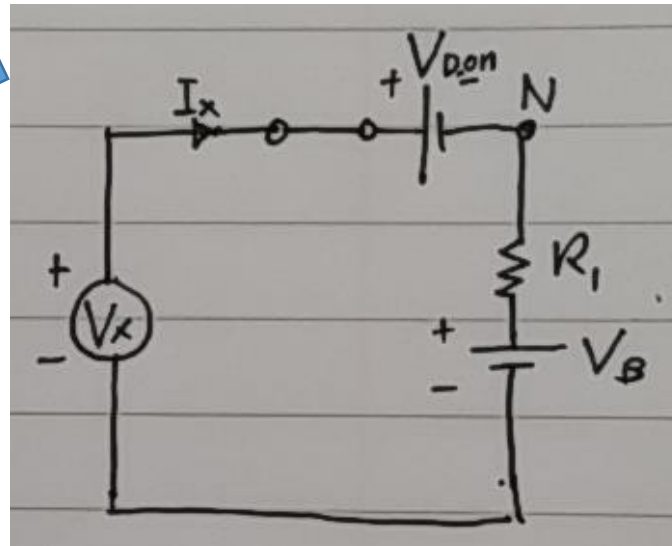

$$V_{x1} = V_{D_{on,+}} + V_B$$




Example 2 : $I_x - V_x$ graph

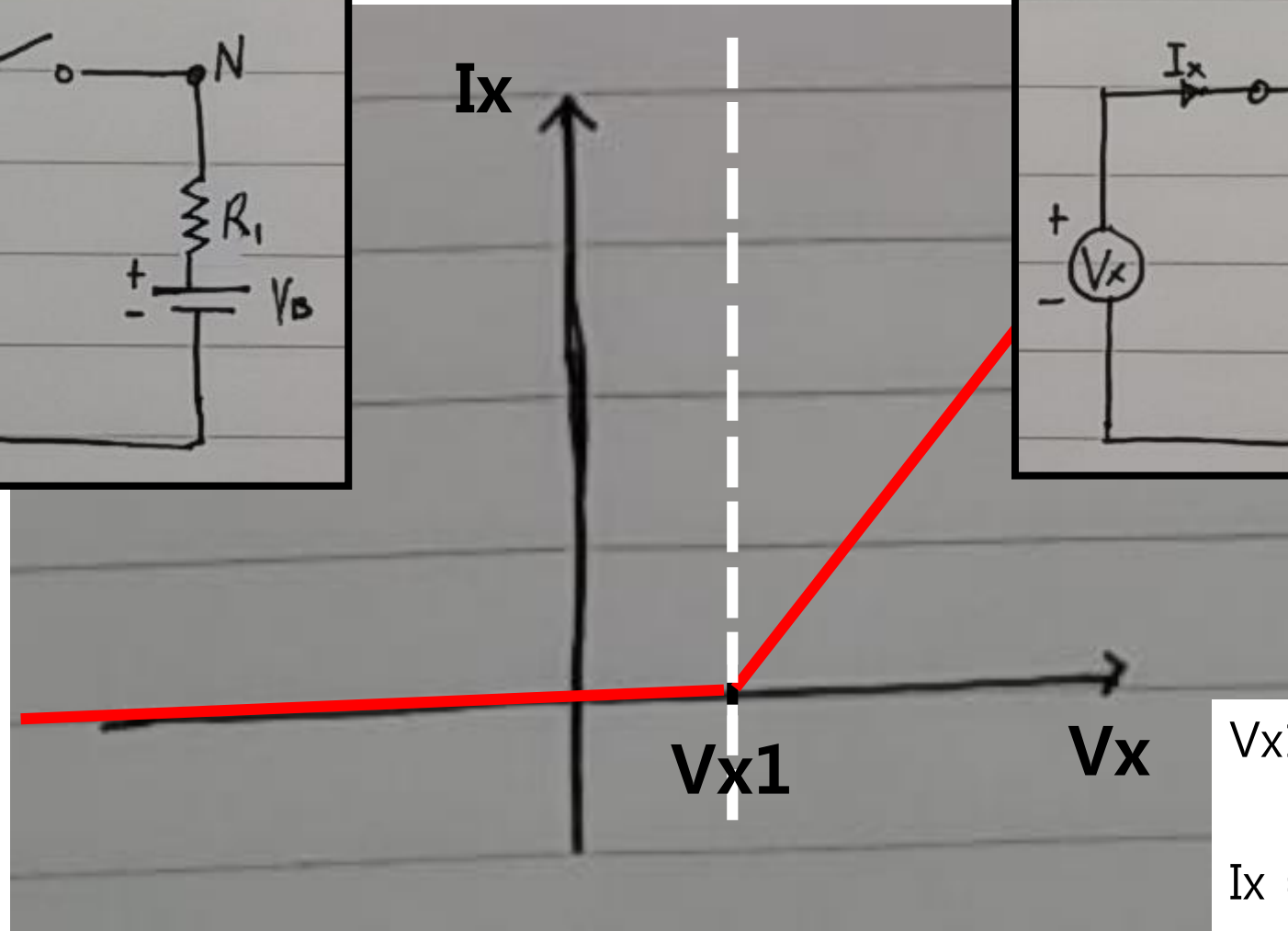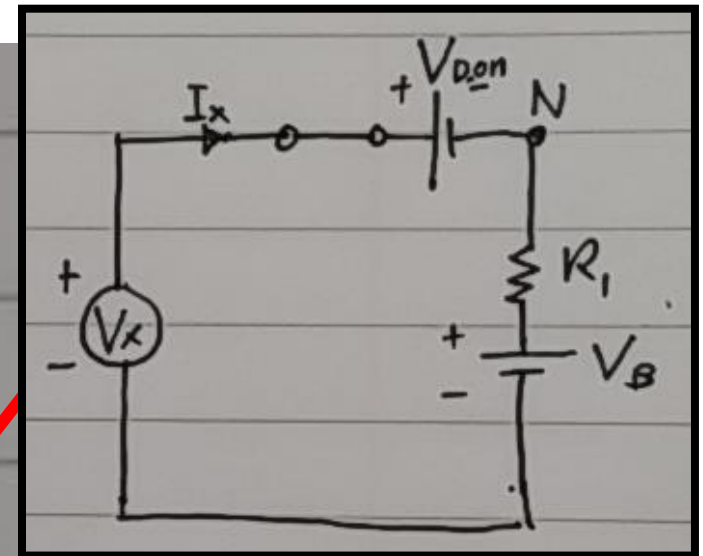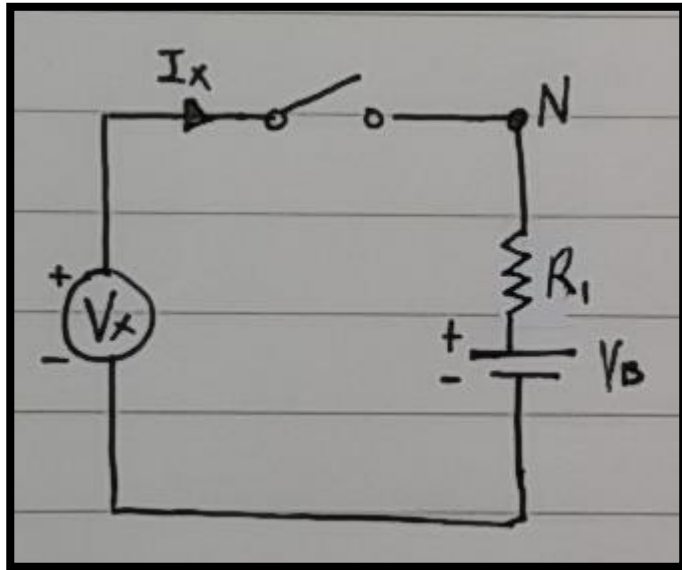

$$V_{x1} = I_x R_1 + V_{Don,+} + V_B$$

$$I_x = \frac{V_{x1} - (V_{Don,+} + V_B)}{R_1}$$

Example 2 : $V_N - V_x$ graph

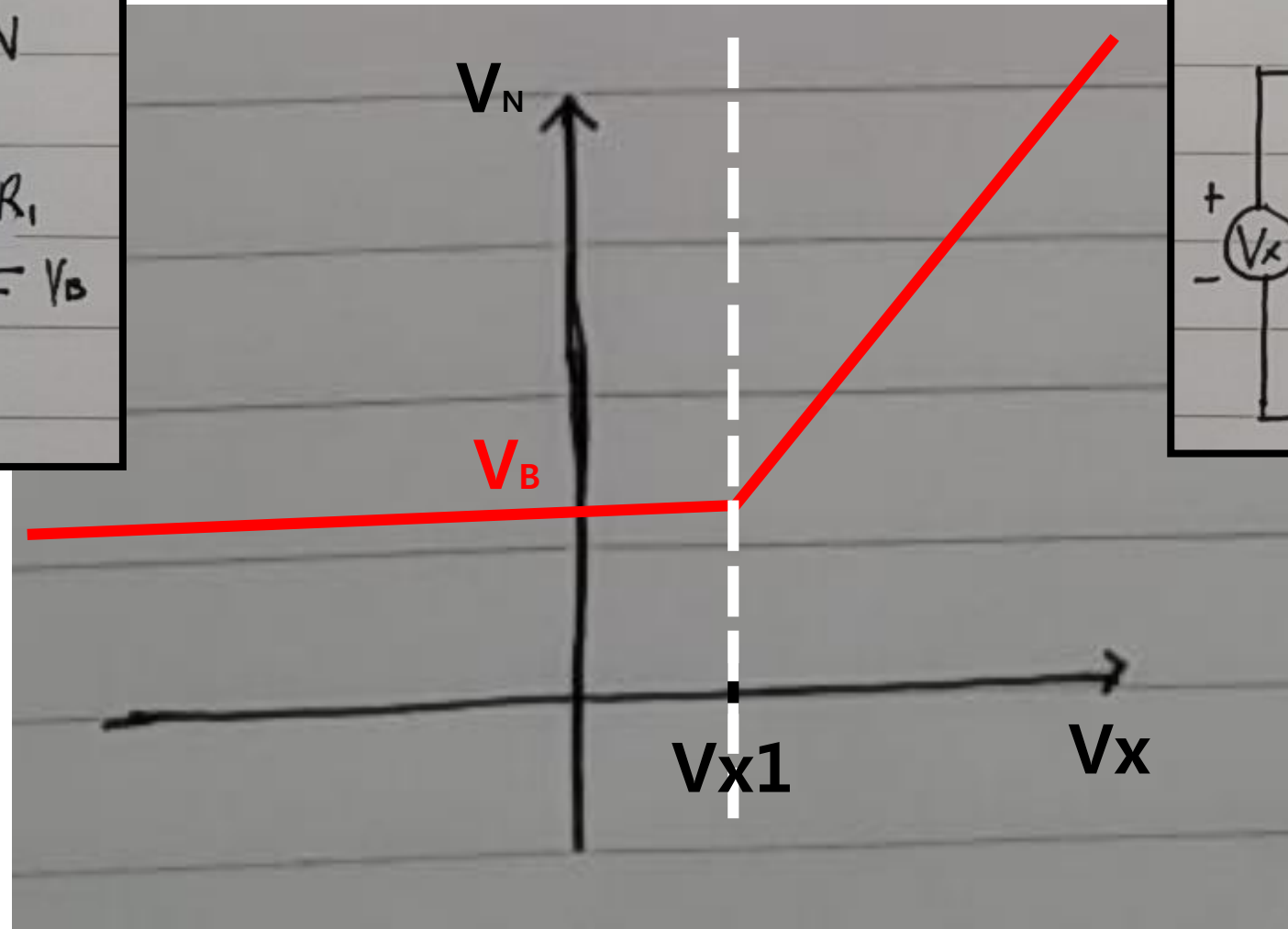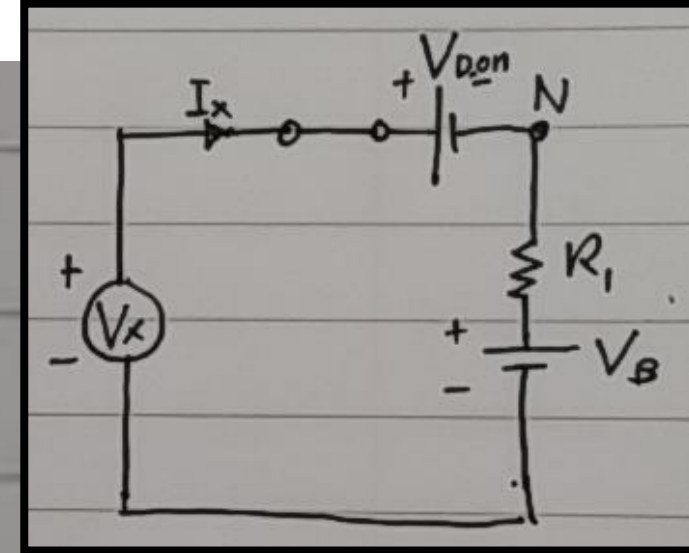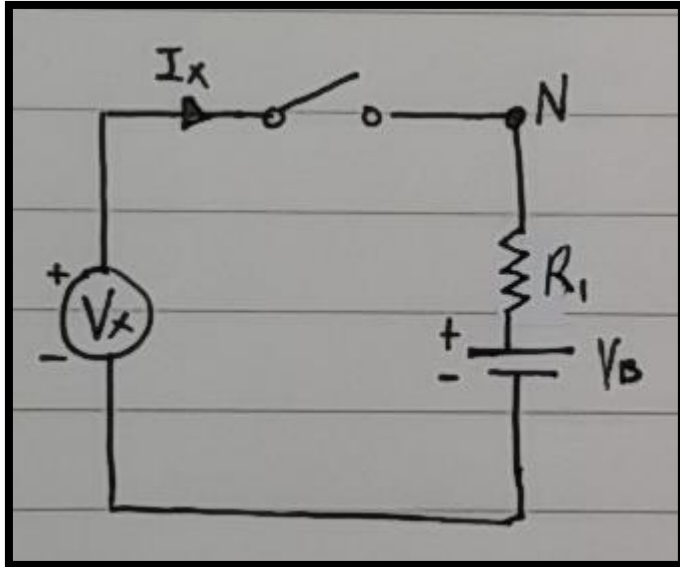

$$-V_x + V_{D,on} + V_N = 0$$

$$V_N = V_x - V_{D,on}$$

The End

Thank you