

Quiz for Lesson 19

Oct. 29, 2015


Electronic Circuits 1

Prof. Woo-Young Choi

Name: _____ Student ID: _____

Prob. 1

Determine the small-signal voltage gain for the following cascaded common-emitter amplifier. Assume both transistors are in the forward active region and include the Early effect. Express your answers in terms of $r_{\pi 1}$, $r_{\pi 2}$, g_{m1} , g_{m2} , r_{o1} , r_{o2} , R_{C1} , and R_{C2} .

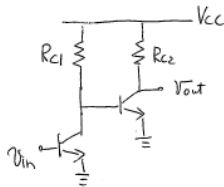

Prob. 2

The transconductance of a BJT in the common-emitter configuration is influenced by temperature, process, and input voltage level changes. Determine whether each of the following changes increases or decreases the transconductance: a) Temperature increase, b) Larger doping concentrations in the base and the emitter than the target values, c) Increase in the input voltage level.

Prob. 3

Determine the small-signal voltage gain of the following common-emitter with emitter degeneration. Assume the transistor is in the forward active region and there is no Early effect.

