

## Quiz for Lesson 20 and 21

Nov. 2, 2015


Electronic Circuits 1

Prof. Woo-Young Choi

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_

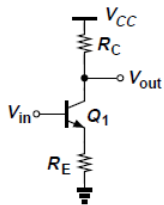
### Prob. 1

Determine the input resistance of the following common-emitter amplifier with emitter degeneration. Assume the transistor is in the forward active region and there is no Early effect.


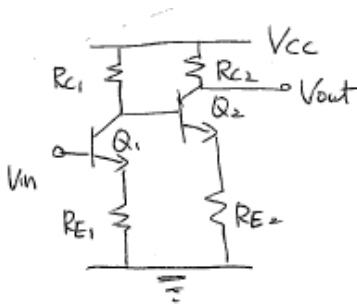
### Prob. 2

Determine the small-signal voltage gain for the following cascaded amplifier. Assume the transistors are in the forward active region and the Early effect can be ignored.




### Prob. 3

Determine the output resistance of the common-emitter amplifier with emitter degeneration shown in Prob. 1. Assume the transistor is in the forward active region. Include  $r_o$  due to the Early effect.

**Prob. 4**

Determine the value of  $R_E$  so that the collector bias current (DC value of  $I_C$  without any input) is 1mA in the circuit shown below at room temperature.  $Q_1$  has  $I_S$  of  $1 \times 10^{-16} \text{A}$  and  $\beta = 100$ ,  $V_{CC} = 1.5 \text{V}$ ,  $R_1 = 6 \text{k}\Omega$  and  $R_2 = 9 \text{k}\Omega$ . Assume  $Q_1$  is in the forward active region and the base current can be ignored for this problem. Do not consider the the Early effect.

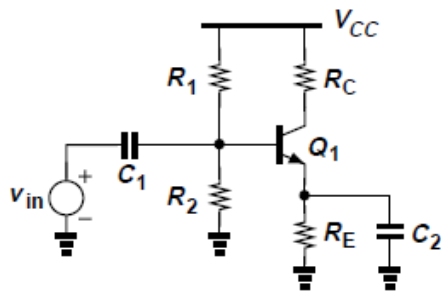**Prob. 5**

Explain why the common-emitter with emitter degeneration is less sensitive to the supply voltage fluctuation than the common-emitter is.

**Prob. 6**

$V_{in}(t)$  is given as  $V_o \sin(2\pi ft)$  where  $f$  is large enough so that impedances for  $C_1$  and  $C_2$  can be approximated as zero. What is the small-signal output voltage measured between the collector and the ground for the circuit shown in Prob. 4? Use the conditions given in Prob. 4 along with  $R_C = 500\Omega$ .