

Quiz for Lesson 27

Nov. 19, 2015

Electronic Circuits 1

Prof. Woo-Young Choi

Name: _____

Student ID: _____

Prob. 1

Plot I_D vs V_{DS} in an NMOS for several different values of V_{GS} 's when $V_{GS} > V_{TH}$. Include the channel length modulation effect. Explain the meaning of λ and g_m in your plot.

Prob. 2

Values for following parameters of an NMOS in saturation are known: V_{GS} , V_{DS} , μ_n , C_{ox} , W/L , V_{TH} . How should a circuit designer change above parameter values in order to increase the transconductance by factor of two? Give two different methods. Do not consider the channel length modulation effect.

Prob. 3

Determine the numerical value of the transconductance of M_1 in the following circuit. Use $\mu_n C_{ox} = 100 \mu A/V^2$ and $V_{TH} = 0.4V$. Do not consider the channel length modulation effect.

