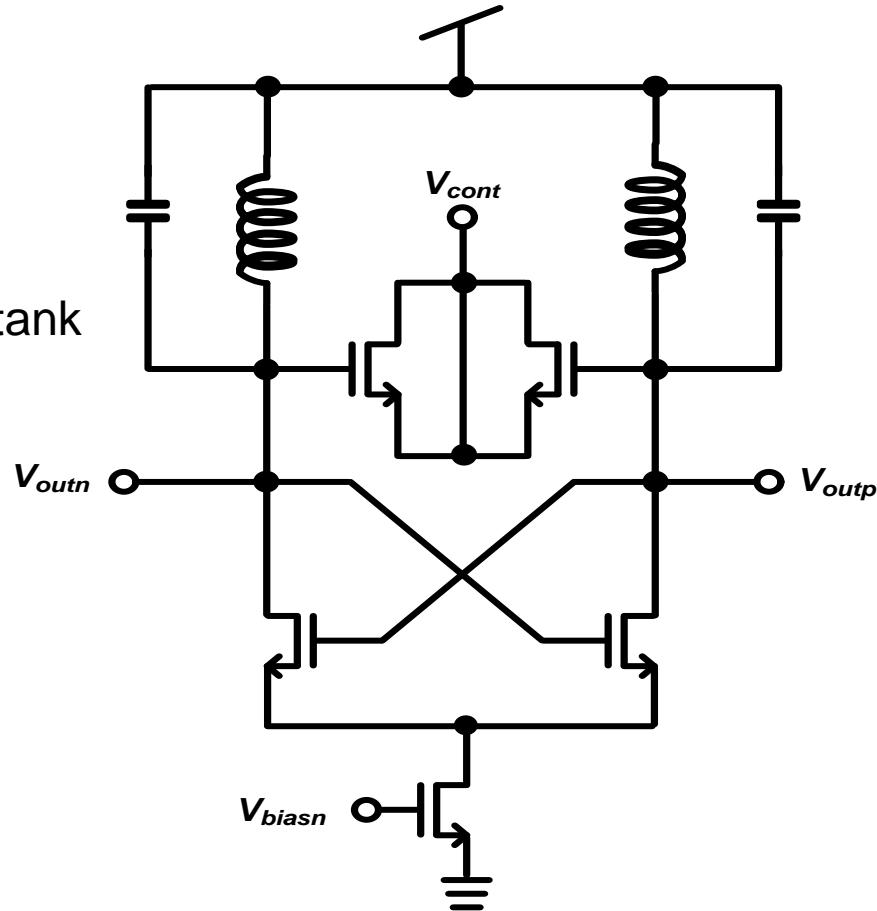


LC VCO Structure

LV VCO Structure



- LC Tank
 - Spiral inductor (symmetric type)
 - Ideal cap
- Cross coupled circuit
 - Negative resistance
 - To compensate for the loss of the tank
- Source MOSFET
- Varactor
 - Accumulation varactor
- OSC frequency

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$




Varactor

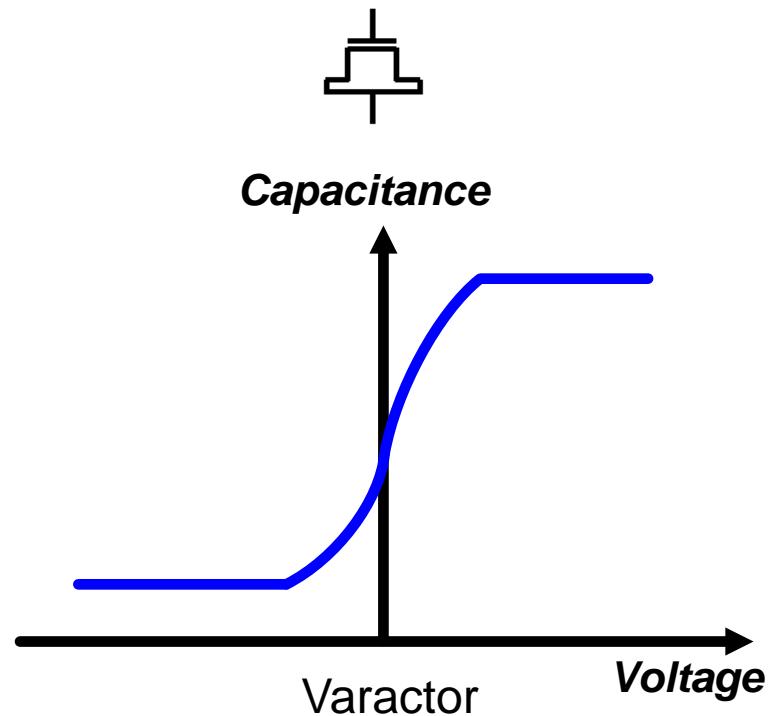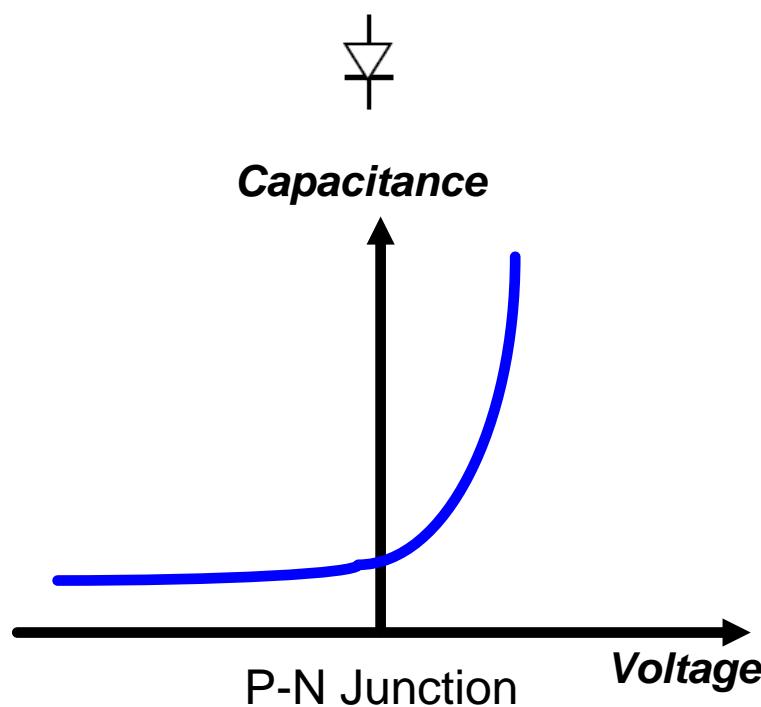- Varactor type
 - P-N Junction
 - MOS Varactor
 - Inversion mode
 - Accumulation mode





Accumulation Mode Varactor

- On (Accumulated channel)

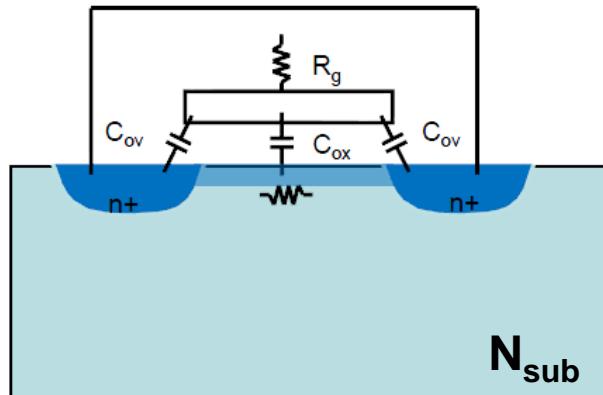


- OFF(Depleted)

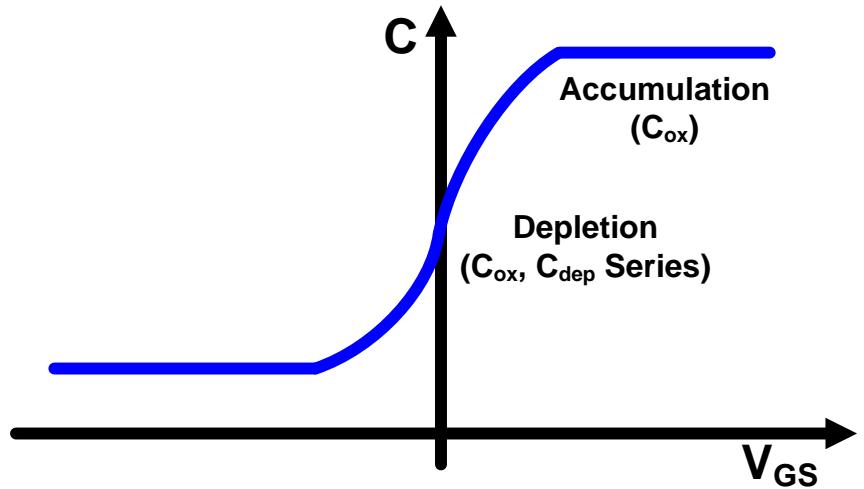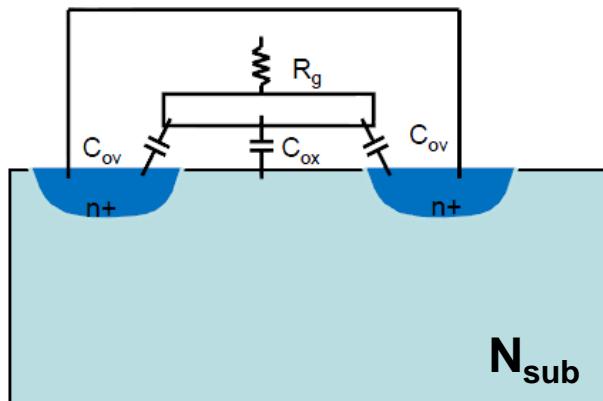

TSMC Varactor


Varactor selection

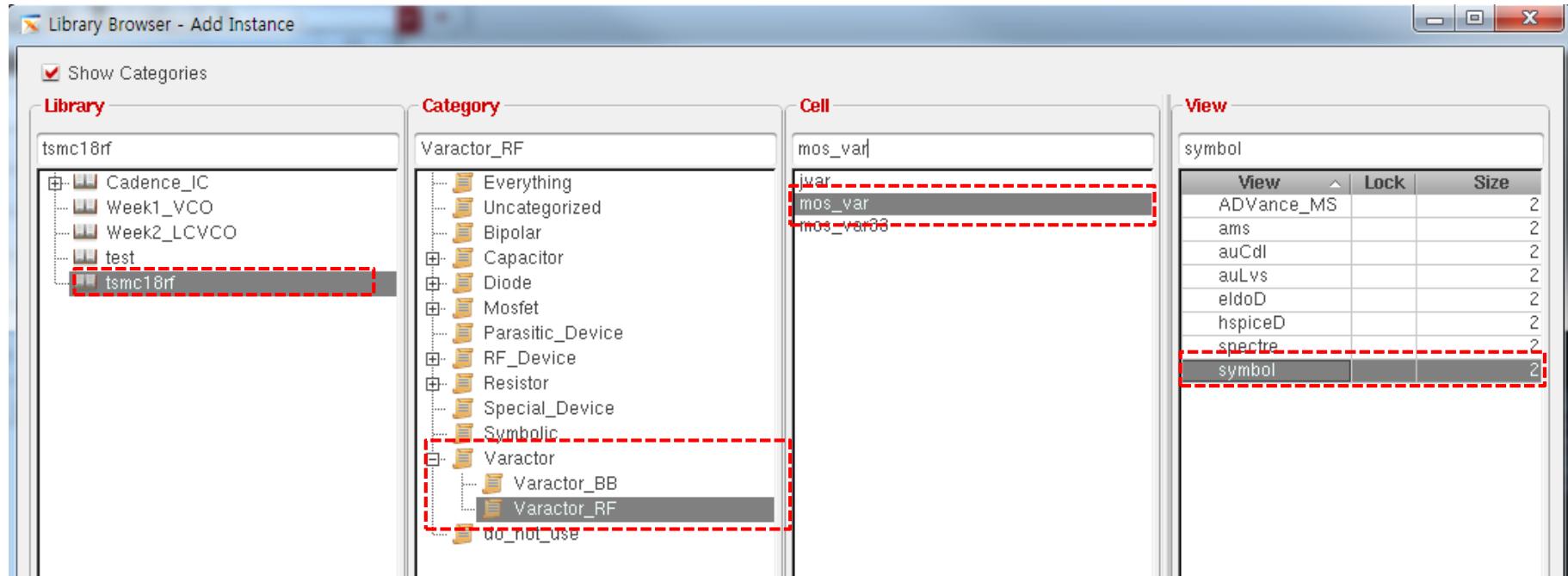- Tsmc18rf → Varactor → Varactor_RF → mos_var → symbol



Varactor Setting

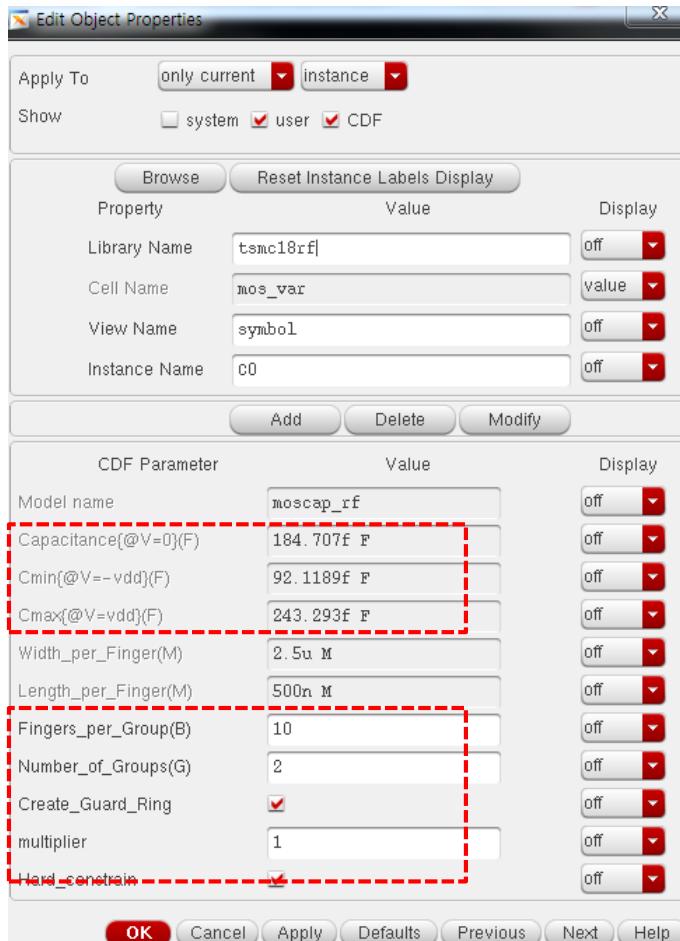- Setting of Fingers_per_Group, Number_of_Group and multiplier
- Extract min and max capacitance



- Fingers_per_Group(B) : 10

- Number_of_Groups (G) : 2

- Multiplier : 1


→ Min Capacitance : 92f

→ Max Capacitance : 243fF



→ Δ Capacitance : 151fF

Varactor Modeling

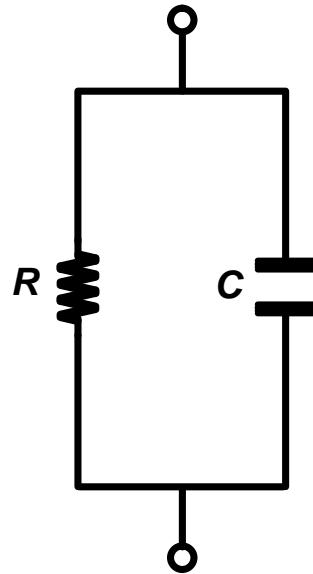- An equivalent circuit model of varactor
 - Parallel connection of resistance and capacitance
 - Analyze capacitance into using Y-parameter



< Equivalent circuit of varactor >

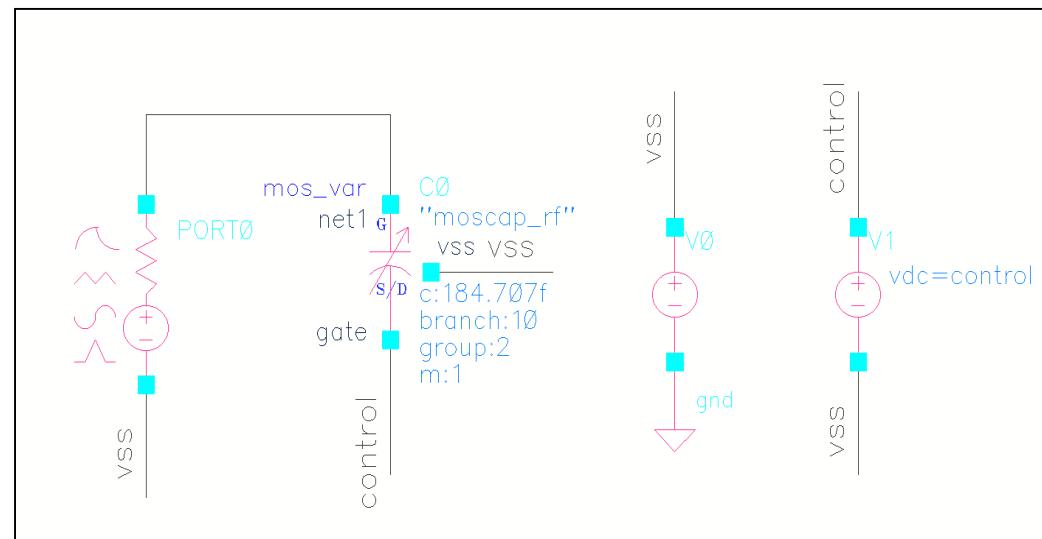
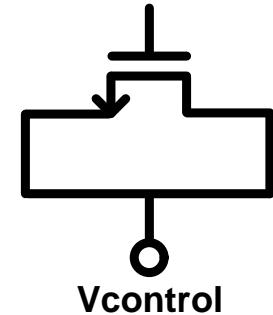


< Test schematic >

S - Parameter

Simulation condition setting

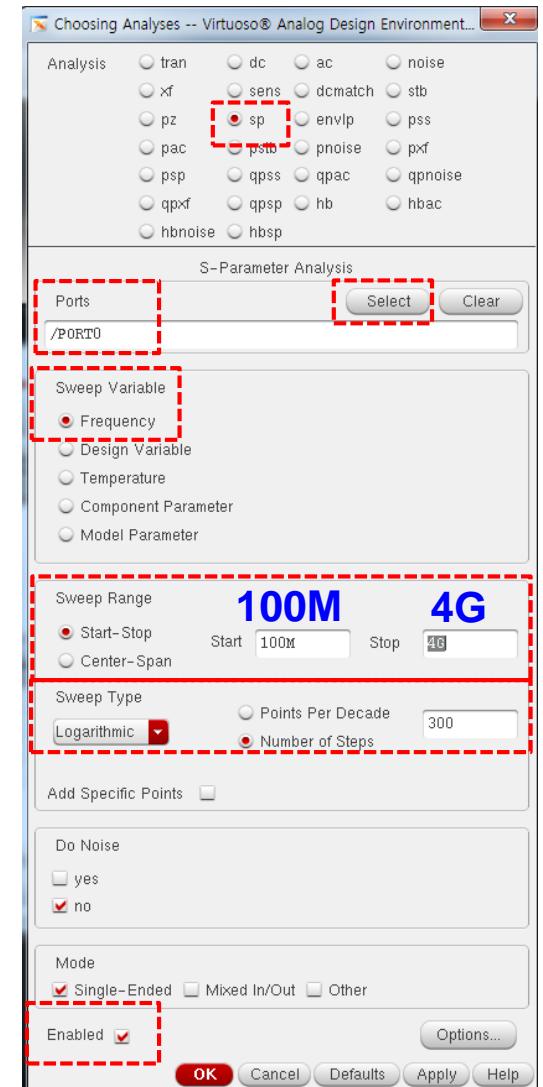
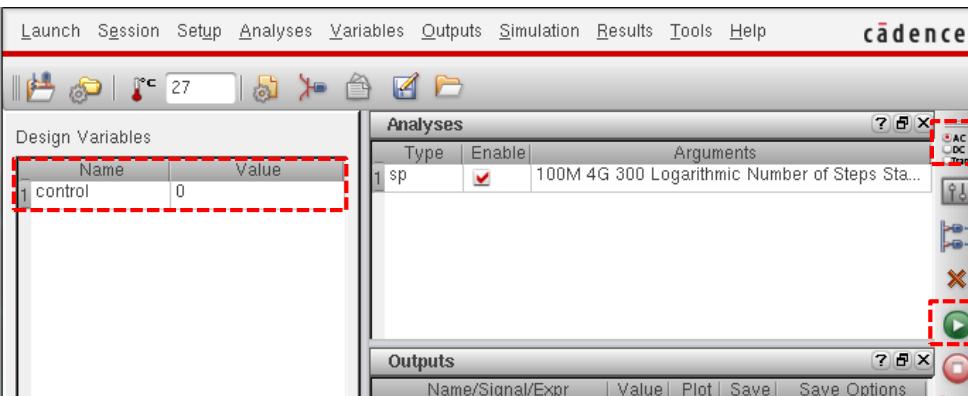
- Control voltage : 0V
- Analysis : sp (S-Parameter Analysis)
- Ports : Port0 (schematic node choice)
- Sweep Variable : Frequency
- Sweep Range : 100M ~ 4G
- Sweep Type : Logarithmic
- Number of Steps : 300
- Enabled check → OK → Netlist and Run



Y- Parameter

Simulation condition setting

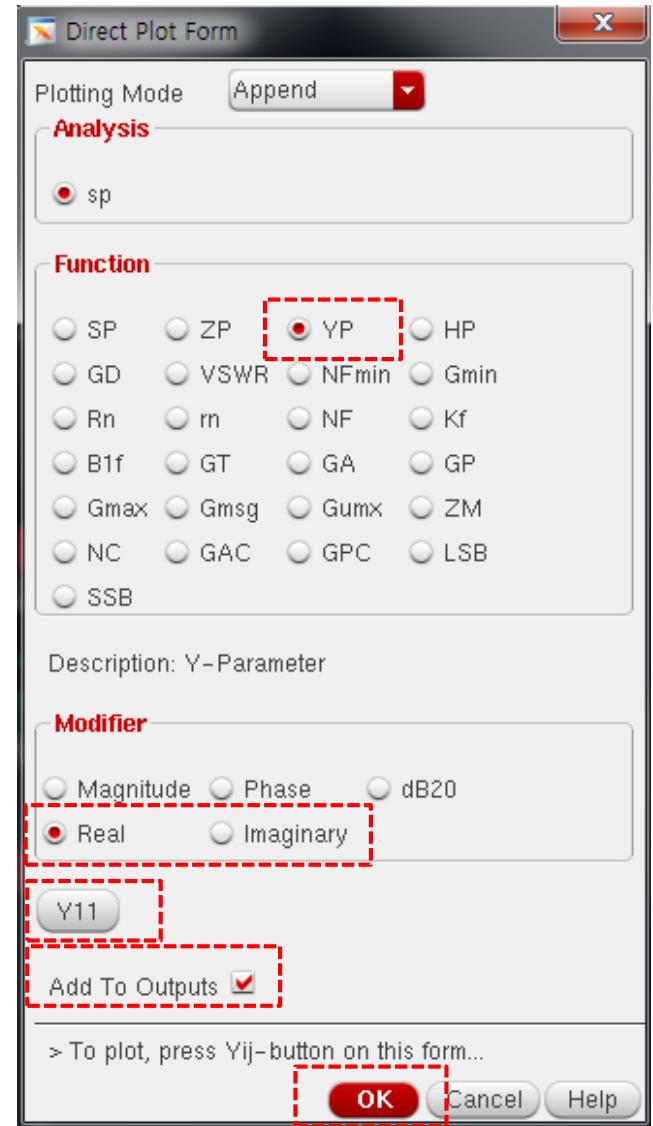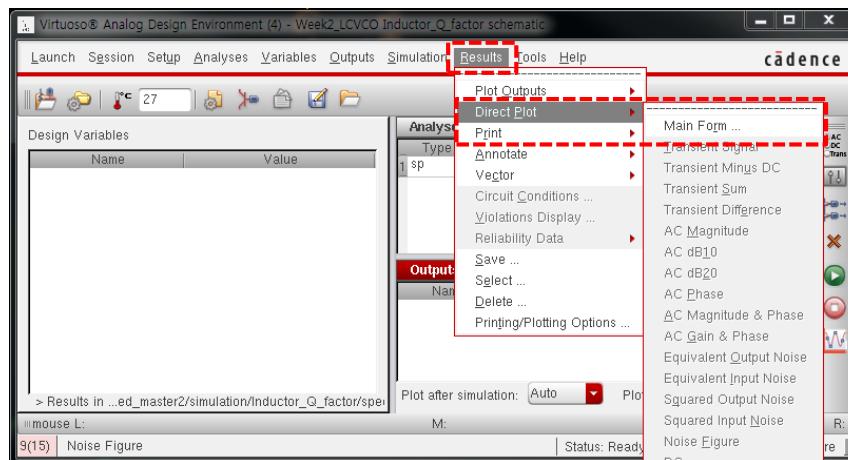
- Results → Direct Plot → Main Form
- Function : YP
- Add To Outputs choice
- Modifier : Real → Y11 and Imaginary → Y11
- OK



Y- Parameter

- $Y = \frac{1}{R} + j\omega C$

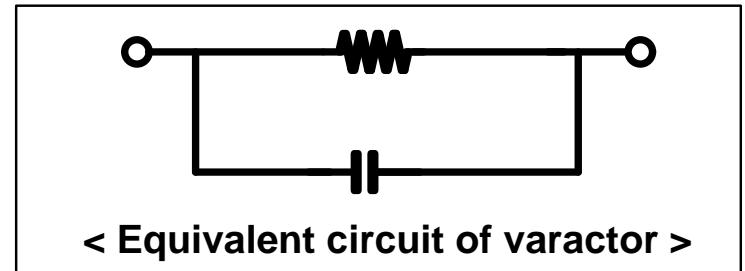
- Resistance = $\frac{1}{Real[Y_{11}]}$
- Capacitance = $\frac{Imaginary [Y_{11}]}{\omega}$



Capacitance

Simulation condition setting

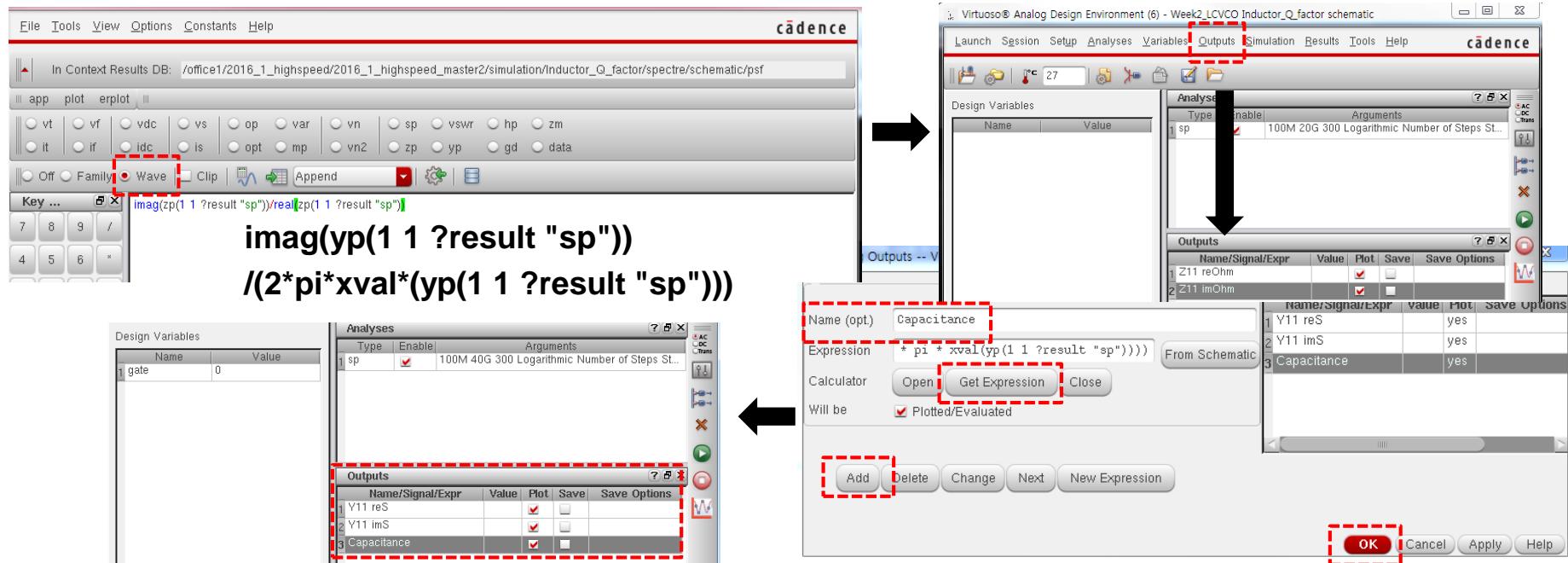
- $C = \frac{\omega C}{\omega} = \frac{Imag[Y11]}{\omega}$
- Calculator (Visualization & Analysis XL)
- Wave choice → `imag(yp(1 1 ?result "sp")) / (2*pi*xval(yp(1 1 ?result "sp")))`
- Outputs → Setup → Name (Capacitance) → Get Expression → Add → OK



Capacitance (Control = 0V)

Capacitance simulation

- Capacitance : 184fF @ 1.50GHz

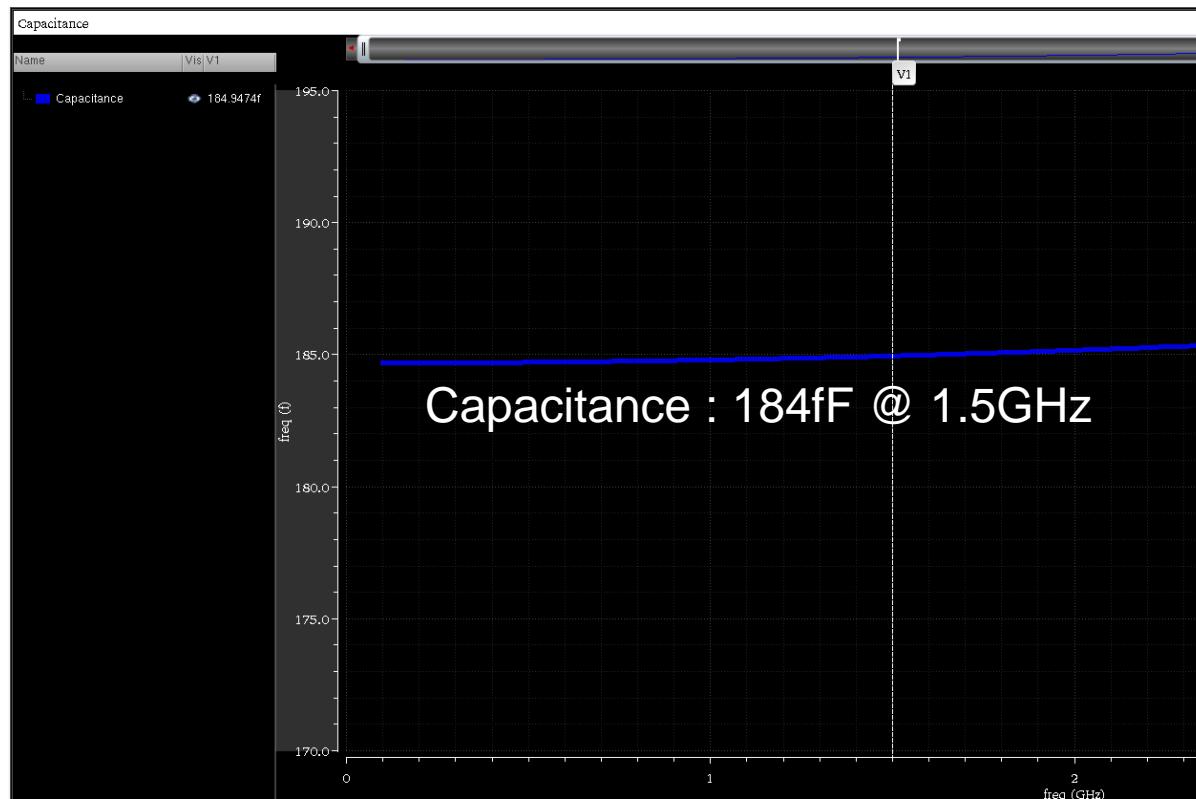


Capacitance Variation

- Control voltage sweep
 - Tools → Parametric Analysis
 - Control voltage : -1.8V ~ 1.8V (Linear steps :0.3V)




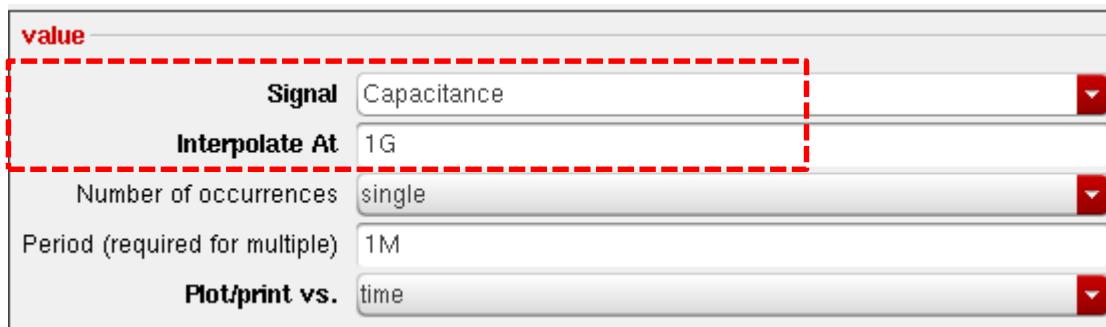- Calculator → Family → value → 파형 선택 (Capacitance) → Plot
 - Interpolate At : 1G




Capacitance Variation

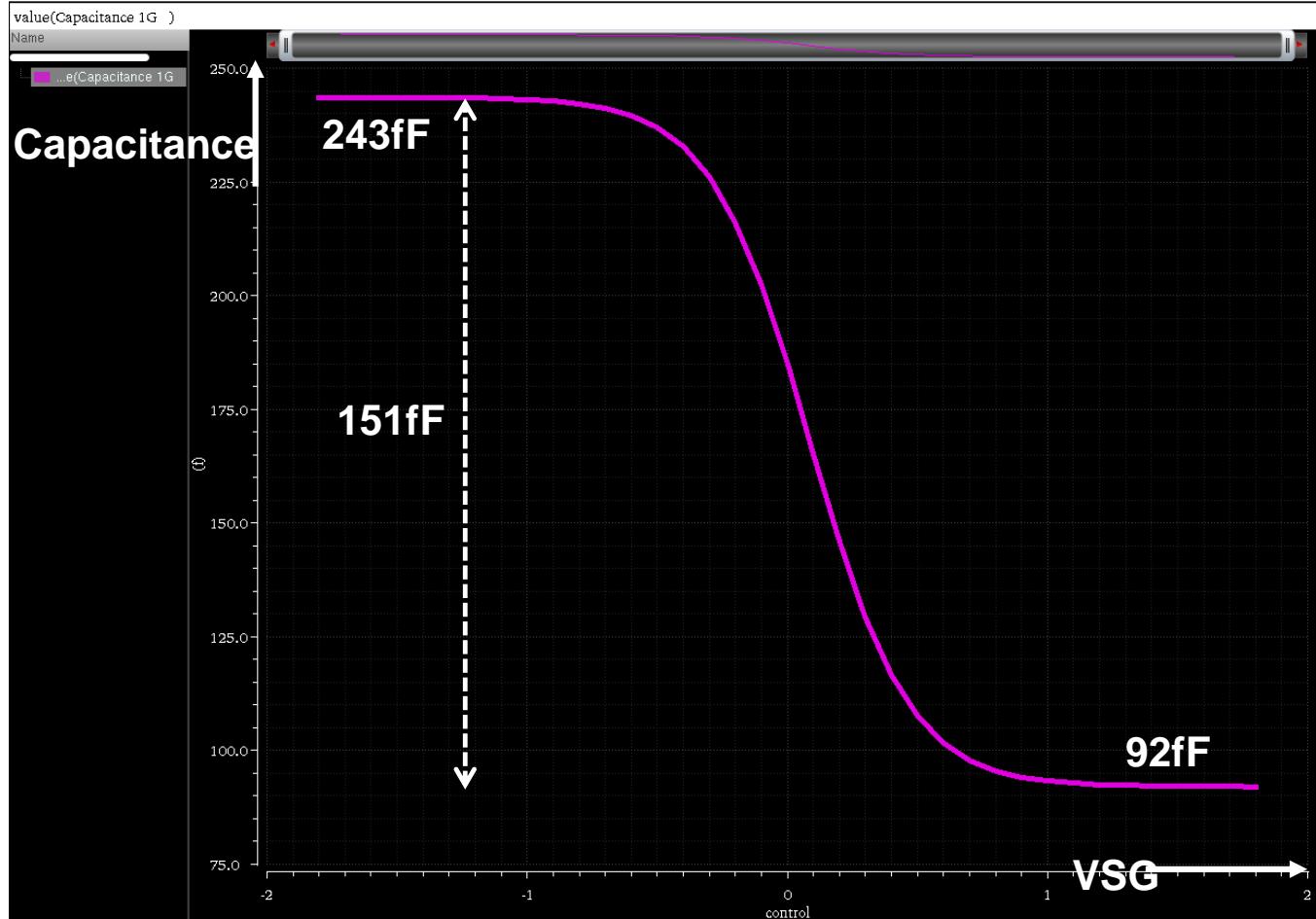- V_{SG} vs Capacitance
 - Multiplier : 1




Capacitance Variation

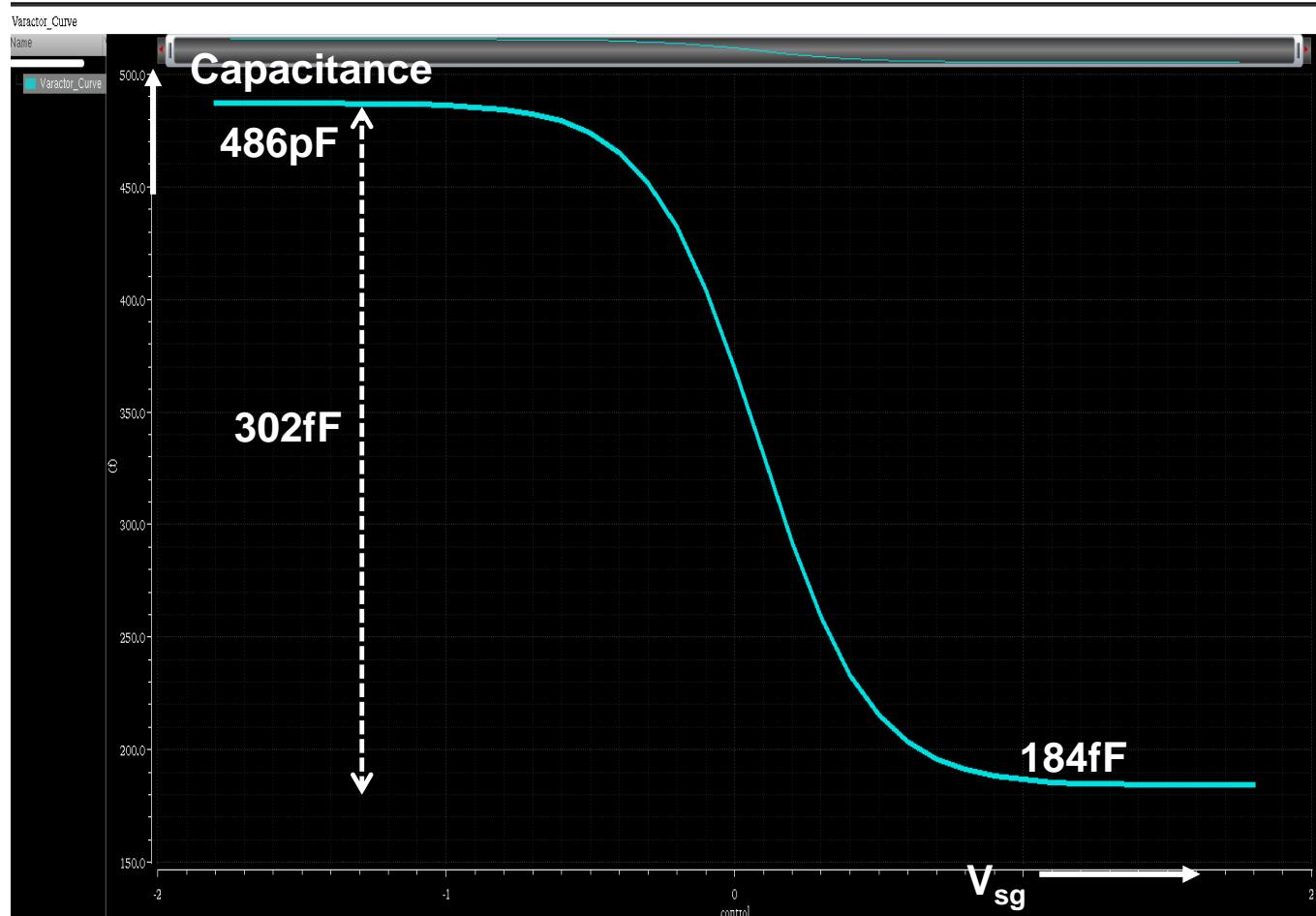- V_{GS} vs Capacitance
 - Multiplier : 2





Varactor Operation

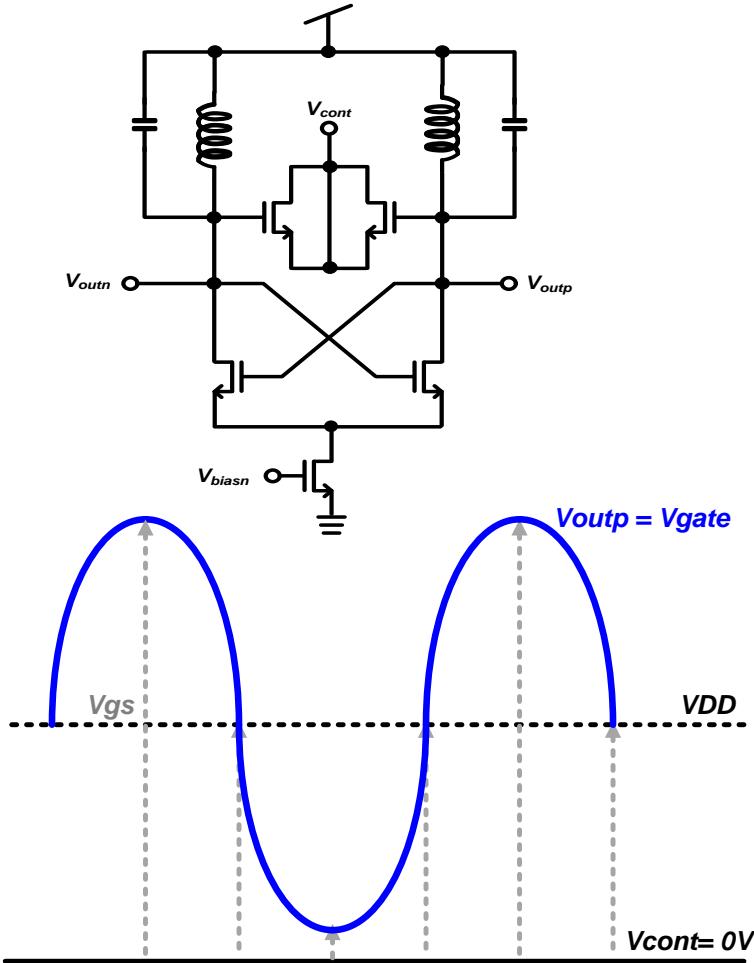- Change average capacitance from control voltage.




VCO Output Node

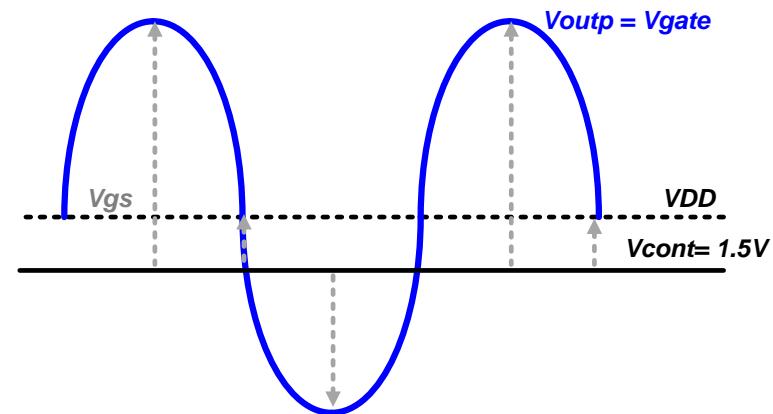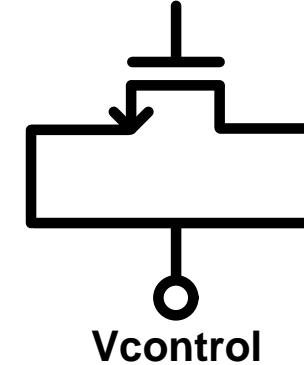

LC VCO Schematic

Simulation LC VCO schematic


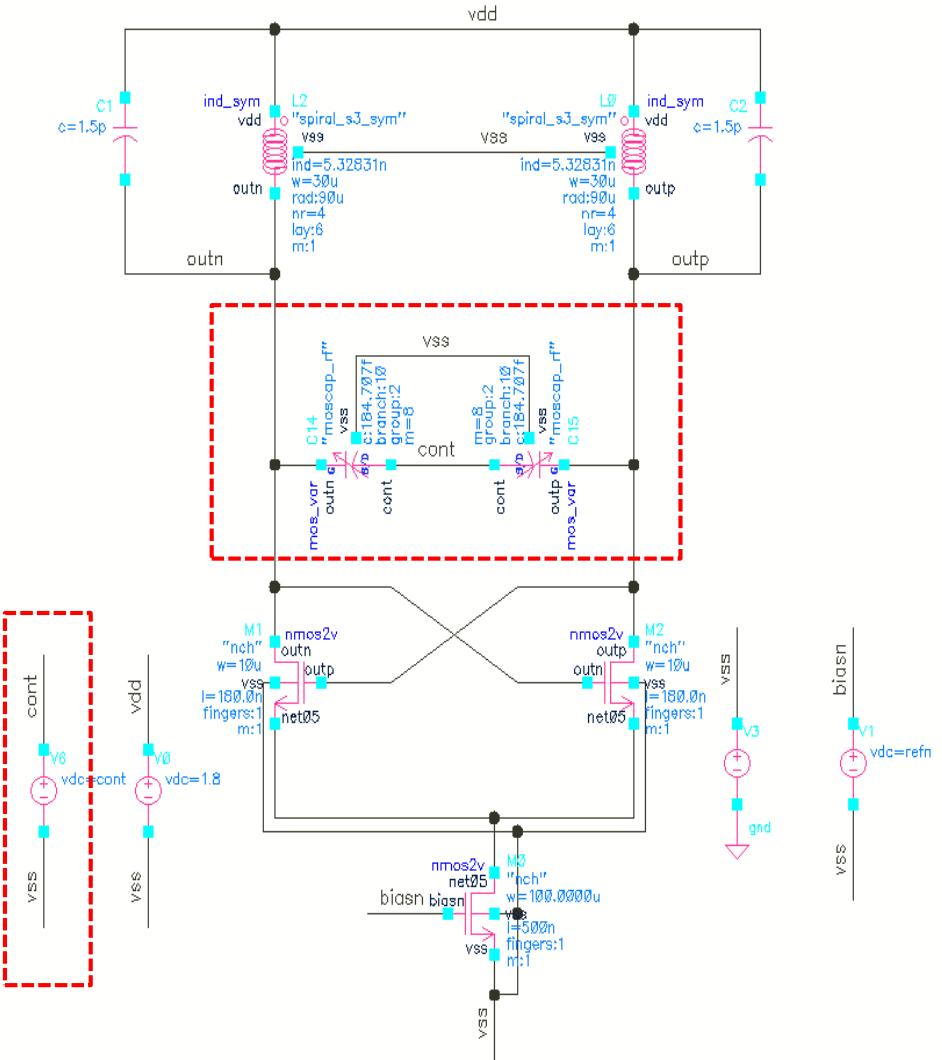
- Inductor : 5.42nH
- Capacitor : 1.5pF
- Input NMOS
 - Length : 180n
 - Total Width : 10u (finger :1)
- Source NMOS
 - Length : 500n
 - Total Width : 100u (finger :1)
- Varactor
 - Fingers_per_Group(B) : 10
 - Number_of_Group(G) : 2
 - Multiplier : 8
- vdd : 1.8V
- biasn : 0.8V
- cont : 변수 지정 (cont)



OSC Frequency ($V_{cont} = 0V$)

Control Voltage 0V

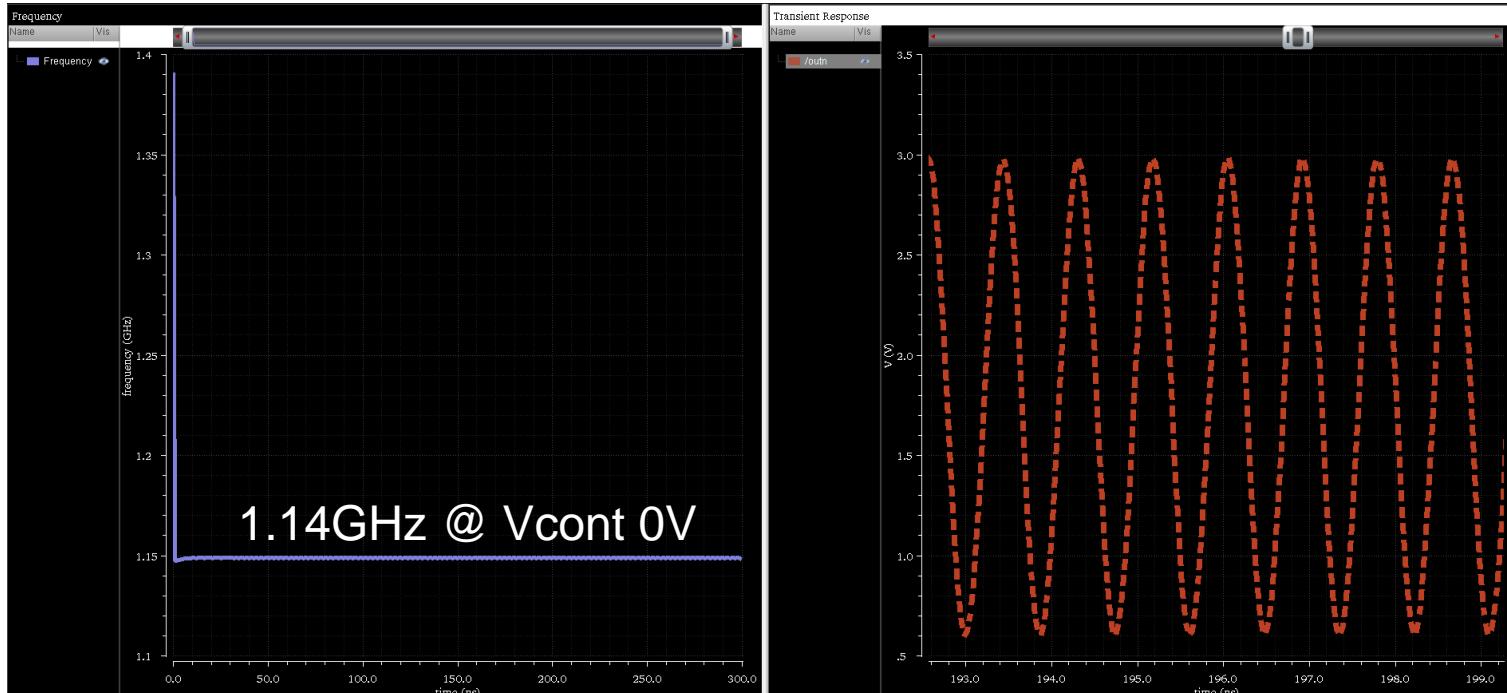
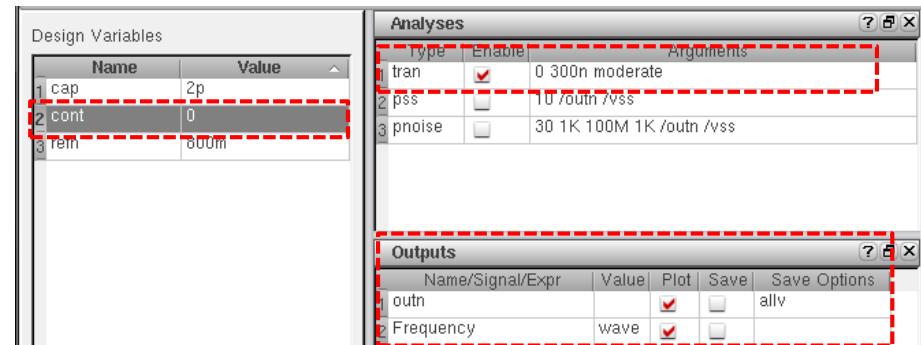
- OSC frequency : 1.14GHz
- Transient simulation (300ns)
- Output 파형 및 Frequency 측정



OSC Frequency (Vcont = 1.8V)


Control Voltage 1.8V

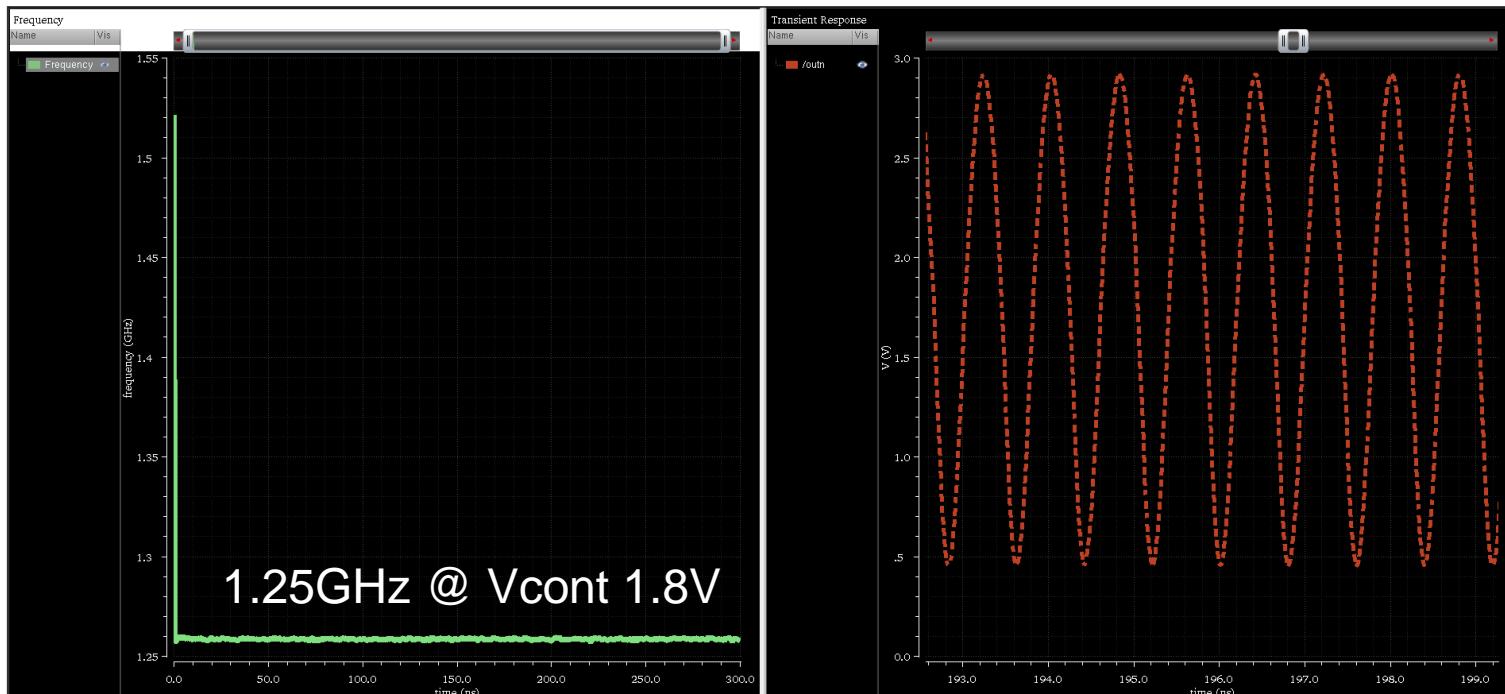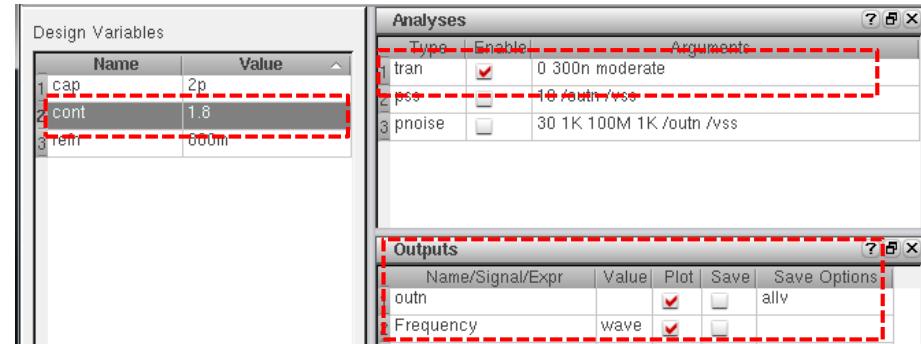- OSC frequency : 1.25GHz
- Transient simulation (300ns)
- Output 파형 및 Frequency 측정




Frequency Tuning Range

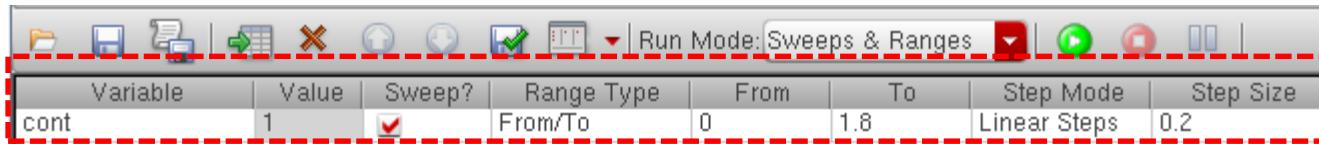- Control voltage sweep
 - Tools → Parametric Analysis
 - Control voltage : 0 ~ 1.8V (Linear steps :0.2V)




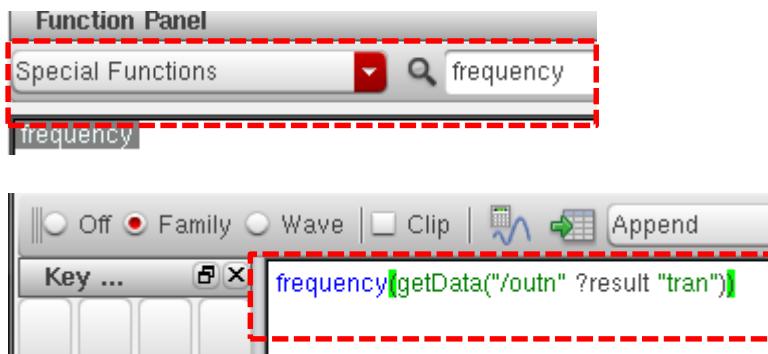- Calculator → Family → 파형 선택 (Output) → Function (frequency) → Plot




Frequency Tuning Range

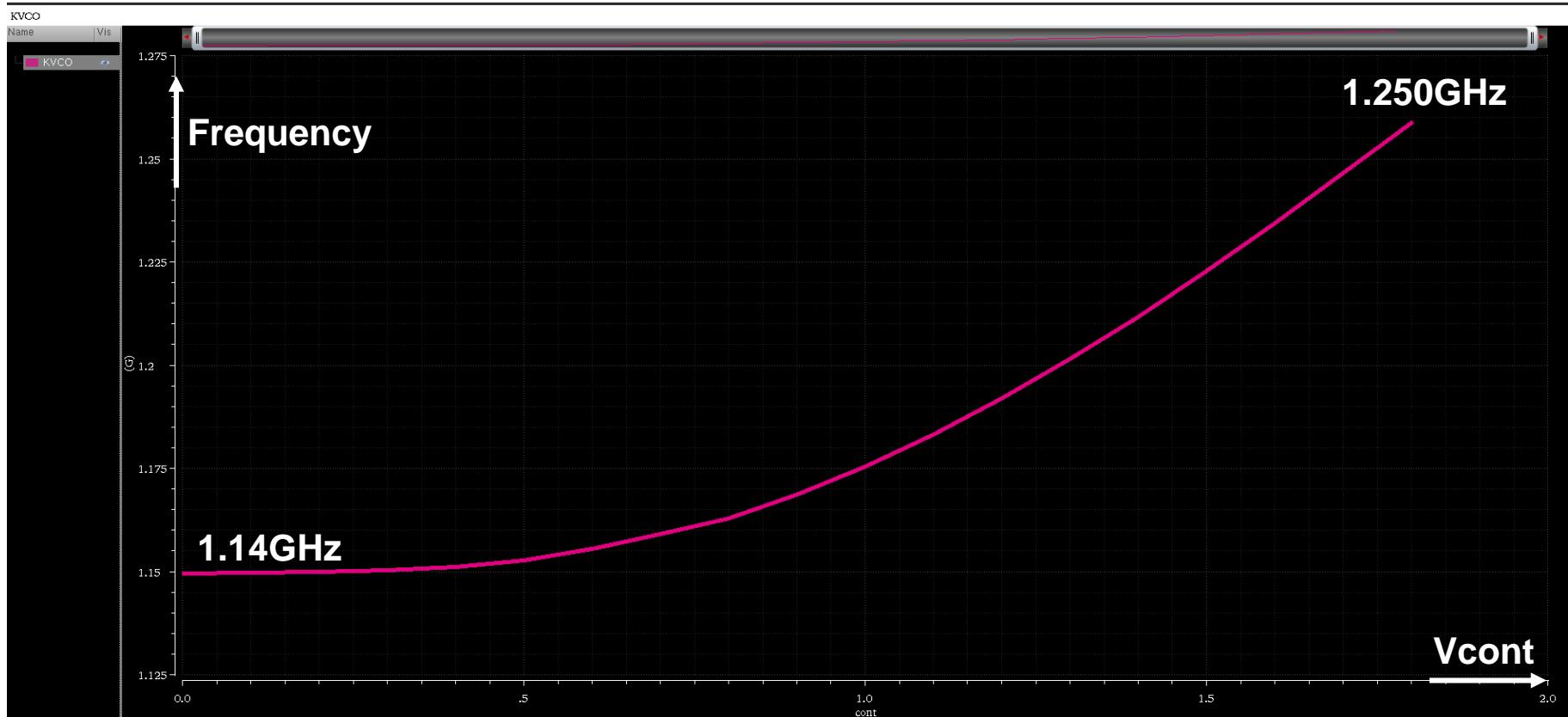- Varactor control sweep
- Varactor control voltage range : 0V ~ 1.8V
- Frequency tuning range : 110MHz




Frequency Tuning Range

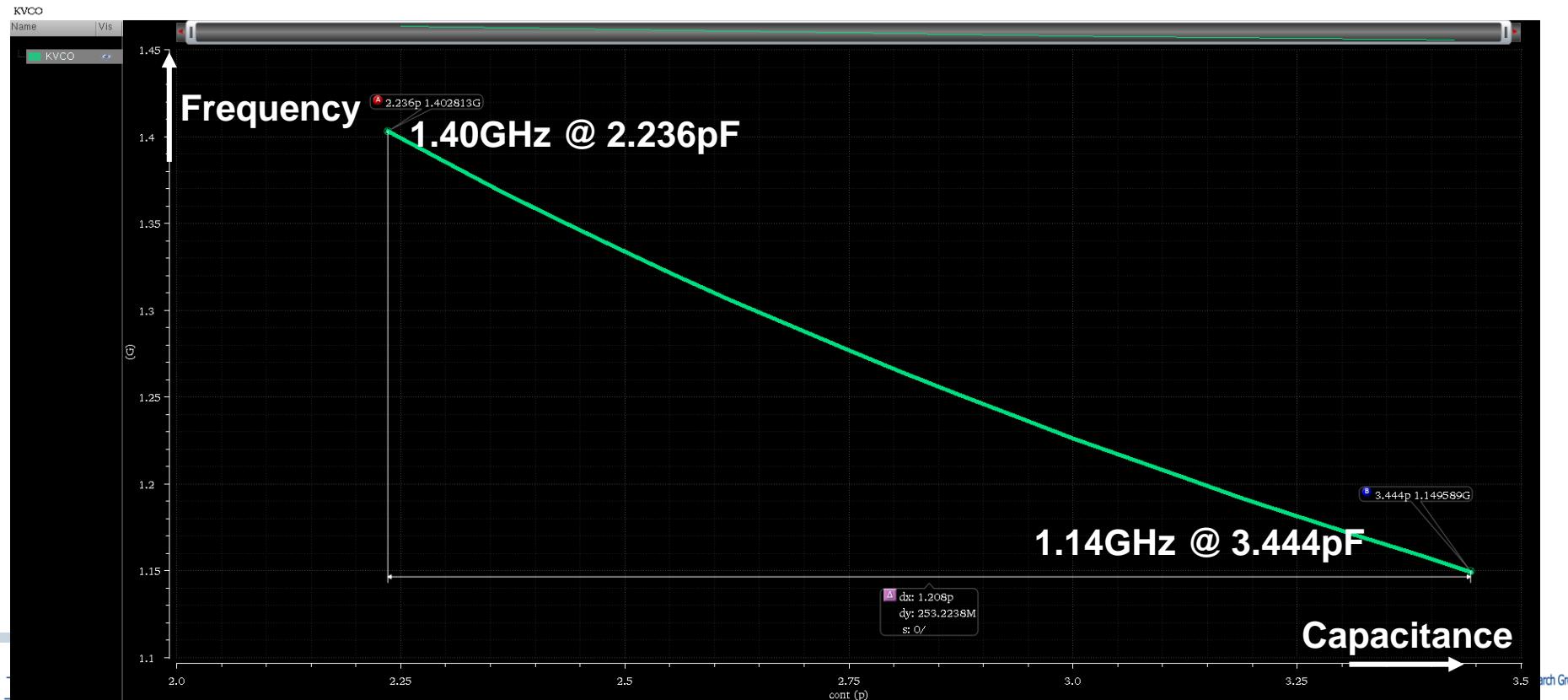- Capacitance value sweep
- Varactor capacitance
 - Control voltage 0V : 1944fF (Total capacitance 3444fF)
 - Control voltage 1.8V : 736fF (Total capacitance 2236fF)
- frequency tuning range : 260MHz




Frequency Tuning Range

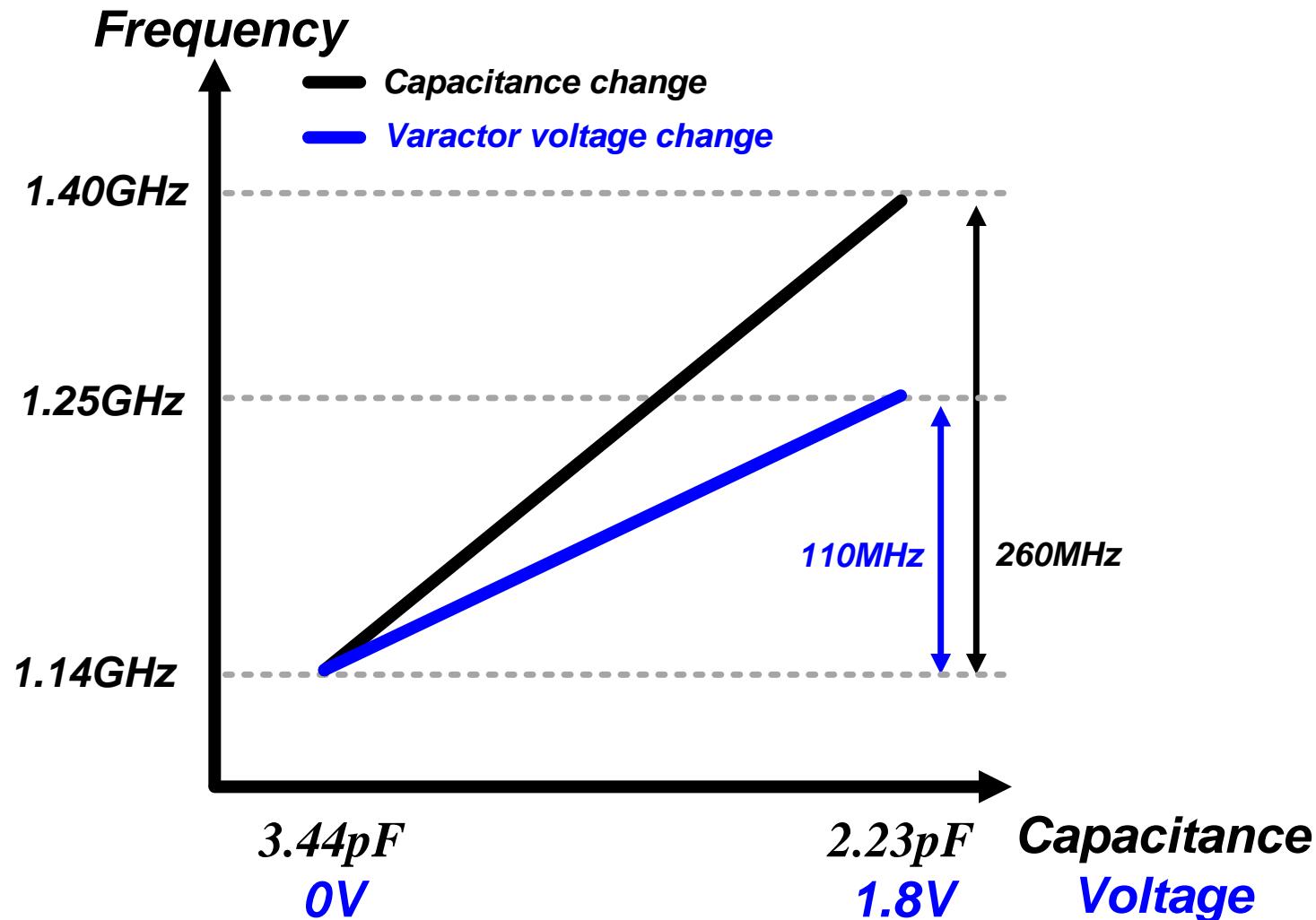

Phase Noise (cont : 1V)

Phase Noise



- 1.17GHz, -131dBc @ 1MHz

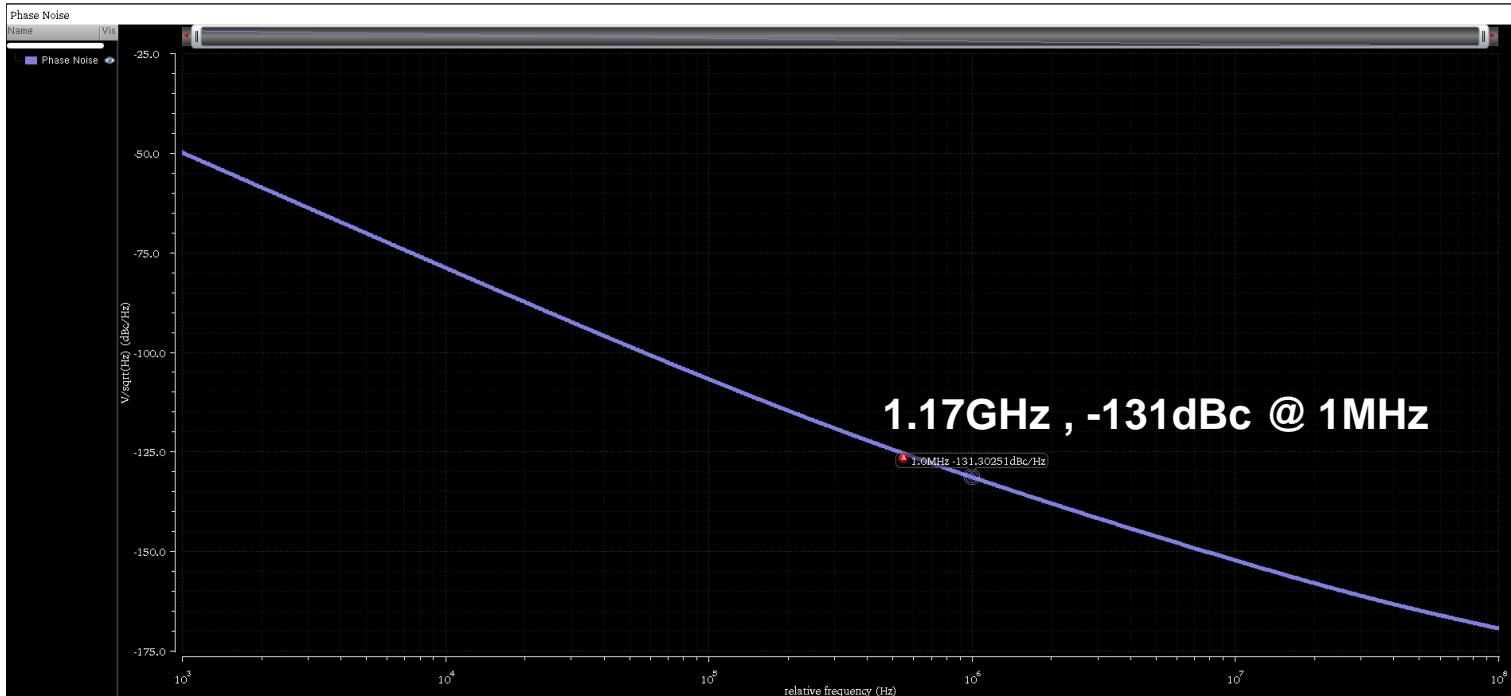

VCO Comparison #1

Phase noise

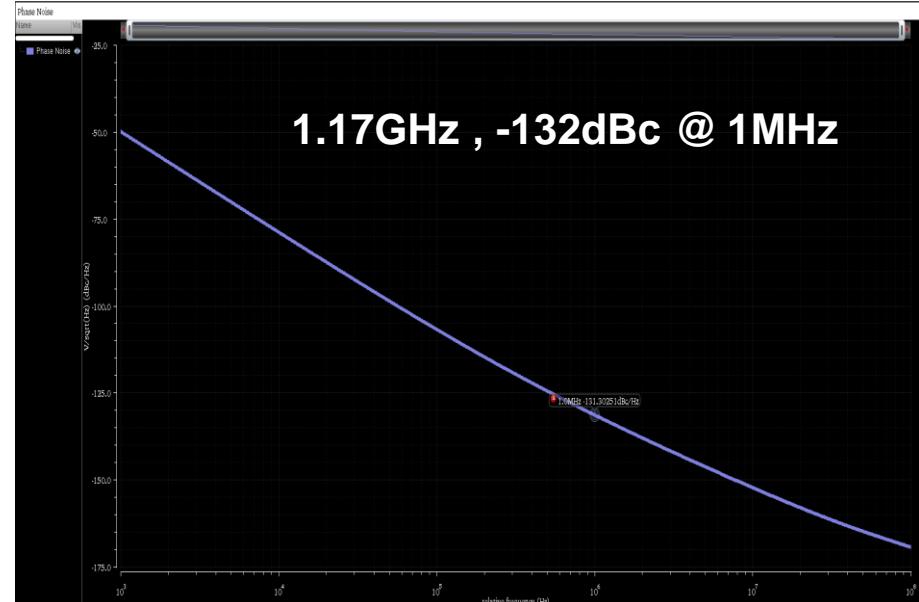
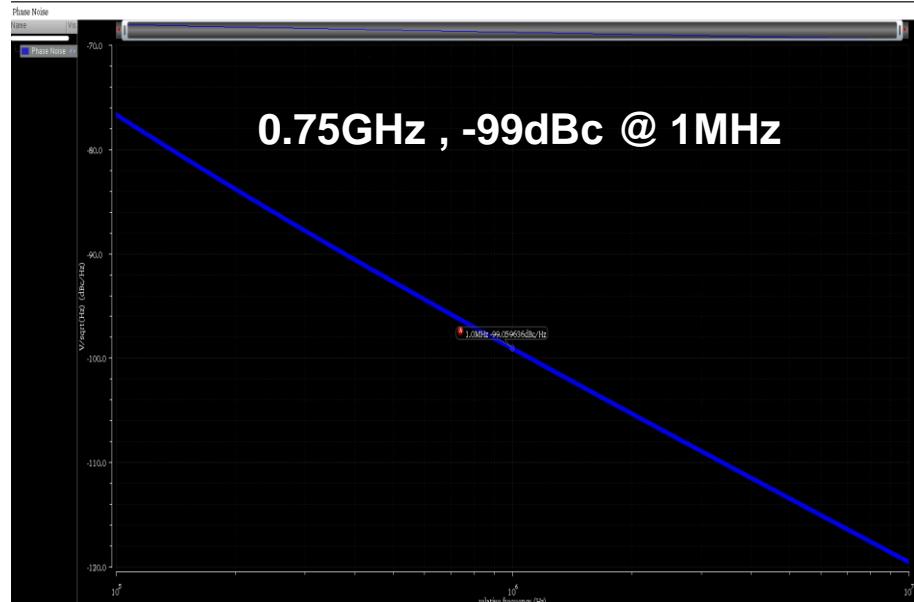
- Ring VCO : -99dBc @ 0.75GHz 1MHz offset
- LC VCO : -132dBc @ 1.35GHz 1MHz offset
- **LC VCO is better for phase noise.**



VCO Comparison #2

- Frequency tuning range

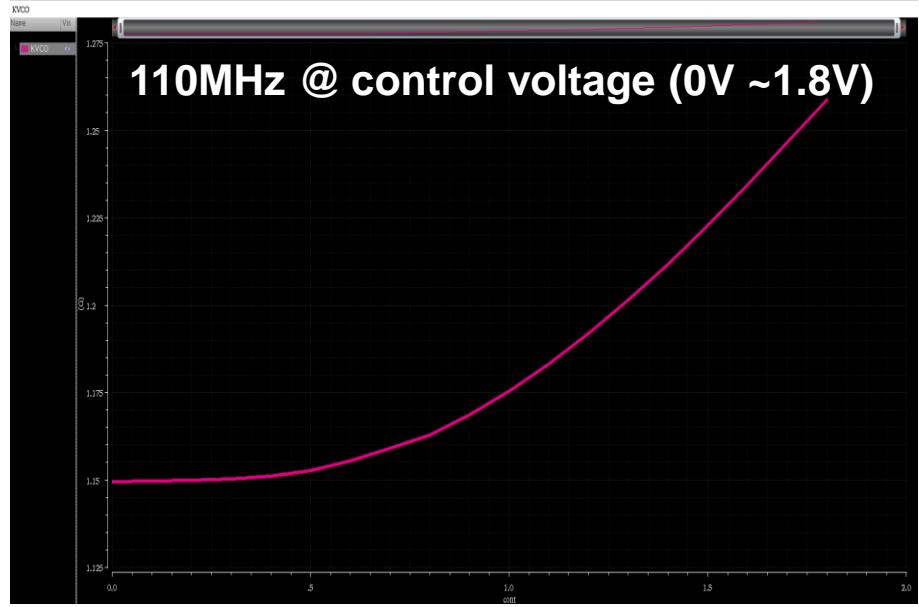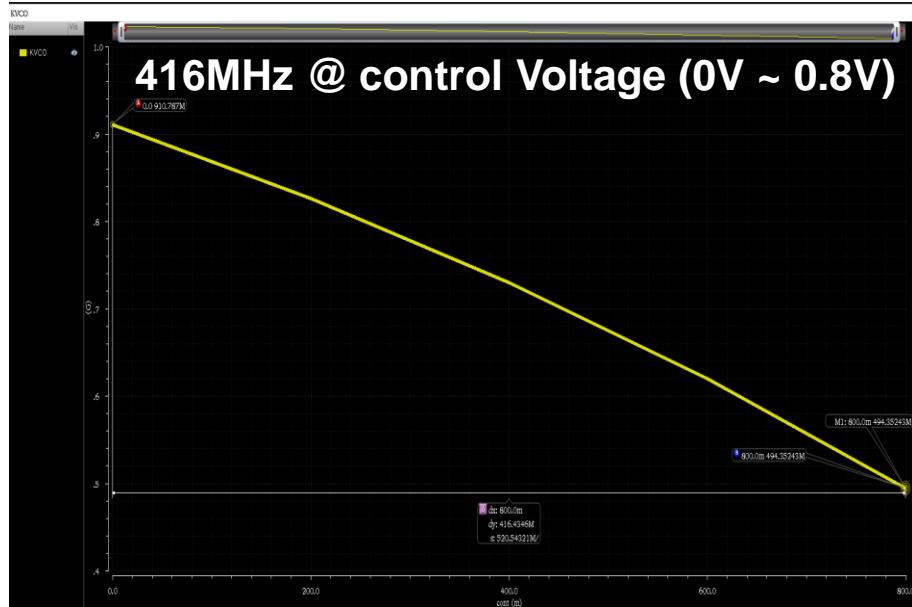- Ring VCO : 416MHz @ control voltage (0V ~ 0.8V)
- LC VCO : 110MHz @ control voltage (0V ~ 1.8V)
- **Ring VCO is better for frequency tuning range.**



Assignments

- Design 2GHz (±100MHz) LC VCO with frequency tuning range 100MHz.
 - Verify and plot output waveforms and frequency tuning range.
 - Verify and plot phase noise with control voltage 0V , 0.9V and 1.8V.
 - Indicate LC VCO schematic, inductor and capacitor value, and using varactor design value.
-
- LC VCO specification
 - VDD supply voltage : 1.8V
 - Bias voltage : 0.8V
 - Phase noise : Min -115dBc/Hz
 - Frequency tuning range : Min 100MHz
-
- Due: 29 Mar. 9:30(Hardcopy)

Q & A

superpyunki@gmail.com