

Quiz 5

May 24, 2016

E&M II

Prof. Woo-Young Choi


Name:

Prob. 1(3)

A transmission line circuit is connected to an ideal current source, which produces a constant step current of I_0 at $t=0$ as shown below. The length of the line is L and the velocity of wave propagation on the line is v .

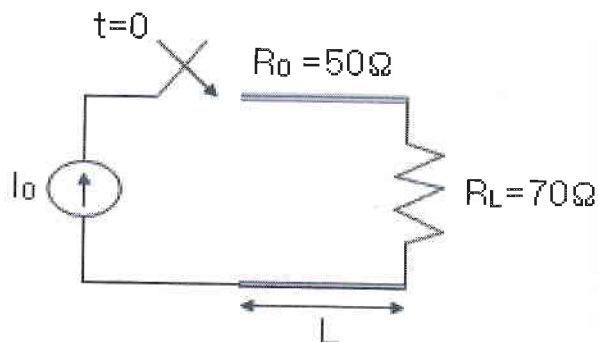
- (a) Sketch the voltage on the line, $V(z)$, for $t = 0.5 L/v$.
- (b) Sketch the current on the line, $V(z)$, for $t = 1.5 L/v$.
- (c) Sketch the voltage on the line, $V(z)$, for $t = \infty$.

Make sure you express the magnitude of waves in terms of I_0 .



Prob. 2(4)

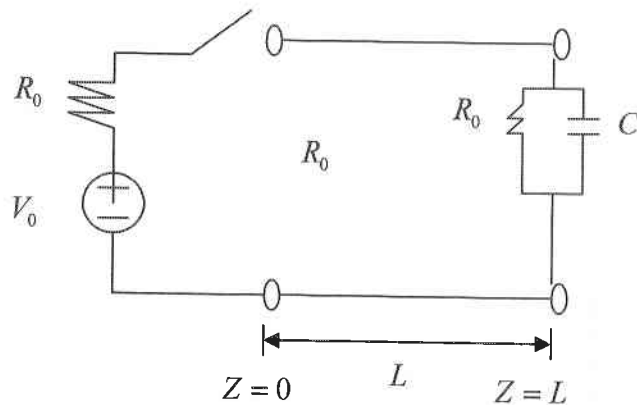A load made up of a resistor and a capacitor in parallel is connected to a transmission line as shown below. A step voltage is applied to the transmission line at $t = 0$. The capacitor is free of charge initially and the voltage wave propagates the transmission line with velocity v .




(a)(2) Plot $v_L(t)$, the voltage across the load. Make sure you specify important parameters in your plot.

(b)(2) Plot $v(t)$ at $z = L/2$. Make sure you specify important parameters in your plot.

Prob. 3(3)

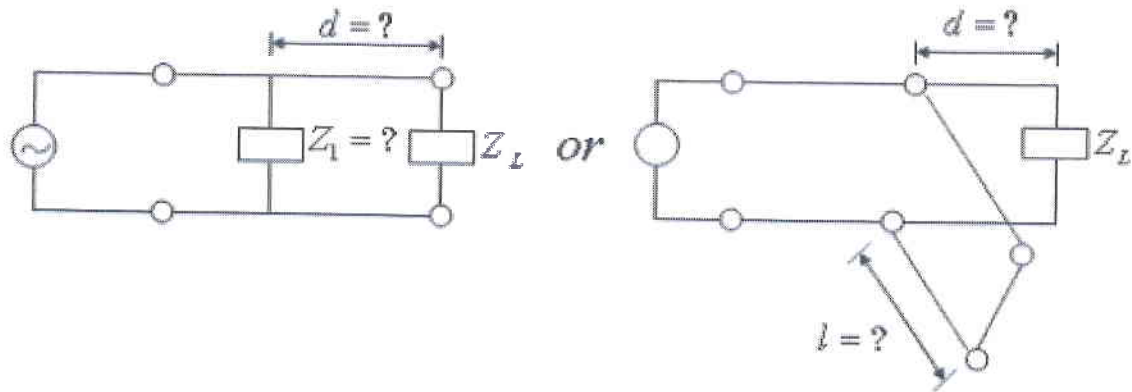We want to achieve impedance matching for a load having $Z_L = 20 - j 20(\Omega)$ by placing a short-stub on the transmission line. Use the Smith Chart answering following questions. Assume the transmission line has characteristic impedance of 50Ω .



- Determine the shortest possible distance for d in terms of wavelength λ .
- Determine the impedance for Z_1 .
- Determine the shortest possible short stub length in terms of wavelength λ .

