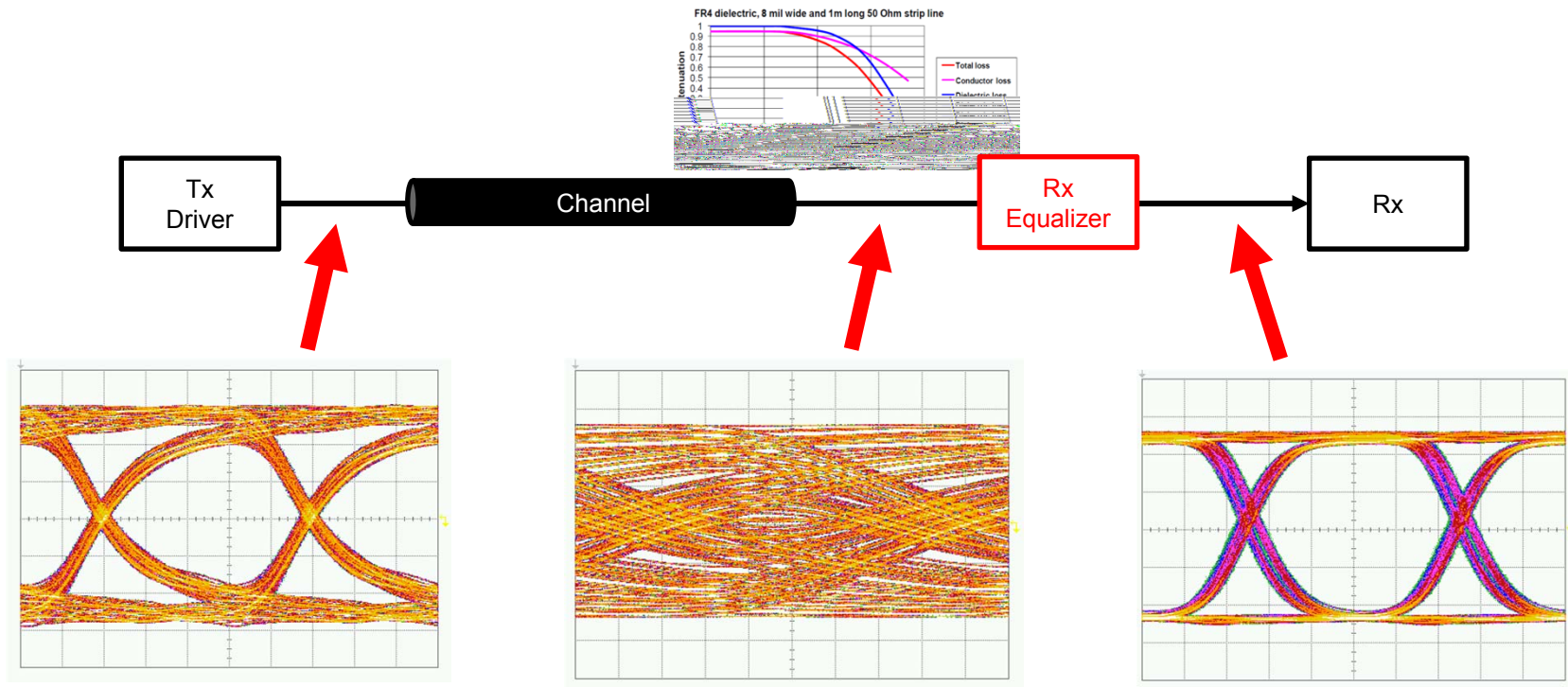


# **High-speed Serial Interface**


## **Lect. 9: Equalizers**

# Why equalization?

- Intersymbol interference (ISI) caused by frequency-dependent loss of channel



# Linear Equalizer

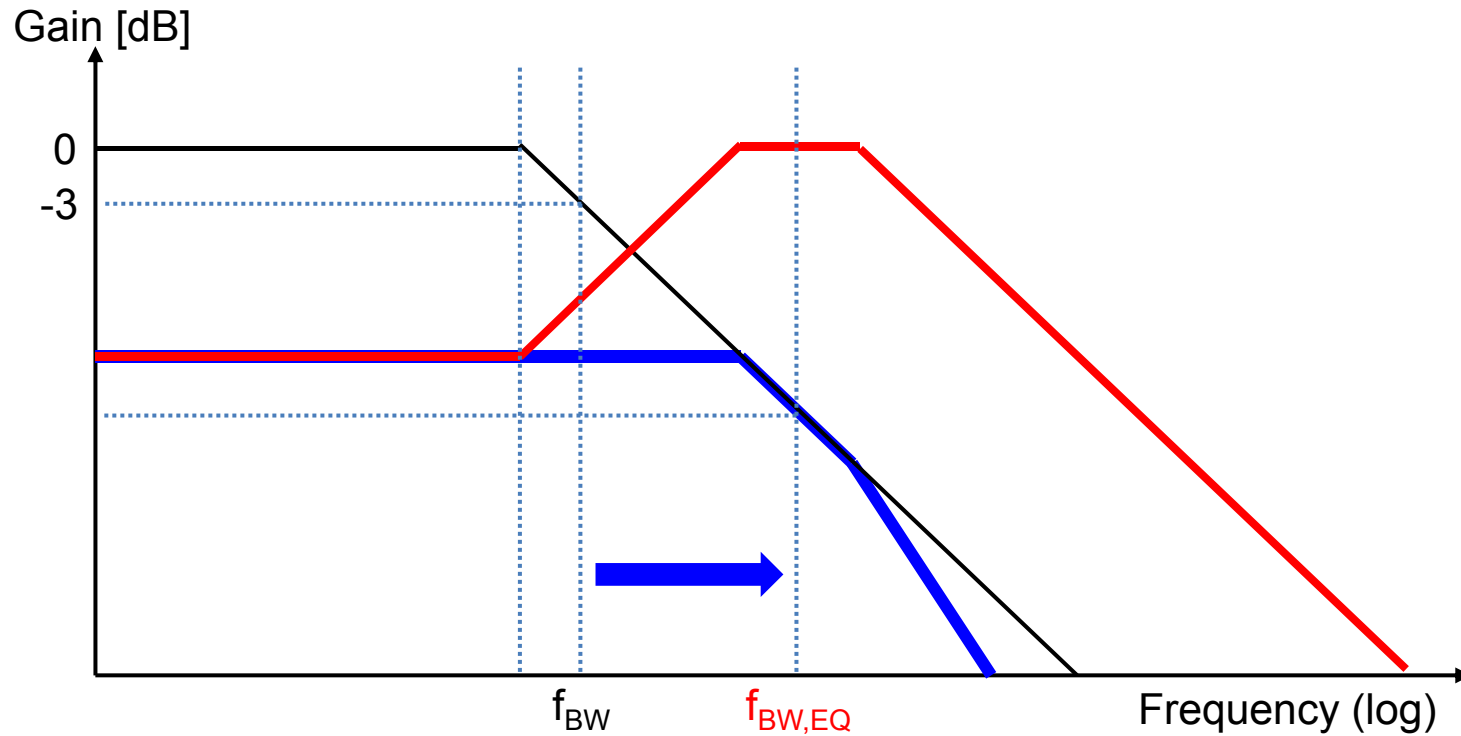


High-pass filter / High-frequency boosting

→ Continuous Time Linear Equalizer (CTLE)
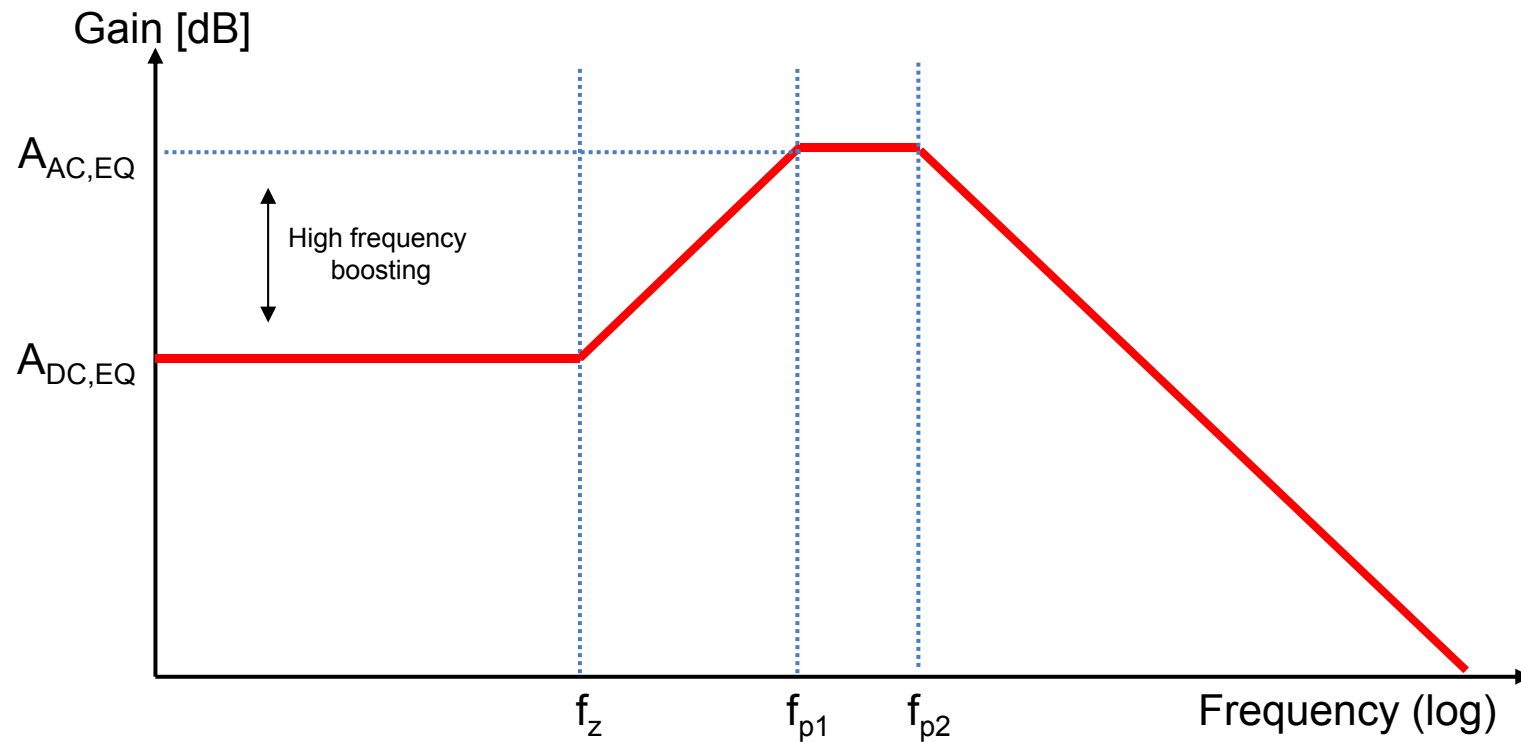
# CTLE Frequency Response

Assuming channel has one pole,  
CTLE should provide 1 zero and 2 poles




# Tunability

- CTLE should be tunable
  - Channel variation
    - Variations in channel fabrication
    - Uncertainty in channel modeling
    - Channel degradation/defect after usage
  - PVT variation of equalizer

➔ Tunability is a must


# Tunability

- Tuning for pole/zero locations

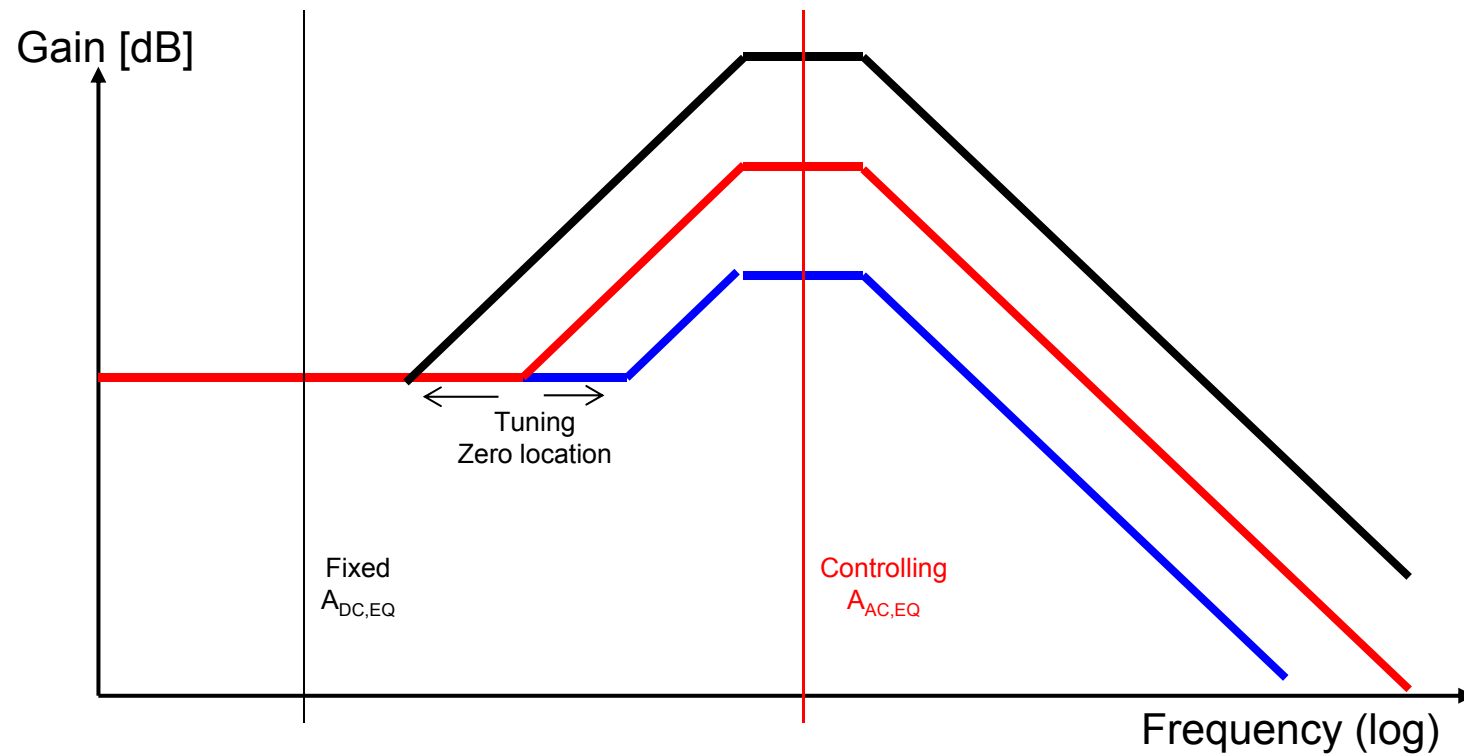

# Controllability

- Tuning DC gain

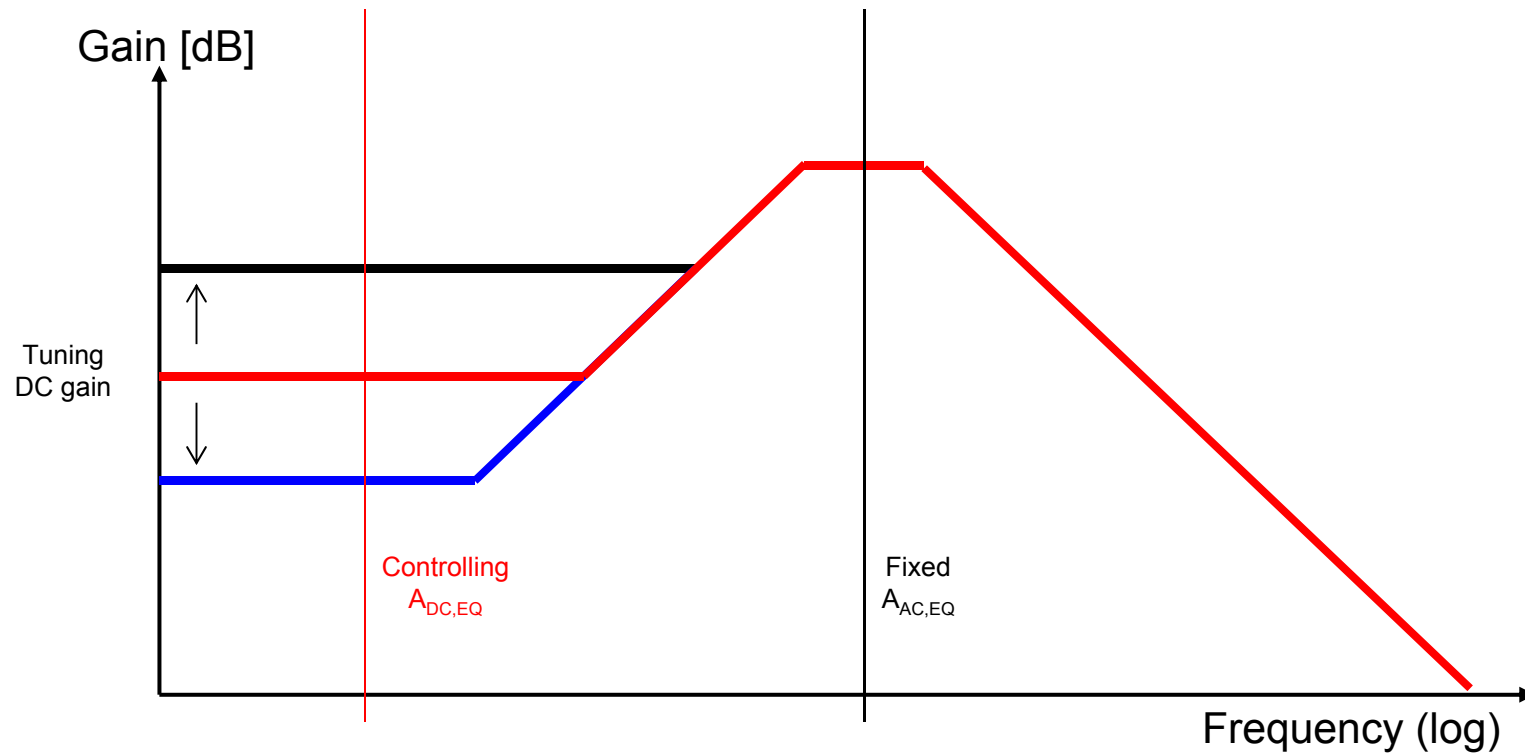

# Passive CTLE

- Various passive high-pass filters available

No power consumption

But


- Lossy
- PVT dependent
- Difficult to achieve 50-ohm matching
- Difficult to tune
- Often large size



# Active CTLE

- Differential amplifier
  - Basic differential amp. has 1 pole from load capacitance


$$|G(\omega)| \sim \frac{\left( \frac{1}{\omega} \right)}{\left( \frac{1}{\omega} \right)}$$

 

# Active CTLE

- Inductive load
  - Shunt inductor provides a pole/zero pair


$$|G(\omega)| \sim \left( \frac{1}{1 + \omega^2 L_{load}^2} \right)$$

 

# Source Degeneration for CTLE

$$|G(\omega)| \sim \left( \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_{deg}^2}}} \right)$$
 
$$\frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_{deg}^2}}} \left( \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_{deg}^2}}} \right)$$




# Source Degeneration for CTLE

- Capacitive generation provides high-frequency boosting since a capacitor has lower impedance at high frequency

$$\left( \frac{1}{1 - \frac{1}{2}} \right) \parallel \frac{1}{2}$$

 
$$\left[ \frac{1}{2} \right] \parallel \left[ \frac{1}{2} \right]$$



→ Design Exercise
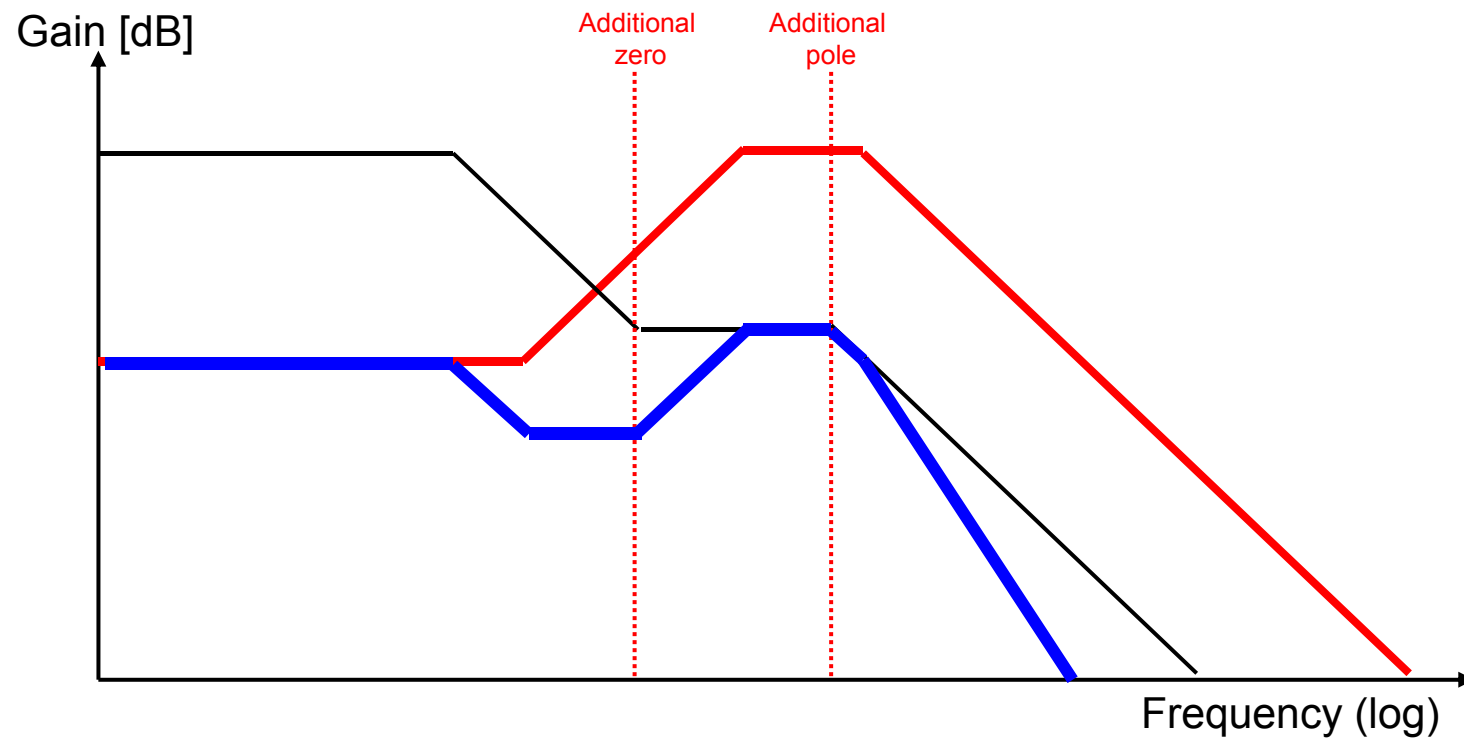
# Limitations of CTLE

- Channels may not be properly modeled with one pole




# Limitations of CTLE

- Applicable to only ISIs due to linear frequency-dependent loss
- Other causes for ISI are;
  - Impedance mismatching
  - Differential offset
  - Cross-talk
  - Parasitic poles and zeros (ex: package parasitic)




# Limitations of CTLE

- High-frequency Noise boosting

 
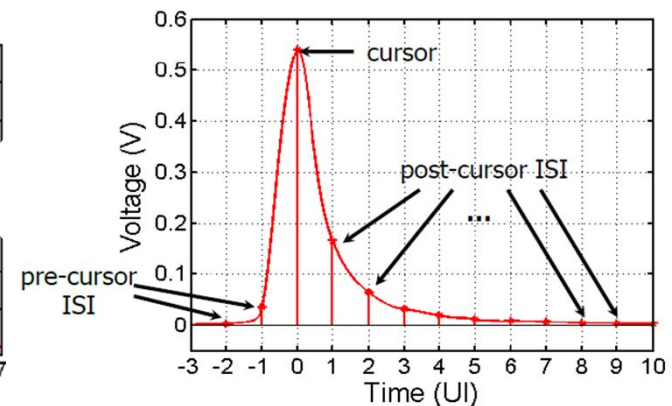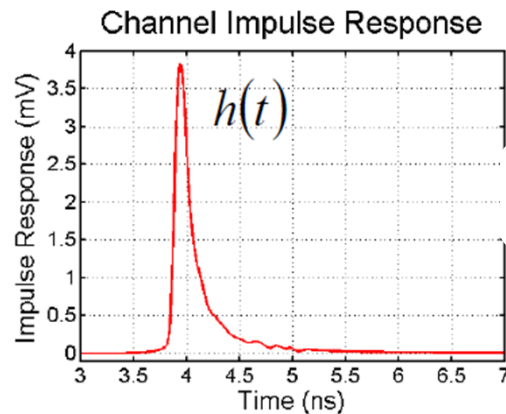 
# Time-Domain Analysis

- Frequency-Domain Analysis
  - Freq. Response of Input x Freq. Response of Channel x Equalizer = Freq. Response of Output
- Time-Domain Analysis




- Equalization: Force pre- and post-cursors to zero



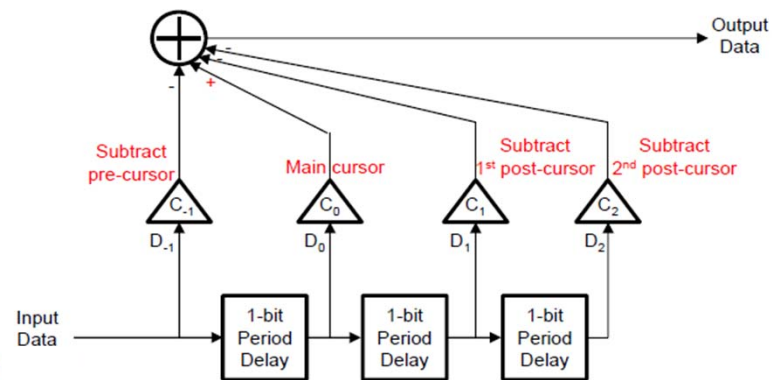
# FIR Filter

- Any CTLE filter can be converted into a discrete-time domain filter
- IIR (Infinite Impulse Response) → FIR (Finite Impulse Response)



Tap and Delay

 


- Hard to implement Rx FIR filter because the precise amount of delay (clock period) is not available in Rx

→ Tx FIR filter

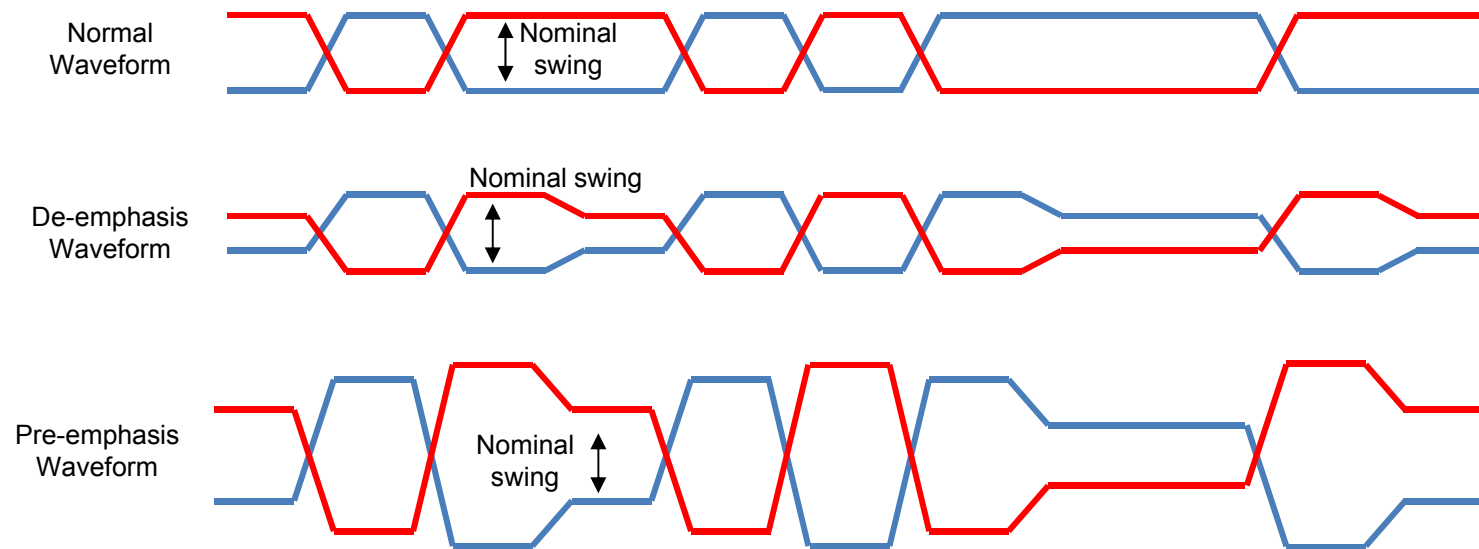
# Pre-/De-Emphasis

- Tx FIR is also called Feed-Forward Equalizer (FFE) or Pre-/De-Emphasis
  - Pre-emphasis: to enhance high-frequency components
  - De-emphasis: to reduce low-frequency components


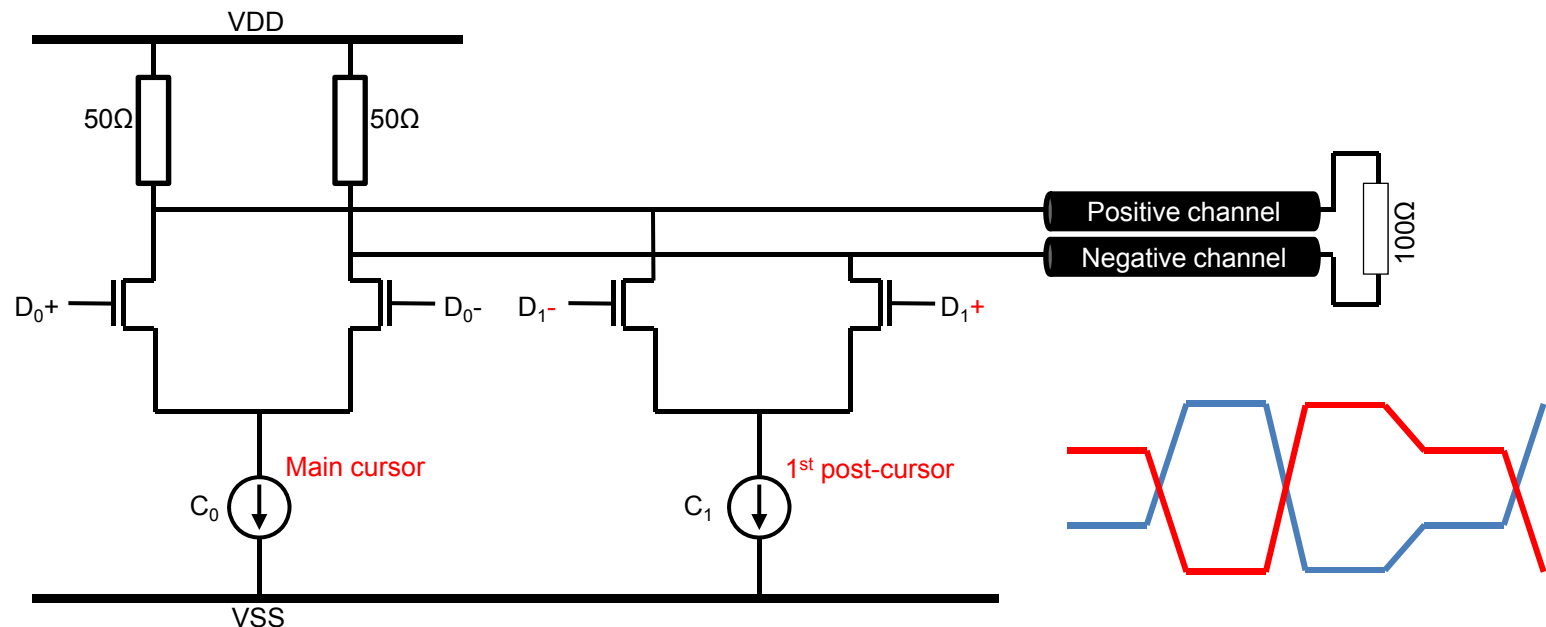
# Circuit implementation


- Current-mode drivers can be easily used for pre-/de-emphasis
  - $D_1 = D_0 \rightarrow V_{out,diff} = +/-50 \times (C_0 - C_1)/2$
  - $D_1 \neq D_0 \rightarrow V_{out,diff} = +/-50 \times (C_0 + C_1)/2$
  - Level difference is defined as sum and subtract



→ Design Exercise
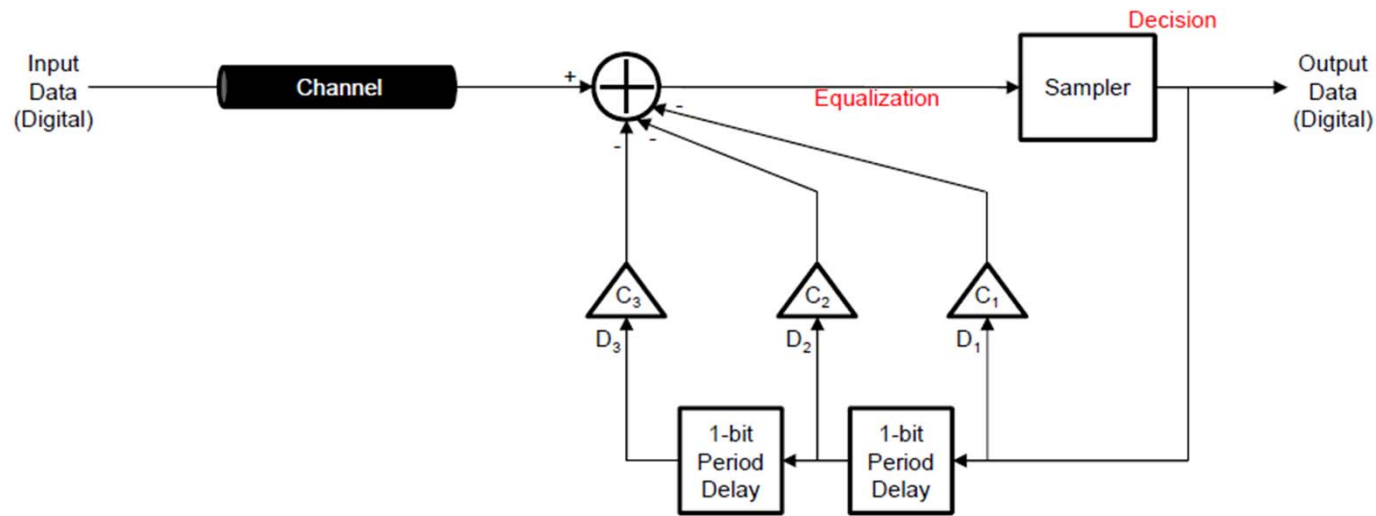
# Decision Feedback Equalizer (DFE)

- Non-linear equalization based on sampling



- Complicated but can provide high-performance equalization
- Requires clock signals for sampling
- Often used with CTLE

