

# **High-Speed Serial Interface Circuits and Systems**


**Lect. 2 – Ring Oscillators**

Oscillator: A device undergoing periodic changes in certain physical quantities



Our interests: MOS circuits that oscillate


Consider a negative feedback system

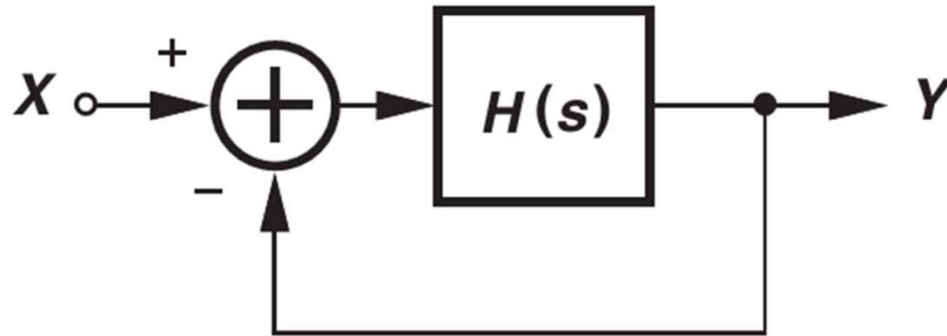

$$\frac{Y}{X}(s) = \frac{H(s)}{1 + H(s)}$$

What happens when  $H(j\omega) = -1$  ?

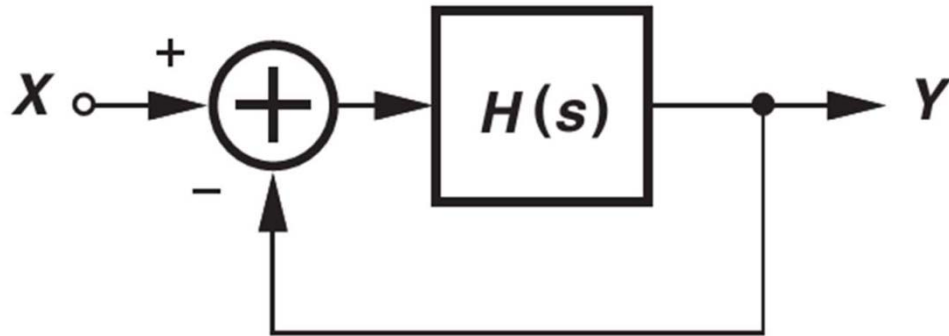- ➔ Unstable
- ➔ Output without input?
- ➔ Oscillation at  $\omega$



$$\frac{Y}{X}(s) = \frac{H(s)}{1 + H(s)}$$


Barkhausen oscillation condition:  $|H(j\omega)| = 1$  and  $\angle H(j\omega) = 180^\circ$




Heinrich Barkhausen (1881-1956)

German  
physicist / electrical engineer

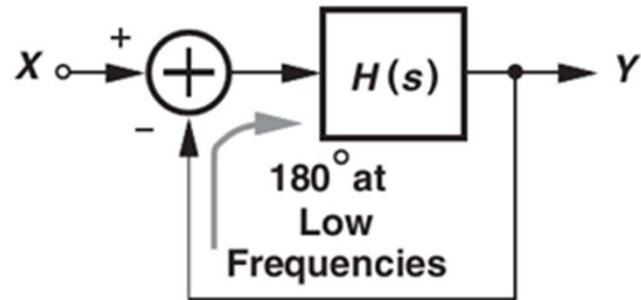
Invented first vacuum tube  
electronic oscillator in 1920




Barkhausen oscillation criterion:  
 $|H(j\omega)| = 1$  and  $\angle H(j\omega) = 180^\circ$

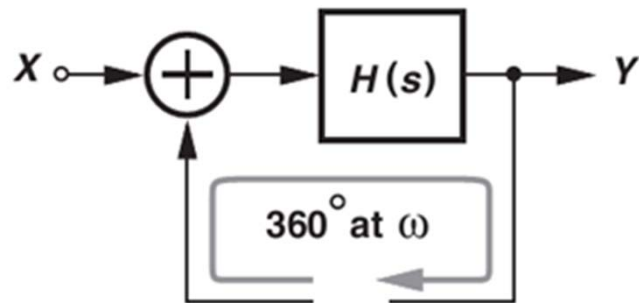

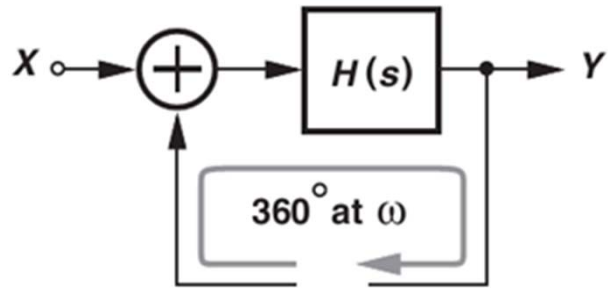➔ in phase and same magnitude  
 after one round trip




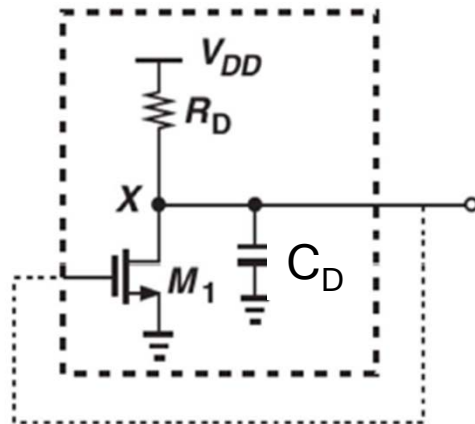Oscillation:  
in phase and same magnitude after one round trip




$C_D$  represents all capacitive elements

Oscillation?

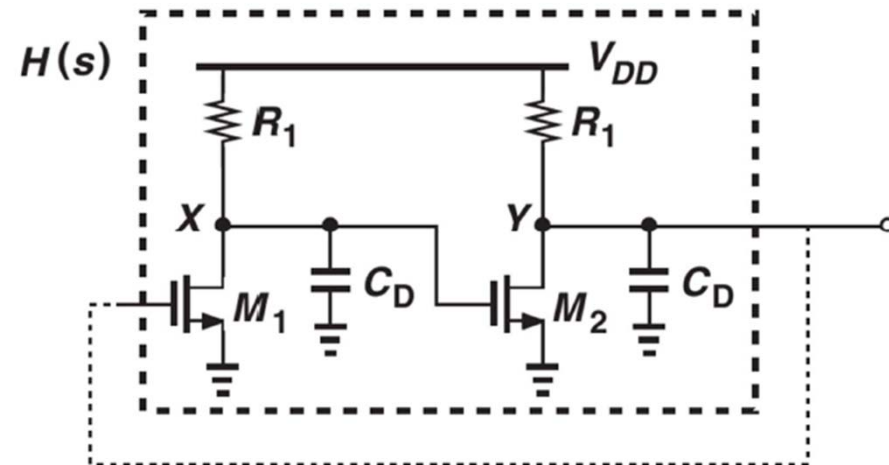

Oscillation?

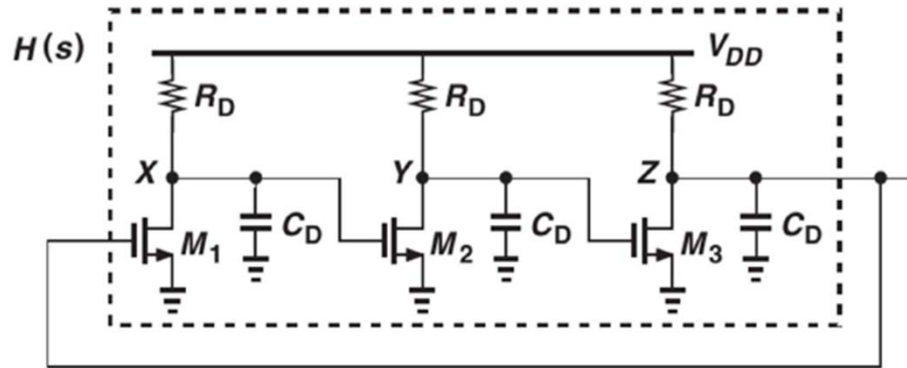

$$H(j\omega) = -\left(\frac{g_m R_D}{1 + j\omega R_D C_D}\right)^3$$

Ring oscillator

$$\angle\left(\frac{g_m R_D}{1 + j\omega R_D C_D}\right)^3 = -\pi$$

$$|H(j\omega)|^3 = 1$$




$$-3 \tan^{-1}(\omega R_D C_D) = -\pi$$

$$\omega R_D C_D = \tan\left(\frac{\pi}{3}\right) = \sqrt{3}$$

$$\therefore \omega = \frac{\sqrt{3}}{R_D C_D}$$

$$|H(j\omega)|^2 = \frac{(g_m R_D)^2}{1 + (\omega R_D C_D)^2} = \frac{(g_m R_D)^2}{1 + 3} = 1$$


$$\therefore g_m R_D = 2$$

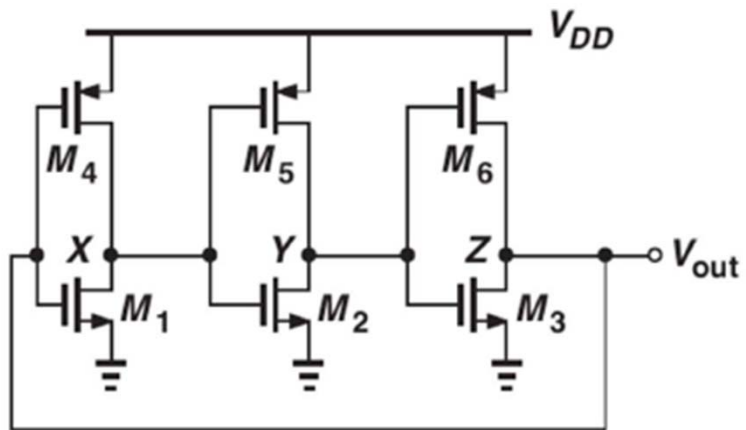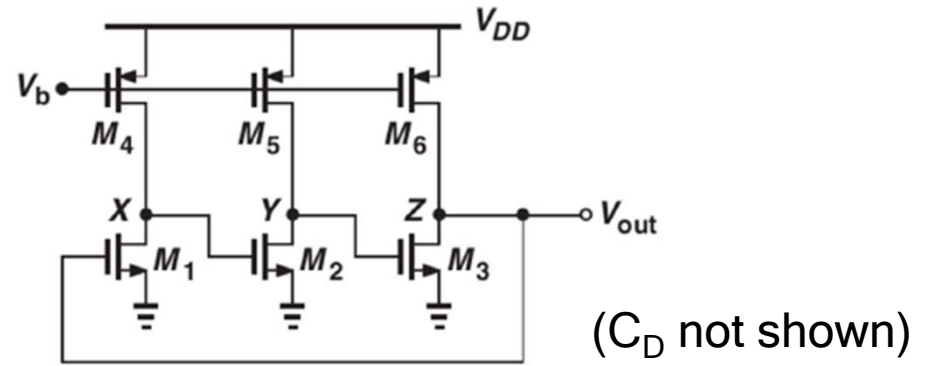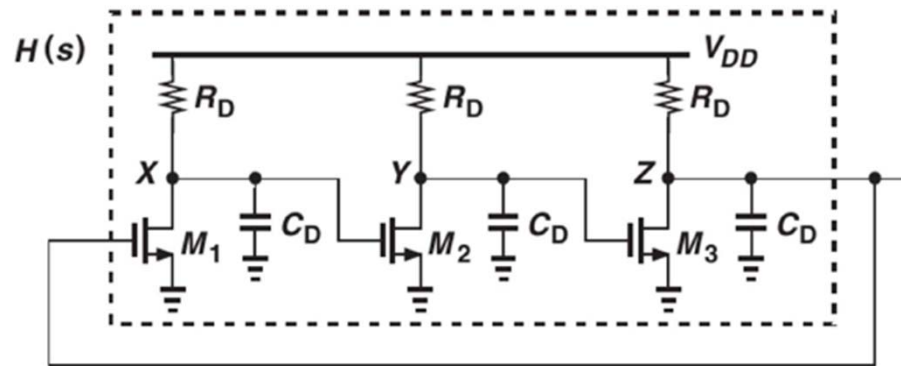

→ CMOS inverter


Gain for each stage
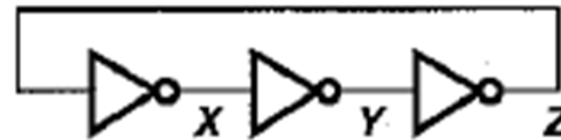
$$A_v = (g_{m1} + g_{m2})(r_{0n} \parallel r_{0p})$$



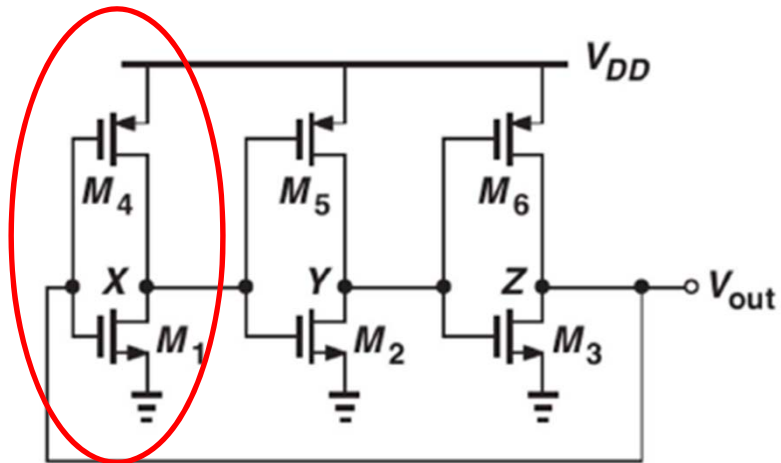
Without any input, what initiates oscillation?








How large is the oscillation?

→ Large signal analysis

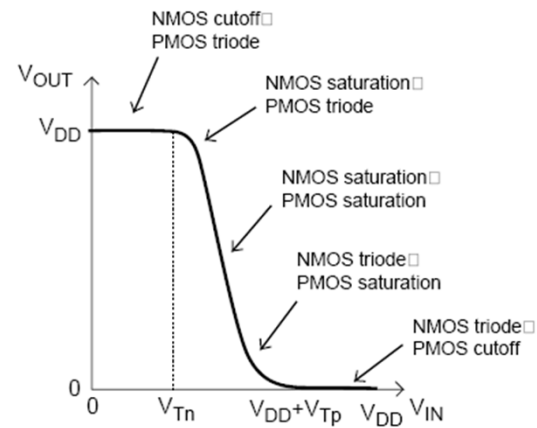

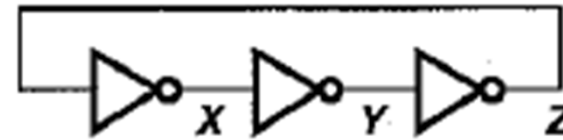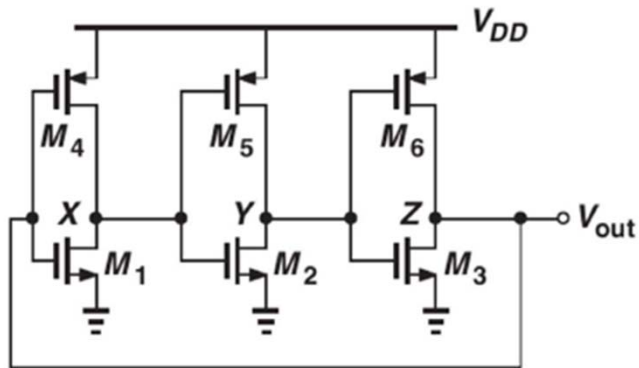

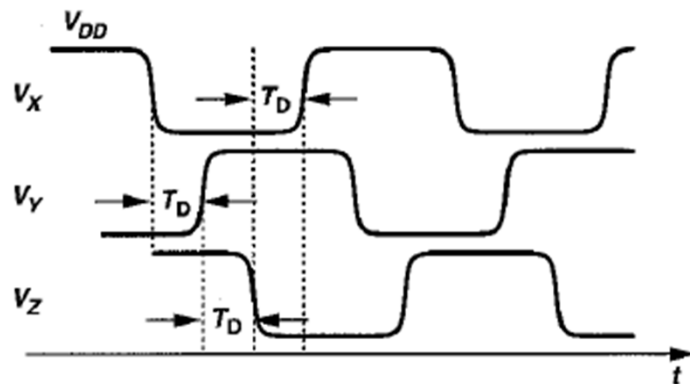Oscillation frequency with large-signal analysis?





$T_D$ : Time delay between input and output:

$$f_{\text{osc}} = 1 / (2 \times N \times T_D)$$

Requirement for N ?

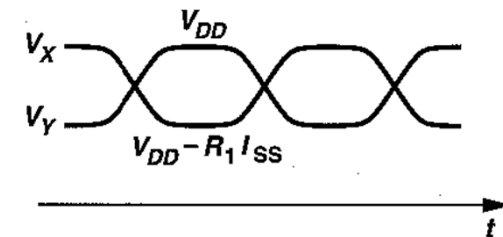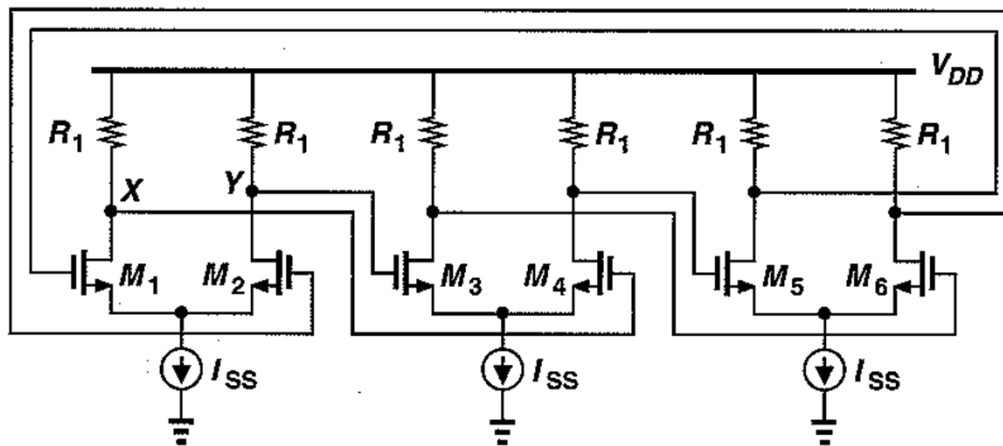
## Differential amplifier for ring oscillator



Can be faster than CMOS inverter chain but consumes more power

Even-number stage possible

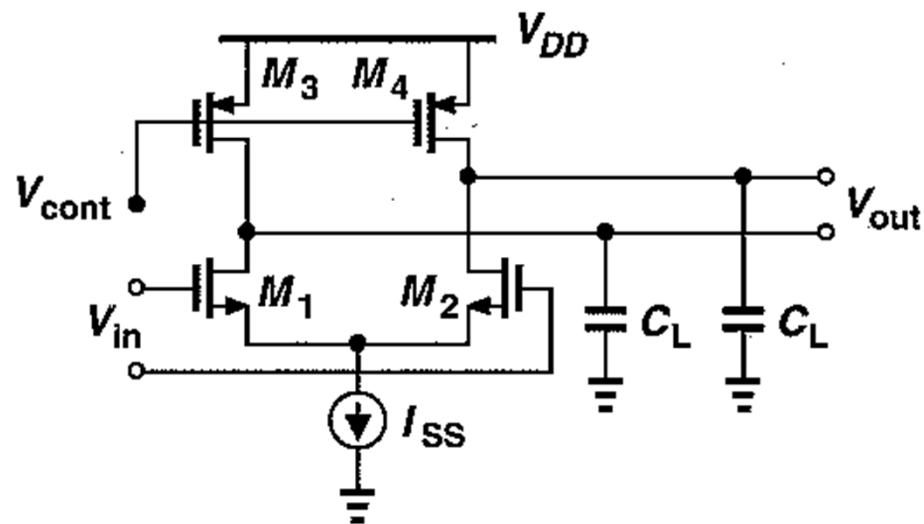How can we control oscillation frequency with voltages?  
(Voltage-Controlled Oscillator: VCO)



➔ Design Exercise