#### **High-speed Serial Interface**

#### Lect. 7 – TX Driver

(Ref.: Razavi, Prof. Palermo's Lecture Notes for "High-Speed Links Circuits and Systems", Texas A&M)



How to send digital data from Tx to Rx?

- Modulation Format? NRZ (Non-Return-to-Zero)



- More advanced formats are being considered for more demanding applications



PAM4 (Pulse Amplitude Modulation 4)



- NRZ Tx driver structure:

Single or differential signaling, current or voltage mode, termination

## **Simplest Tx Driver**



- CMOS inverter
- Voltage mode
- No static power consumption
- Operation speed is limited by full-swing (rail-to-rail)
- Impedance matching is difficult

## **Open-Drain Tx Driver**



- Current mode
- Output voltage swing:  $I_{ss}R_L$
- Can be fast but static power consumption
- $R_L = Z_o$  for Rx impedance matching
- Noise immunity?

### **Differential Open-Drain**



- Current mode
- Differential signaling
- Output voltage swing: 2  $\rm I_{ss}R_{L}$
- Much better noise immunity
- Impedance matching on Tx side ?

# Single-ended vs Differential Signaling



- Larger output voltage swing for differential signaling
- Common-mode noise rejection with differential signaling
- Self-referencing for receiver threshold for differential signaling
  - Supply and ground levels can be different for TX and RX
- → Differential signaling much preferred for high-speed serial interface
- → High-speed circuits often use differential signaling for their logic circuits

#### **Current-Mode Logic (CML) Driver**



- Current mode
- Differential signaling
- Termination:  $R_1 = R_2 = R_L = Z_0$
- Output voltage swing

$$V_{d,1} = (I_{SS}/2) R_L$$
  $V_{d,pp} = I_{SS} R_L$   
 $V_{d,0} = - (I_{SS}/2) R_L$ 

→ Most popular for high-speed serial interface applications

## **50-\Omega termination**

- Why  $50\Omega$  for transmission lines?
  - Historical reason
    - For coax cables for early microwave systems (1930s),
      - $-33\Omega$  gave best performance in max power handling capacity
      - $75\Omega$  gave the minimum loss
      - 50  $\Omega,$  a value close to the medium (54  $\Omega)$  was selected as a compromise
    - Nowadays, almost all high-speed instruments, interconnects, circuits are 50Ω-based
      - Some CATV systems still use 75- $\Omega$  coax cables

#### CML with Differential Rx Termination





- Output voltage swing:

$$V_{d,1} = (I_{SS}/2) R_L$$
  
 $V_{d,0} = - (I_{SS}/2) R_L$   
 $V_{d,pp} = I_{SS} R_L$ 

- Output voltage swing:

$$V_{d,1} = (I_{SS}/4) 2R_L$$
  
 $V_{d,0} = - (I_{SS}/4) 2R_L$   
 $V_{d,pp} = I_{SS} R_L$ 

#### CML with Differential Rx Termination



## **DC/AC** Coupling



- Rx common-mode voltage? IR/2
  - → Cannot be independently controlled

- Rx common-mode?  $V_{\rm CM}$
- Low frequency cut-off
- Data must be coded
- 8B/10B: Map 8-bit symbol into 10-bit symbol so that counts for 1's and 0's are balanced (not more than five 1's or 0's)

→ Several standards use 8B/10B coding but there is overhead for data rate

## **Voltage-mode Tx Driver**



Current source + **Parallel** Tx termination



 $V_{d,1} = (V_s/2)$  $V_{d,0} = -(V_s/2)$  $V_{d,pp} = V_s$  $I = (V_s/2R)$  $I = \frac{V_{d,pp}}{2R}$ 

 $V_{d,1} = (I/2)R$ 

 $V_{d,0} = -(I/2)R$ 

 $V_{d,pp} = IR$ 

 $I = \frac{V_{d,pp}}{R}$ 

Voltage source + **Serial** Tx termination

→ Voltage mode driver

Factor of 2 Tx power reduction

### **Differential Rx Termination**



Single-ended Rx termination



**Differential Rx termination** 

Further power reduction of factor 2

$$V_{d,1} = (V_s/2)$$
$$V_{d,0} = -(V_s/2)$$
$$V_{d,pp} = V_s$$
$$I = (V_s/2R)$$
$$I = \frac{V_{d,pp}}{2R}$$

$$V_{d,1} = (V_s/2)$$
$$V_{d,0} = -(V_s/2)$$
$$V_{d,pp} = V_s$$
$$I = (V_s/4R)$$
$$I = \frac{V_{d,pp}}{4R}$$

#### **Voltage Mode Driver Implementation**





## **Tx Termination**



Replica circuits fix the voltages so that the desired Tx output impedance is achieved