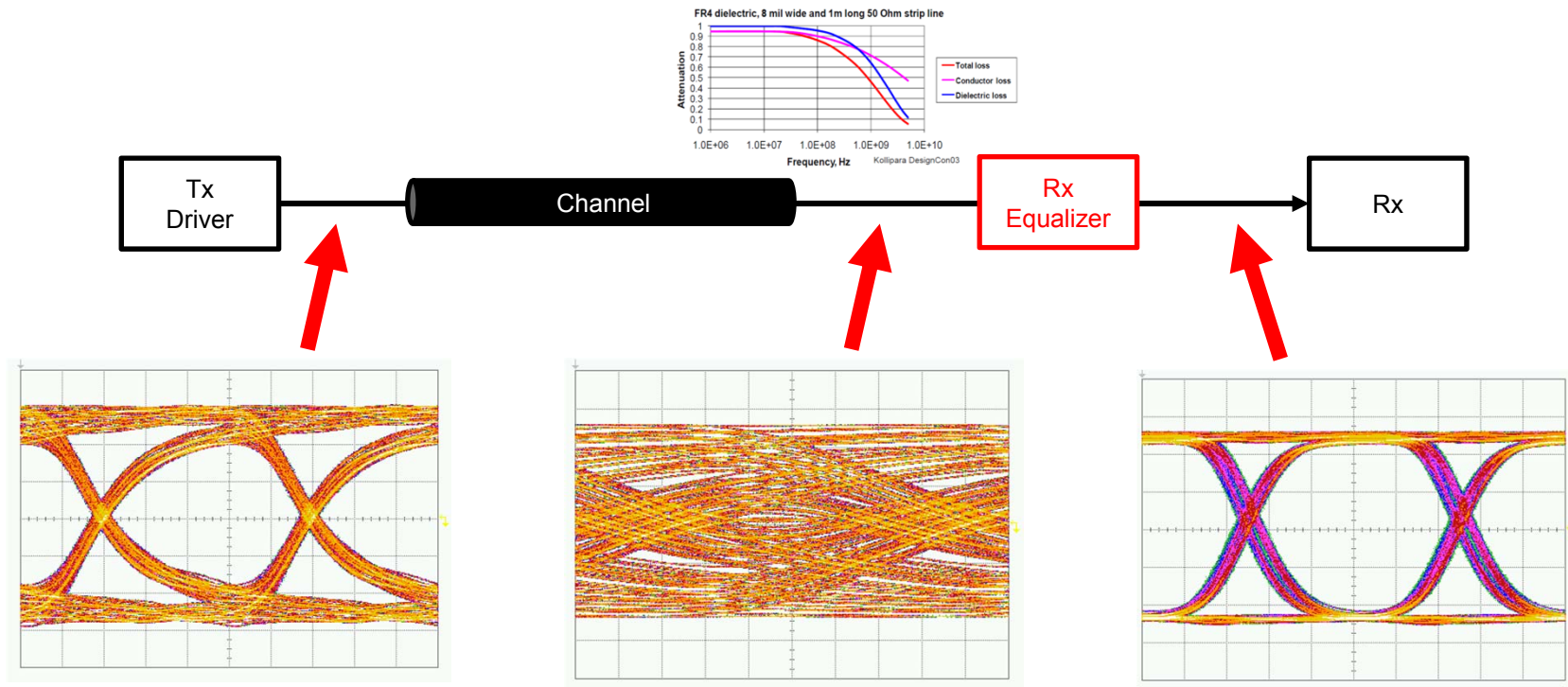


High-speed Serial Interface


Lect. 8: Linear Equalizers

Why equalization?

- Inter-symbol interference (ISI) caused by frequency-dependent loss of channel



Equalizer Frequency Response

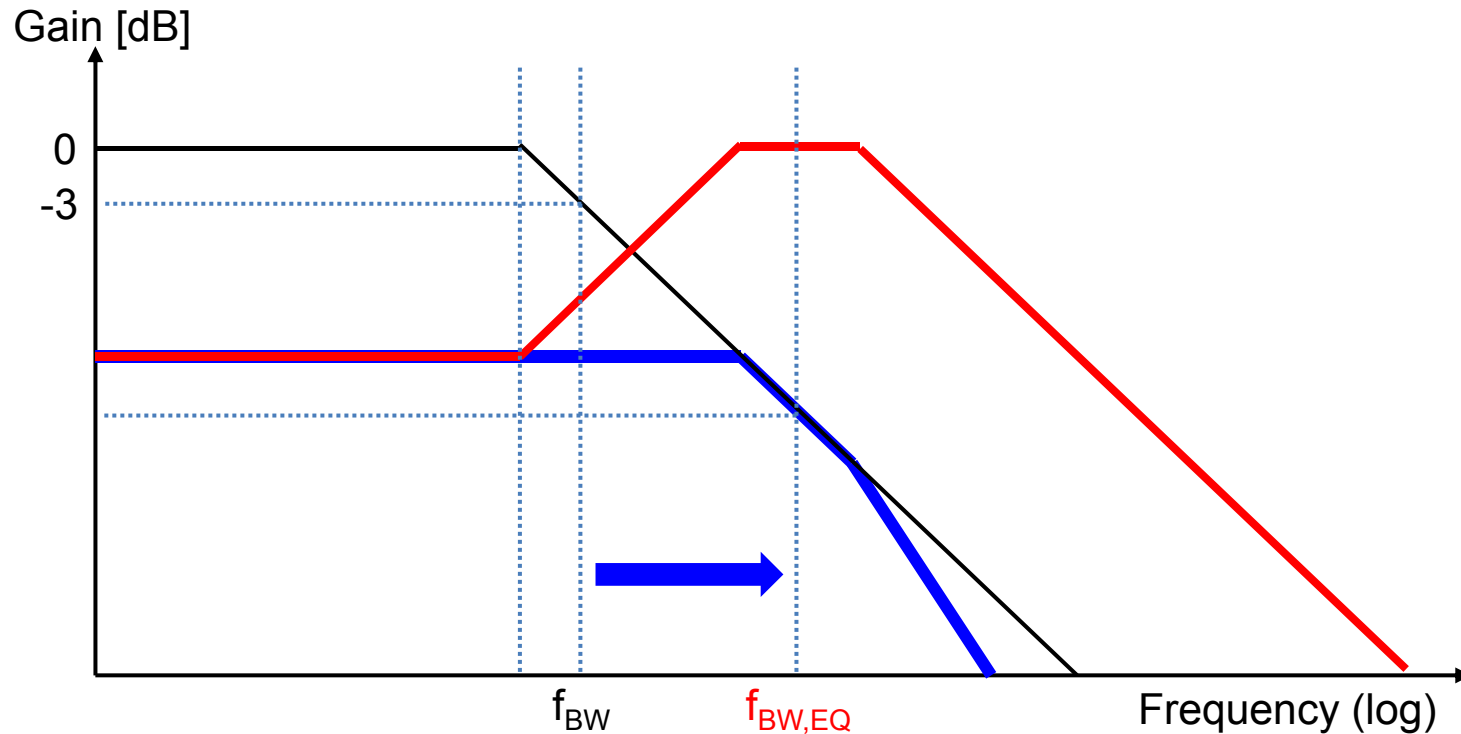


High-pass filter / High-frequency boosting

→ Continuous Time Linear Equalizer (CTLE)

CTLE Frequency Response

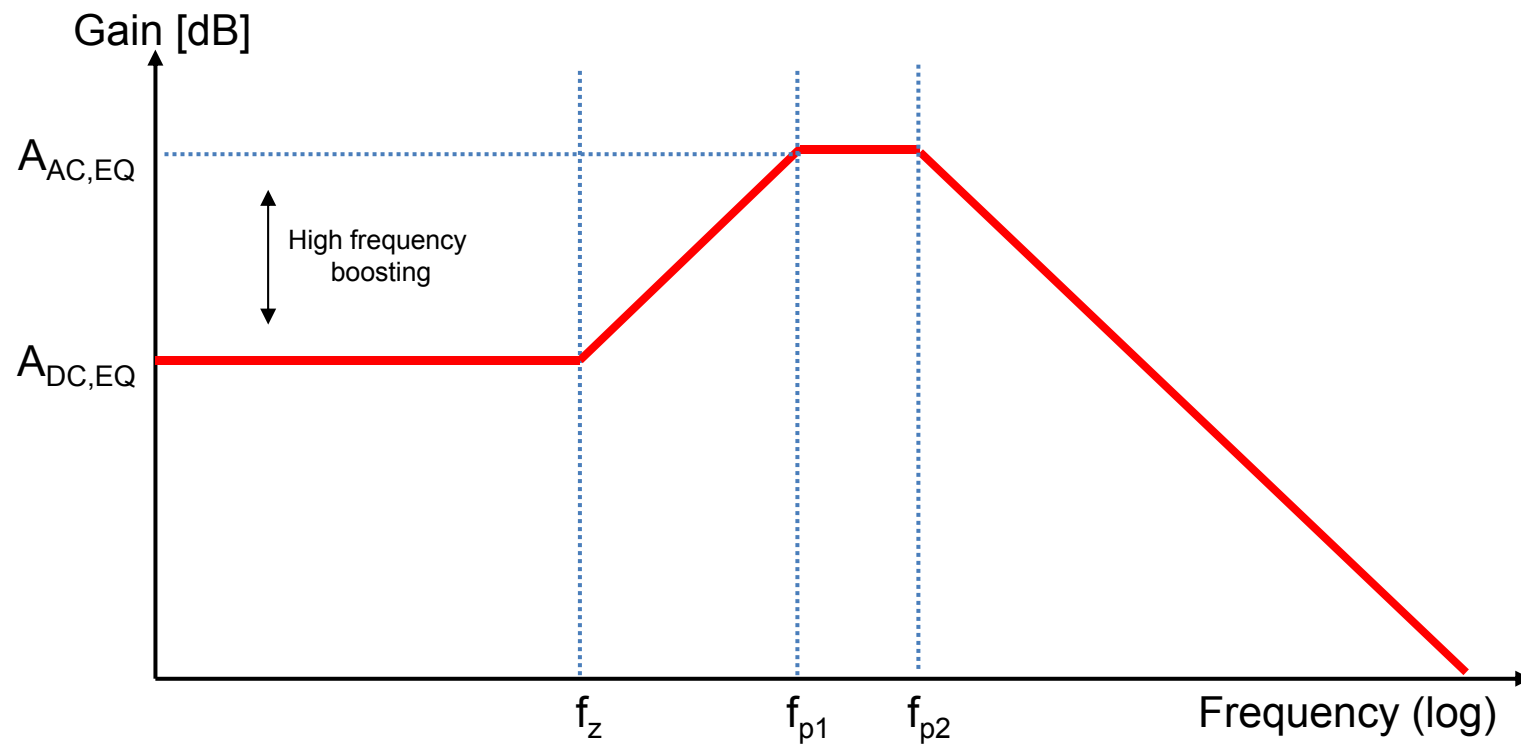Assuming channel has one pole,
CTLE should provide 1 zero and 2 poles




Tunability

- CTLE should be tunable
 - Channel variation
 - Variations in channel fabrication
 - Uncertainty in channel modeling
 - Channel degradation/defect after usage
 - PVT variation of equalizer

➔ Tunability is a must


Tunability

- Tuning pole/zero locations

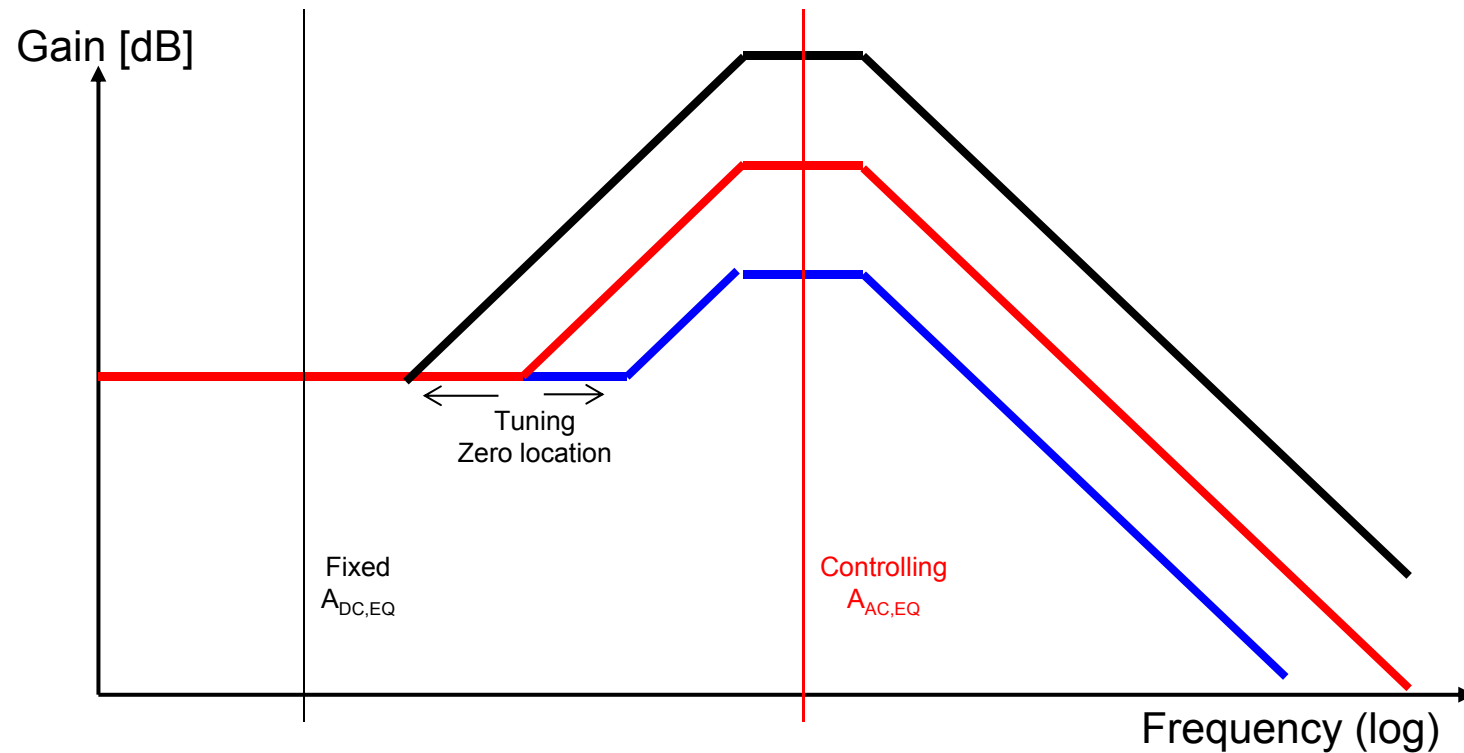

Controllability

- Tuning DC gain

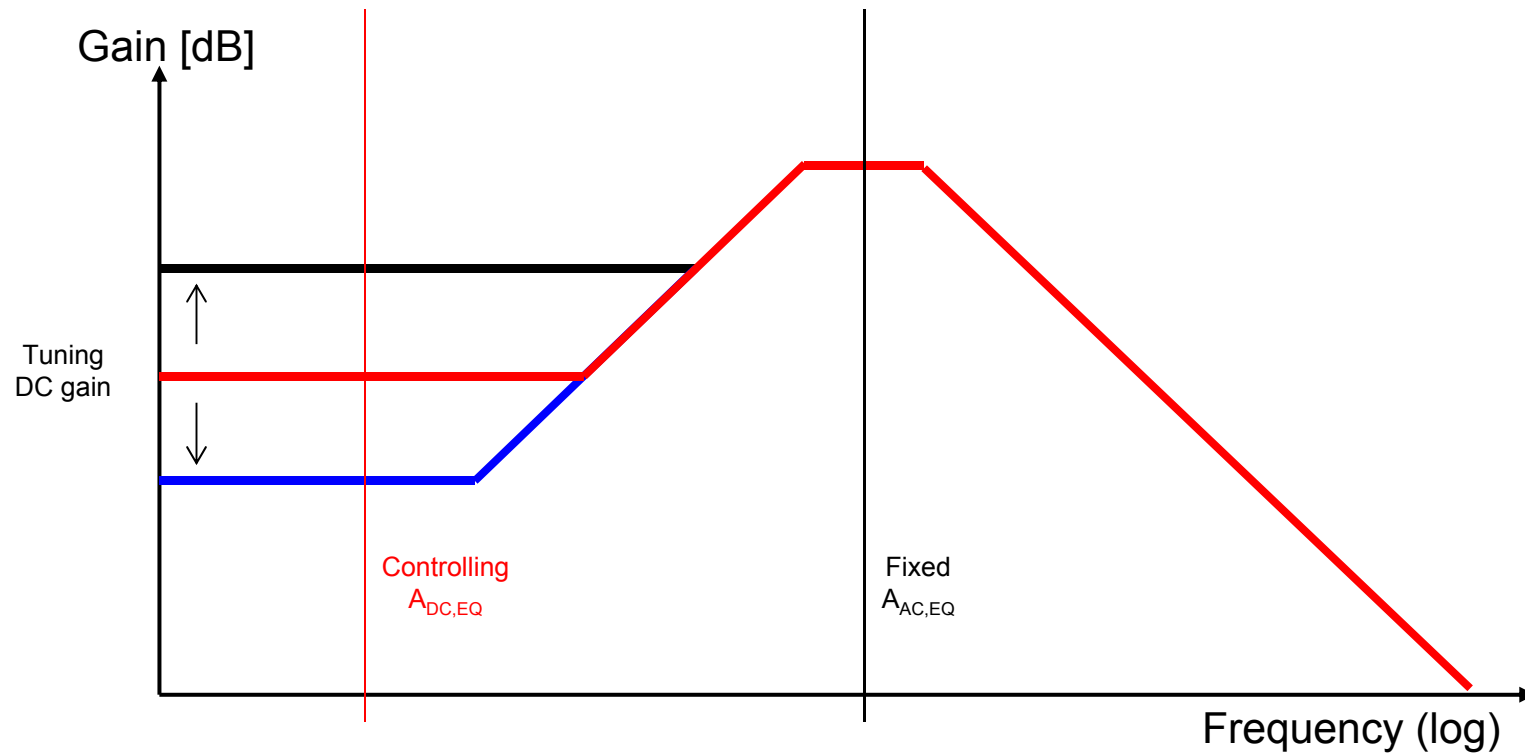

Passive CTLE

- Various passive high-pass filters available

No power consumption


But

- Lossy
- PVT dependent
- Difficult to achieve 50-ohm matching
- Difficult to tune
- Often large size

Active CTLE

- Differential amplifier
 - Basic differential amp. has 1 pole from load capacitance


$$|H(s)| \sim g_m \left(Z_{load} \parallel \frac{1}{sC_{load}} \right)$$
$$= \frac{g_m}{\left(sC_{load} + \frac{1}{Z_{load}} \right)}$$

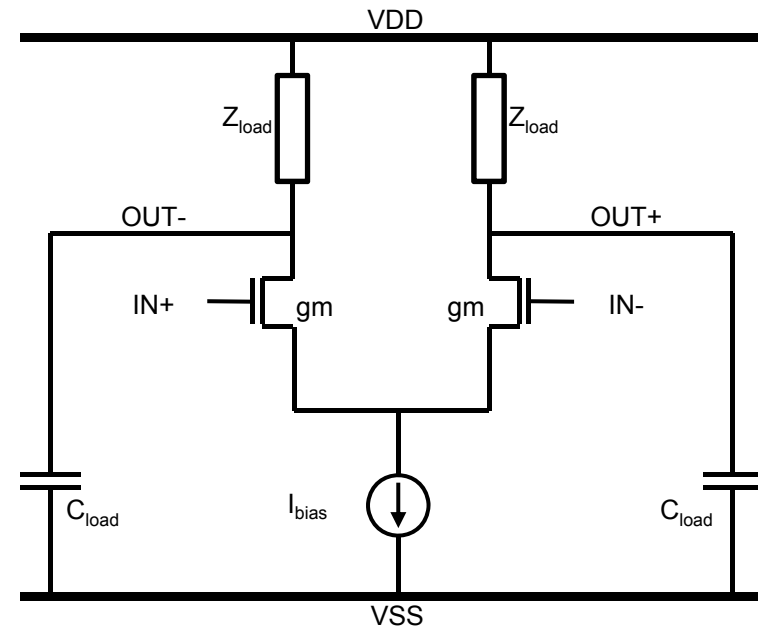

Active CTLE

- Inductive load
 - Shunt inductor provides a pole/zero pair


$$\begin{aligned}
 |H(s)| &\sim g_m \left(Z_{load} // \frac{1}{sC_{load}} \right) \\
 &= \frac{g_m}{\left(sC_{load} + \frac{1}{sL_{load} + R_{load}} \right)} \\
 &= \frac{g_m(sL_{load} + R_{load})}{(s^2L_{load}C_{load} + sR_{load}C_{load} + 1)}
 \end{aligned}$$

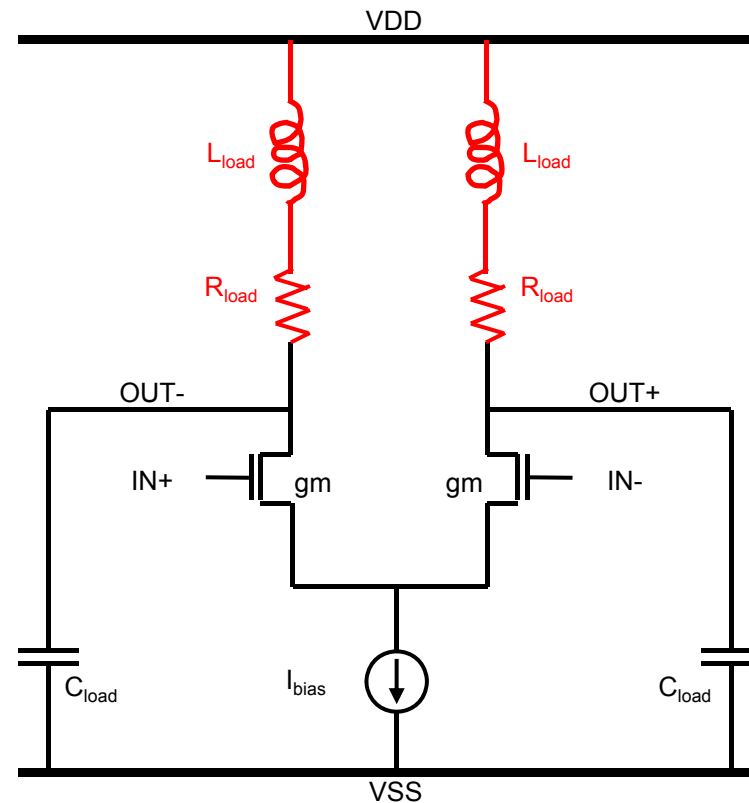

Source Degeneration for CTLE

$$|H(s)| \sim g_m' \left(Z_{load} \parallel \frac{1}{sC_{load}} \right)$$
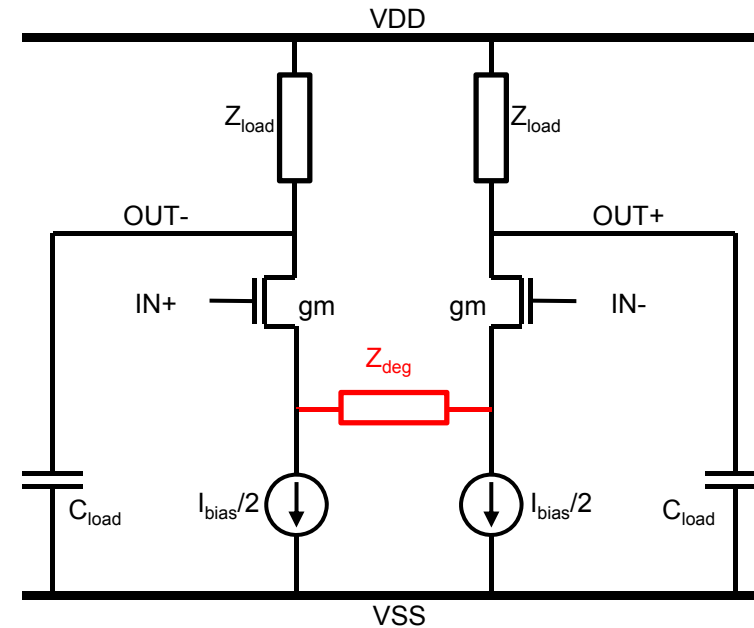
$$= \frac{g_m}{1 + \frac{g_m Z_{deg}}{2}} \left(Z_{load} \parallel \frac{1}{sC_{load}} \right)$$




Source Degeneration for CTLE

- Capacitive generation provides high-frequency boosting since a capacitor has lower impedance at high frequency

$$H(s) = \frac{g_m}{1 + \frac{g_m Z_{deg}}{2}} \left(Z_{load} // \frac{1}{sC_{load}} \right)$$

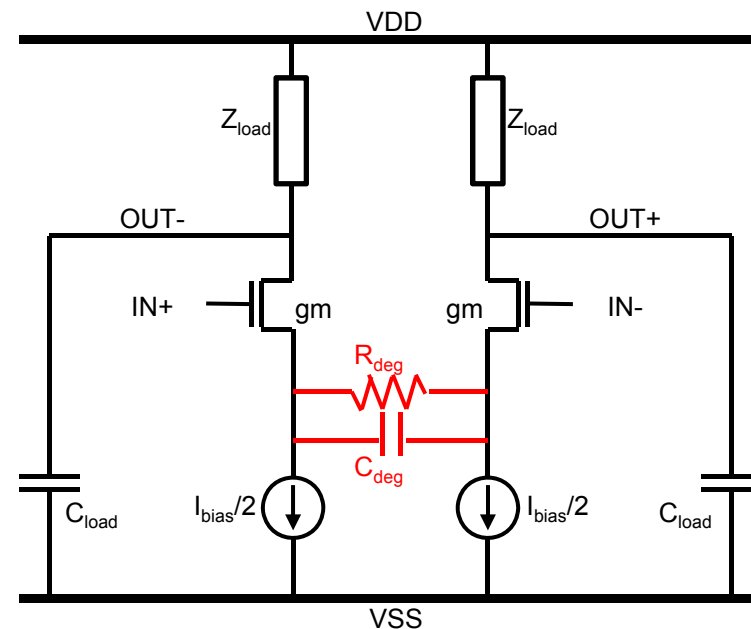
$$= \frac{g_m}{C_{load}} \frac{\left[s + \frac{1}{R_{deg}C_{deg}} \right]}{\left[s + \frac{1 + \frac{g_m R_{deg}}{2}}{R_{deg}C_{deg}} \right] \left[s + \frac{1}{Z_{load}C_{load}} \right]}$$



➔ Design Exercise

Limitations of CTLE

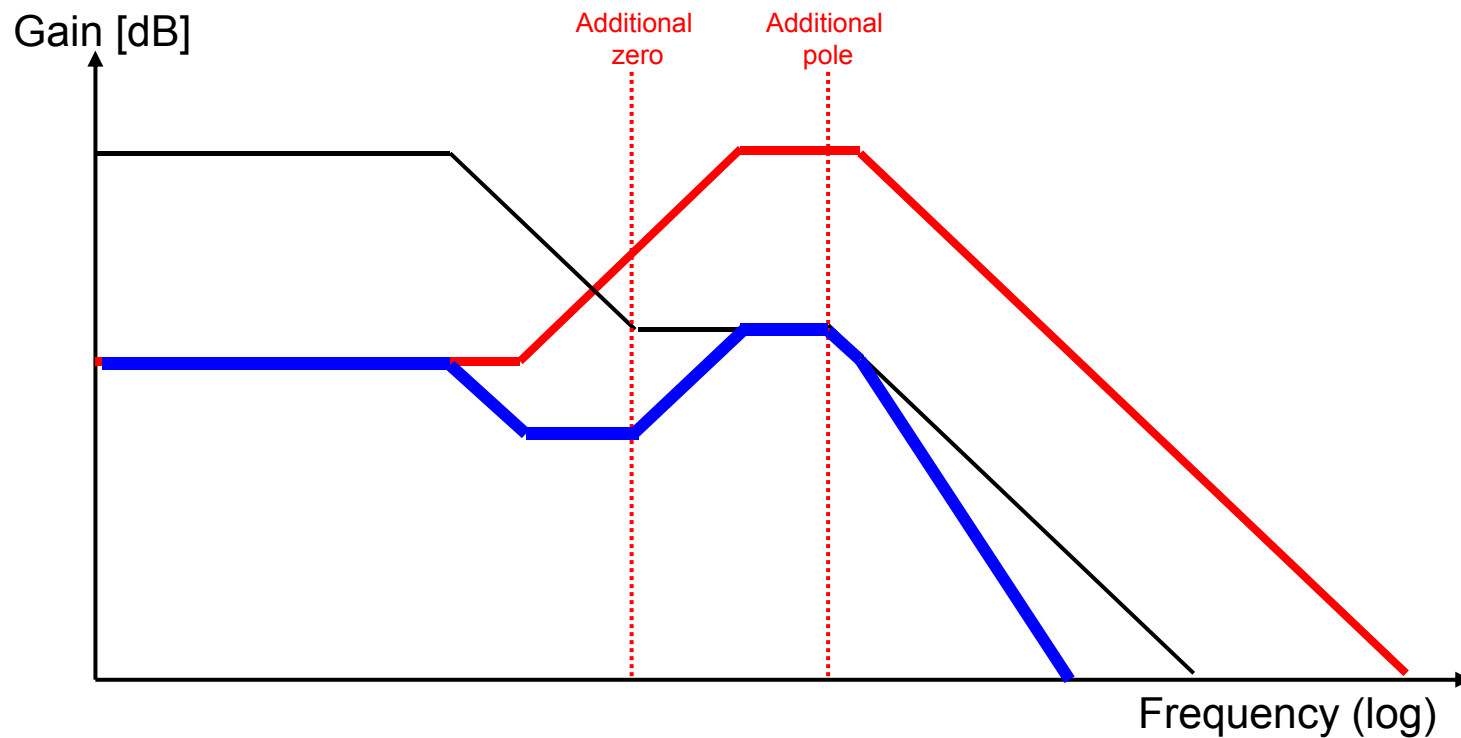- Channels may not be properly modeled with one pole




Limitations of CTLE

- Applicable to only ISIs due to linear frequency-dependent loss
- Other causes for ISI are;
 - Impedance mismatching
 - Cross-talk
 - Parasitic poles and zeros (ex: package parasitics)




Limitations of CTLE

- High-frequency Noise boosting

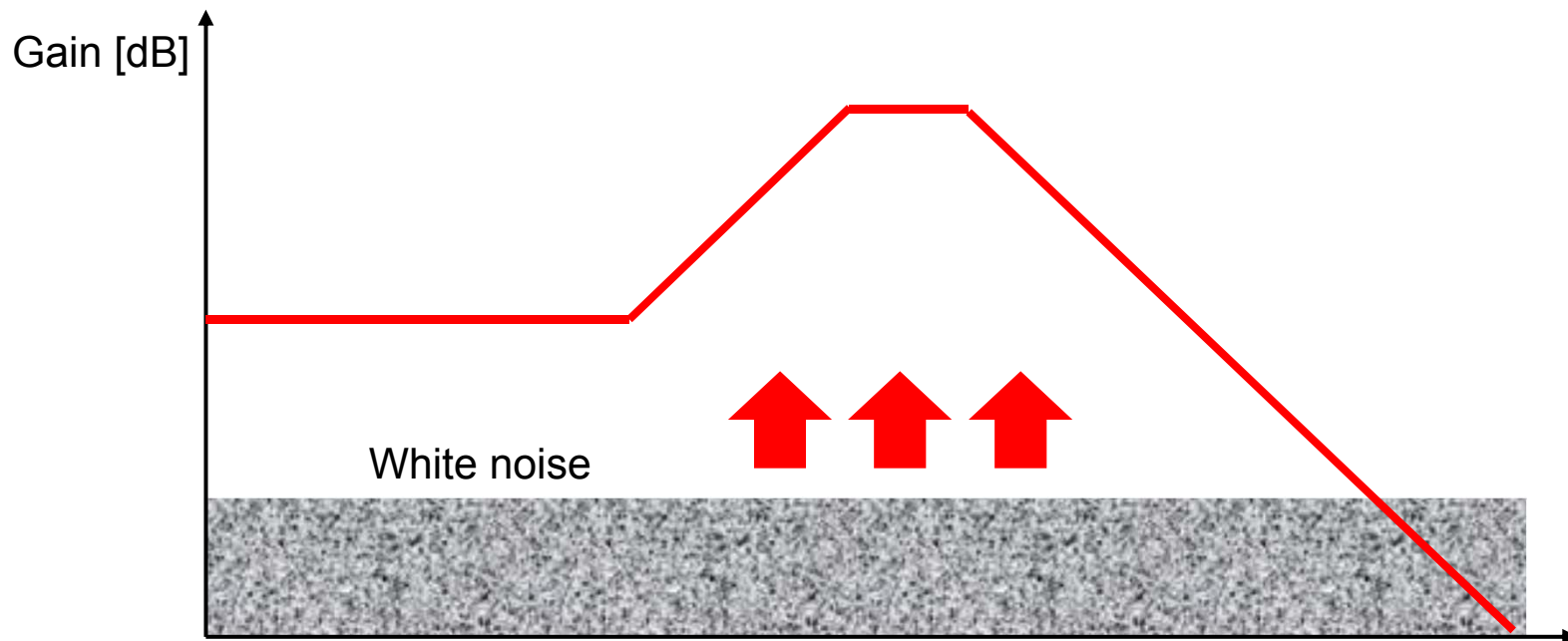



Time-Domain Analysis

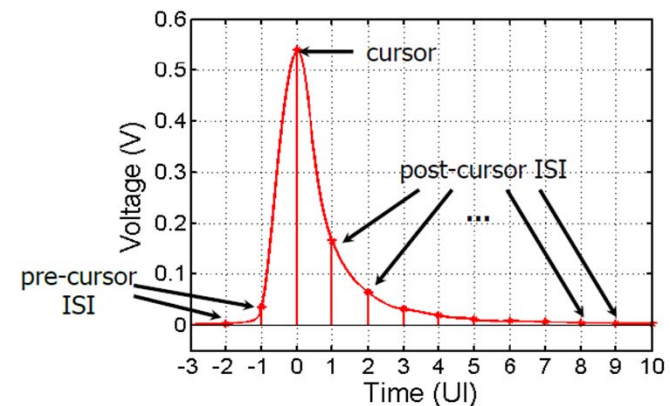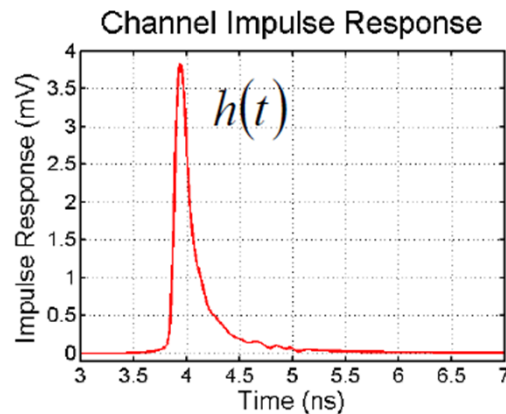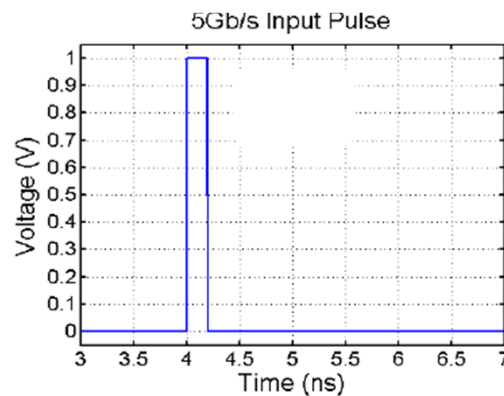- Frequency-Domain Analysis
 - Freq. Response of Input x Freq. Response of Channel \times Equalizer
= Freq. Response of Output
- Time-Domain Analysis



- Equalization: Force pre- and post-cursors to zero

FIR Filter

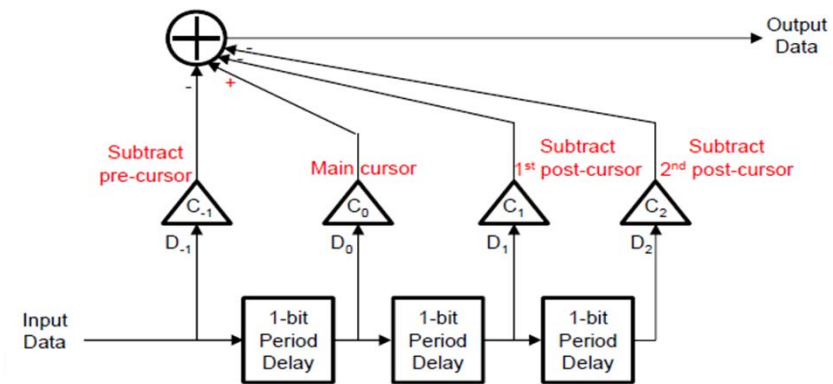
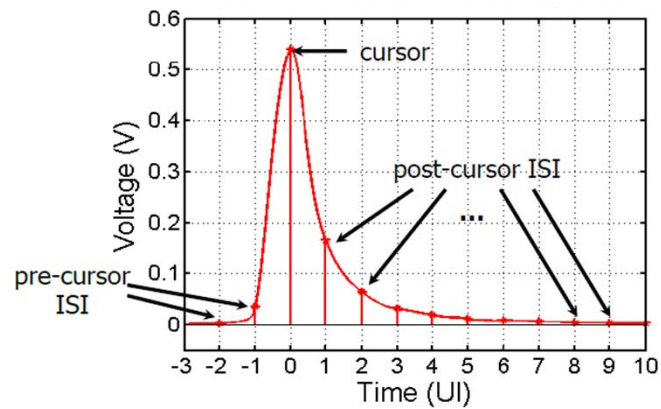


Tap and Delay

➔ FIR (Finite Impulse Response)

IIR (Infinite Impulse Response) for CTLE


FIR Filter

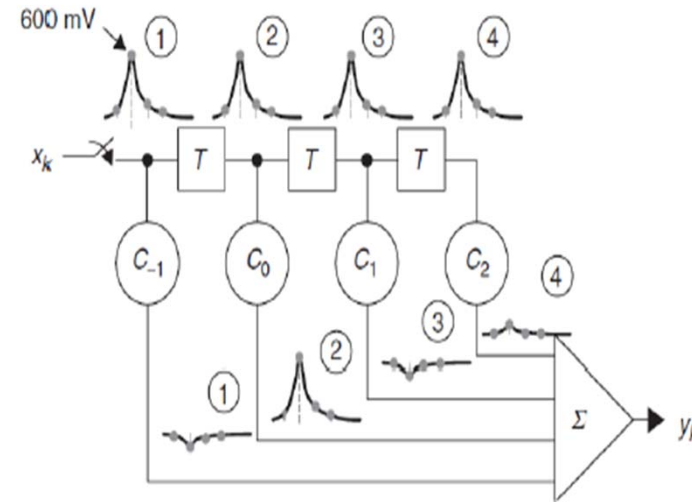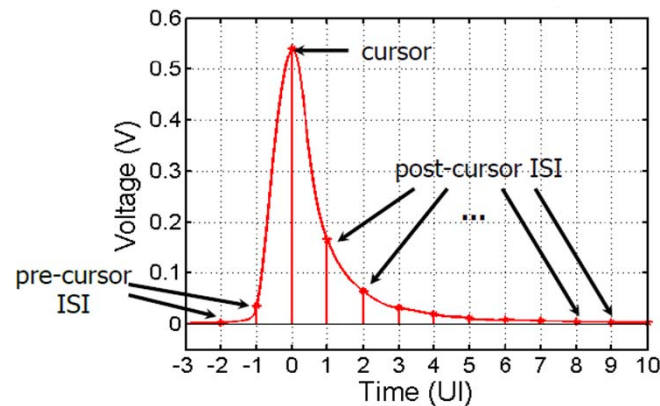

- Difficult to implement Rx FIR filter


Because the precise amount of delay (clock period) is not known in Rx

→ Tx FIR filter

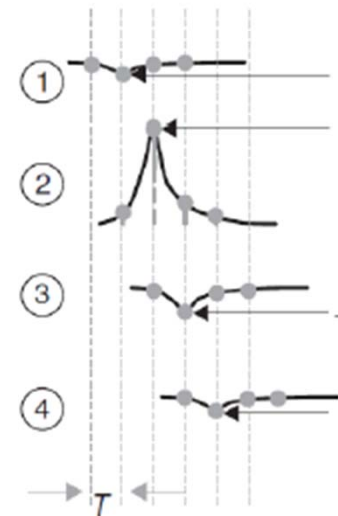


FIR Filter

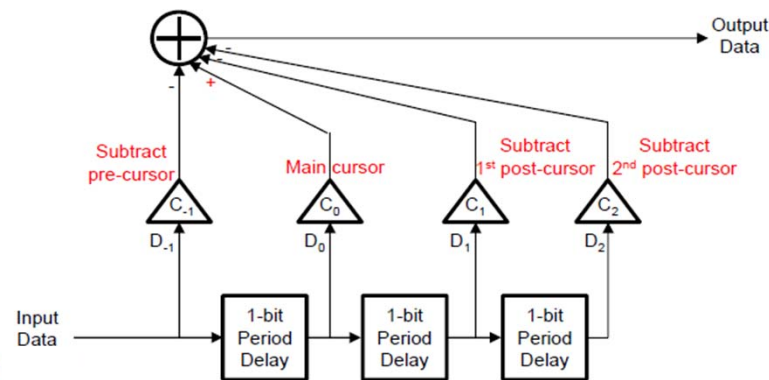- Any CTLE filter can be converted into a discrete-time domain filter
- IIR (Infinite Impulse Response) → FIR (Finite Impulse Response)






Tap and Delay

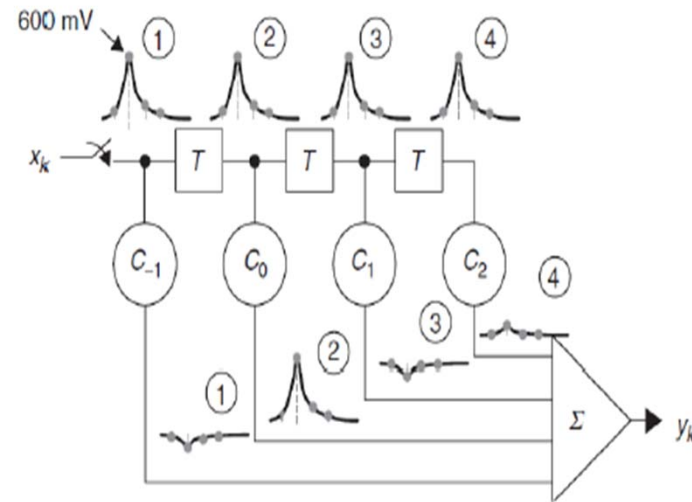



- Hard to implement Rx FIR filter because the precise amount of delay (clock period) is not available in Rx

→ Tx FIR filter

Tx FIR

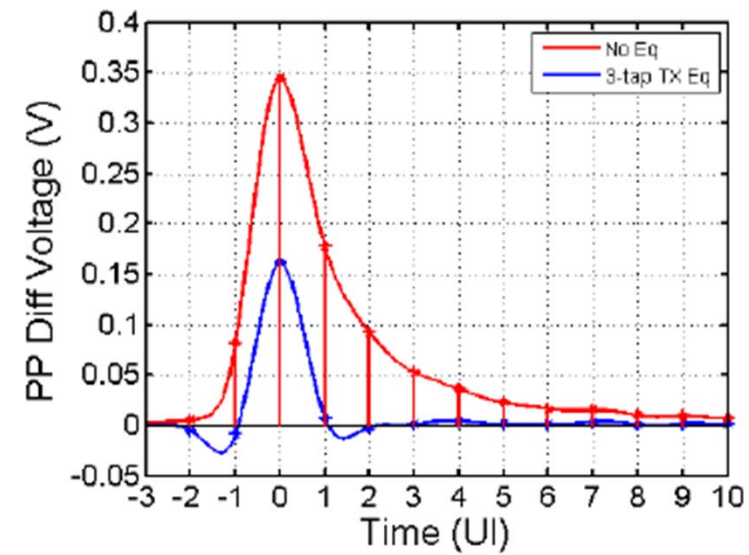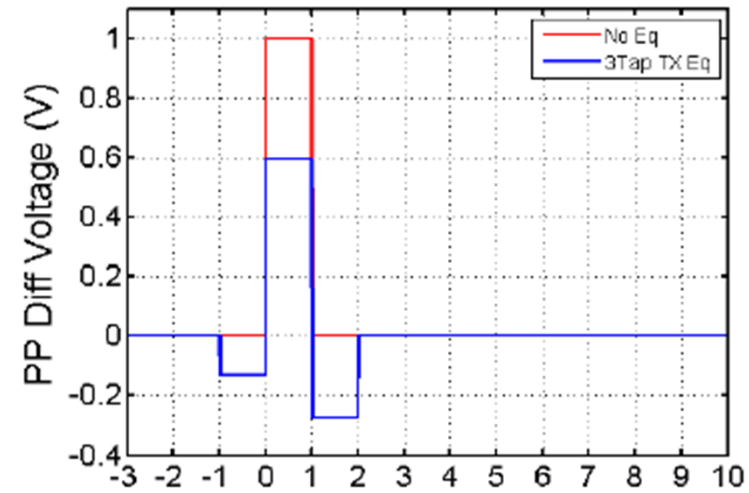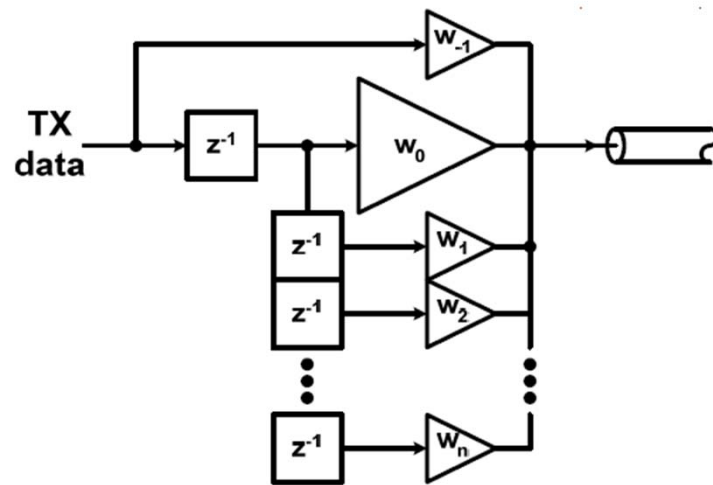

Frequency-Domain Analysis

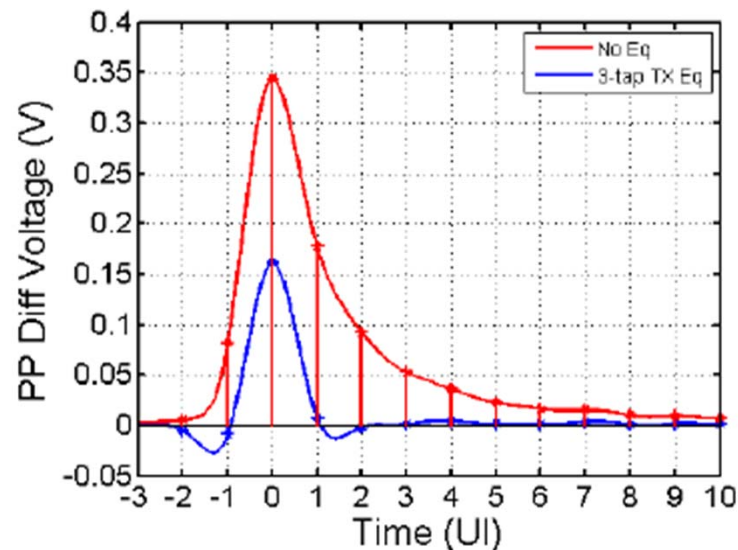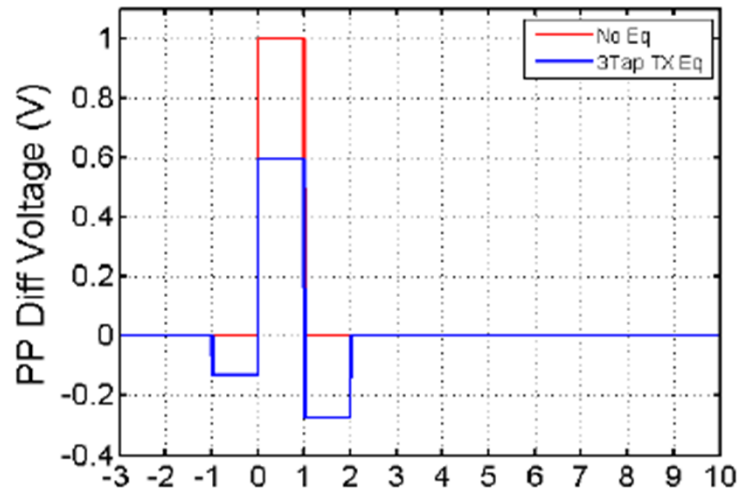

$$W(z) = -0.131 + 0.595z^{-1} - 0.274z^{-2}$$


$$z = e^{j2\pi f T_s} = \cos(2\pi f T_s) + j \sin(2\pi f T_s)$$

Low Frequency Response ($f = 0$)

$$z = \cos(0) + j \sin(0) = 1 : W(f = 0) = 0.190 \Rightarrow -14.4 \text{ dB}$$


Nyquist Frequency Response $\left(f = \frac{1}{2T_s}\right)$
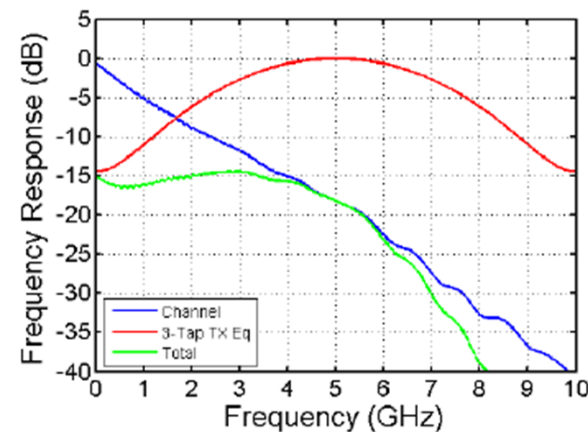
$$z = \cos(\pi) + j \sin(\pi) = -1 : W\left(f = \frac{1}{2T_s}\right) = -1 \Rightarrow 0 \text{ dB}$$



Circuit implementation

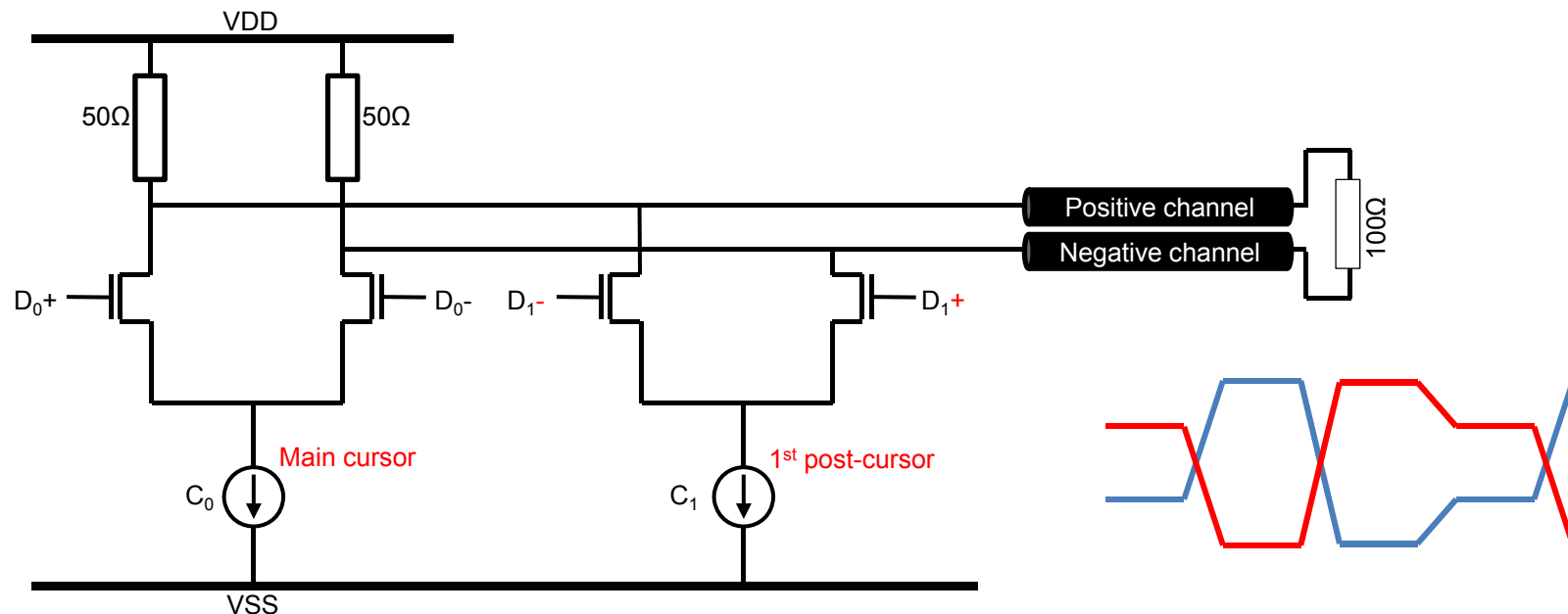- Tx FIR can be easily implemented with current-mode drivers
(For 2-tap Tx FIR)
 - $D_1 = D_0 \rightarrow V_{\text{out,diff}} = \pm 100 \times (C_0 - C_1)/4$
 - $D_1 \neq D_0 \rightarrow V_{\text{out,diff}} = \pm 100 \times (C_0 + C_1)/4$
 - By setting C_1/C_0 , Tx FIR is achieved



Pre-/De-Emphasis

- Tx FIR is also called Feed-Forward Equalizer (FFE) or Pre-/De-Emphasis
 - Pre-emphasis: to enhance high-frequency components
 - De-emphasis: to reduce low-frequency components

